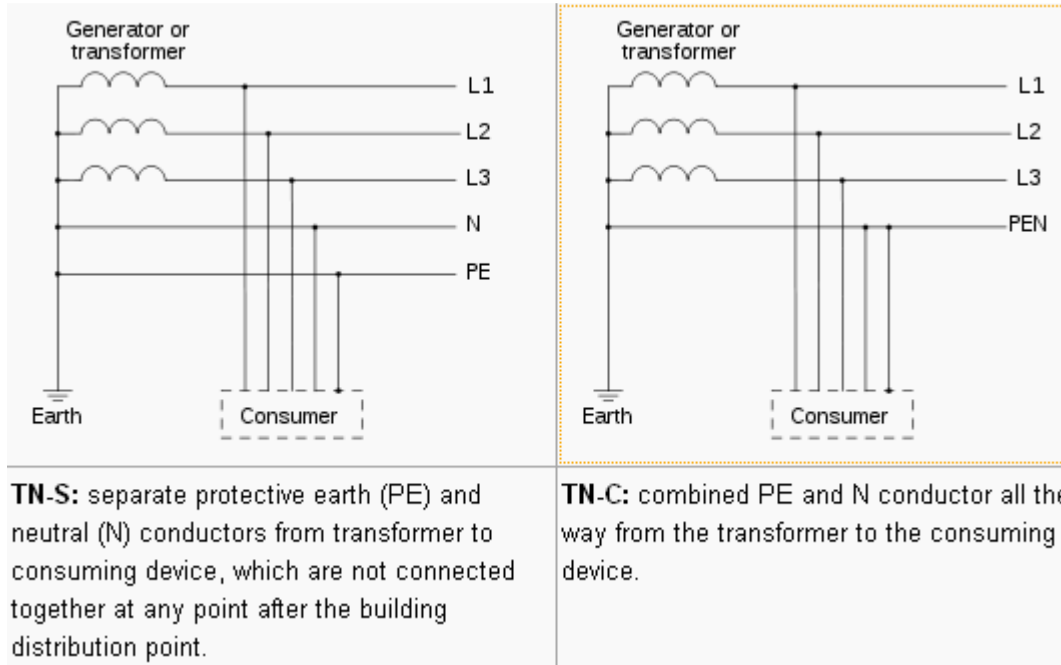


## Answers

Q1)

a)

i)



Since earth fault currents are combined with neutral currents in the TN-C system, it becomes difficult to detect fault currents and operate protective devices at the consumer's installation

b) TT system does not provide a low impedance metallic conductor between enclosures and supply return. Therefore fault current is small. But TN-C-S system provide low impedance metallic conductor between enclosures and supply return. Therefore fault current is large compared to the TT.

c)

i) a) The disconnection time should be according to the regulation

b)  $R_A \times I_{\Delta n} \leq 50 \text{ V}$

ii)  $I_f = \frac{230}{30} = 7.7 \text{ A}$

iii)  $U_f = 7.7 * 20 = 154 \text{ V}$

Q2)

a) You must draw the characteristic curve of fuse and mcb in a same graph. Then you can find the operation of both.

b)

- Heaters :  $\frac{2000}{230} + \frac{7500}{230} * .75 = 33.16 A$
- Cooker :  $\frac{5000}{230} = 21.7 A$
- Socket outlet : 30 A
- Water heater=13 A
- Lighting:  $\frac{2500}{230} * 0.9 = 9.8 A$
- Assumed maximum demand=  $33.16+21.7+30+9.8=107.7 A$

c)

From Table 9A  $4\text{mm}^2$  ( $r1$ ) has a resistance of  $4.61\text{m}\Omega/\text{m}$  and  $1.5\text{mm}^2$  ( $r2$ ) has a resistance of  $(24.20-12.10)= 12.10 \text{ m}\Omega/\text{m}$ .

36 m will have resistance of:  $16.71 \times 36 \times 1.2/1000 = 0.72\Omega$  (multiplier 1.2 for temperature correction)

Then  $Z_s = Z_e + (R1 + R2) = 0.23 + 0.72 = 0.95\Omega$

Maximum earth fault current:

$$I_f = \frac{230}{0.95} = 242.1 A$$

Now use  $I_f$  to calculate disconnection time using characteristic curve of the fuse. It will be just below 5 s.

A  $70\text{C}^0$  thermoplastic cable with a copper conductor has a K value of 115.

Now carry out the adiabatic equation to ensure that c.p.c. is large enough.

$$S = \frac{\sqrt{I^2 * t}}{K} = \frac{\sqrt{242.1^2 * 5}}{115} = 4.72 \text{ mm}^2$$

This shows that the c.p.c. is too small

- Now use 4mm<sup>2</sup>/2.5mm<sup>2</sup>

Now R1 + R2= 12.02 mΩ/m

Total resistance= 12.02 × 36 × 1.2/1000=0.52Ω

Then Z<sub>s</sub> = Z<sub>e</sub> + (R1 + R2)= 0.23 + 0.52 = 0.75Ω

Now we must calculate maximum earth fault current:

$$I_f = \frac{230}{0.75} = 306 \text{ A}$$

Now check disconnection time in Fig 3.3B

Disconnection time is now 3 seconds.

$$S = \frac{\sqrt{I^2 * t}}{K} = \frac{\sqrt{306^2 * 3}}{115} = 4.61 \text{ mm}^2$$

This proves 2.5 mm<sup>2</sup> c.p.c. is not enough.

- Now use 4mm<sup>2</sup>/4mm<sup>2</sup>

Now R1 + R2= 9.22 mΩ/m

Total resistance= 9.22 × 36 × 1.2/1000=0.40Ω

Then Z<sub>s</sub> = Z<sub>e</sub> + (R1 + R2)= 0.23 + 0.4 = 0.63Ω

Now we must calculate maximum earth fault current:

$$I_f = \frac{230}{0.63} = 366 \text{ A}$$

Now check disconnection time in Fig 3.3B

Disconnection time is now 1.4 seconds.

$$S = \frac{\sqrt{I^2 * t}}{K} = \frac{\sqrt{366^2 * 1.4}}{115} = 3.76 \text{ mm}^2$$

This proves 4 mm<sup>2</sup> c.p.c. is suitable.

Q3)

a) See the lecture notes

$$b) R = \frac{\rho}{2\pi l} \ln l/r = \frac{100}{2\pi * 2} * \ln \frac{2}{25 * 10^{-3}} = 34.87 \Omega$$

c)

Electrodes in parallel

Adding chemicals to the soil eg salt

Sharpening the tip of the electrode

Putting gravel stone layer

d) Voltage drop in AB=  $0.55 * 150 * 50 / 1000 = 4.125$  V (Phase to phase)

$$= \frac{4.125}{\sqrt{3}} = 2.38 \text{ V (phase to neutral)}$$

Voltage drop in any one of the lighting circuits=  $18 * 20 * 0.02 = 7.2$  V

Total voltage drop as a percentage =  $(7.2 + 2.38) / 230 * 100 = 4.2\%$