



**University of Moratuwa, Sri Lanka**  
Faculty of Engineering  
Department of Electrical Engineering  
B. Sc. Engineering Honours Degree Course  
Level 2 – Semester 2 Examination

**EE2010 – THEORY OF ELECTRICITY**

Time Allowed: 3 Hours

August 2010

---

**Additional Material**

Graph Paper will be provided if required.

A table of Laplace transforms is provided on the other side of this page.

**Instructions to Candidates**

This paper contains 7 questions in 6 pages, including the cover page.

Answer All Questions.

This examination accounts for 70% of the module assessment.

Each question carries a total 10 marks. Maximum marks allocated for each part of a question is indicated in square brackets at the end of the part.

Total allocation for the paper is 70 marks.

This is a closed book examination and only authorised calculators will be permitted.

**Technical Data:**

Permeability of free space  $\mu_0 = 4\pi \times 10^{-7}$  H/m

Permittivity of free space  $\epsilon_0 = 8.854 \times 10^{-12}$  F/m

Velocity of light in free space  $= 2.998 \times 10^8$  m/s

**Table of Laplace Transforms of common causal functions  $f(t)$**

$f(t)$	$F(s) = \mathcal{L}[f(t)]$
Unit impulse – $\delta t$	1
Unit step – $U(t)$	$\frac{1}{s}$
$t$	$\frac{1}{s^2}$
$t^n$	$\frac{n!}{s^{n+1}}$
$e^{-at}$	$\frac{1}{(s+a)}$
$1 - e^{-at}$	$\frac{a}{s(s+a)}$
$t e^{-at}$	$\frac{1}{(s+a)^2}$
$t^n e^{-at}$	$\frac{n!}{(s+a)^{n+1}}$
$e^{-at} - e^{-bt}$	$\frac{b-a}{(s+a)(s+b)}$
$\sin(\omega t)$	$\frac{\omega}{(s^2 + \omega^2)}$
$\sin(\omega t + \phi)$	$\frac{\omega \cos(\phi) + s \sin(\phi)}{(s^2 + \omega^2)}$
$t \sin(\omega t)$	$\frac{2\omega s}{(s^2 + \omega^2)^2}$
$\cos(\omega t)$	$\frac{s}{(s^2 + \omega^2)}$
$\cos(\omega t + \phi)$	$\frac{s \cos(\phi) - \omega \sin(\phi)}{(s^2 + \omega^2)}$
$t \cos(\omega t)$	$\frac{s^2 - \omega^2}{(s^2 + \omega^2)^2}$
$e^{-at} \sin(\omega t)$	$\frac{\omega}{(s+a)^2 + \omega^2}$
$e^{-at} \cos(\omega t)$	$\frac{s+a}{(s+a)^2 + \omega^2}$
$\sinh(\omega t)$	$\frac{\omega}{(s^2 - \omega^2)}$
$\cosh(\omega t)$	$\frac{s}{(s^2 - \omega^2)}$

### Question 1

- (a) A circuit consists of a parallel combination of (i) an inductance  $L$  in series with a resistance  $R$ , and (ii) a capacitor  $C$ . If the circuit is supplied from an alternating source  $e(t)$  with internal resistance  $r$ , sketch the circuit and write down an expression for the impedance of the circuit at a supply frequency  $\omega$ . [1 mark]
- (b) If  $L=10$  mH,  $R=100$   $\Omega$ ,  $C = 100$   $\mu\text{F}$ ,  $r = 1$   $\Omega$ , and  $e(t) = 100 \sin 1000t$ , determine expressions for the current  $i_L(t)$  through the inductor and the voltage  $v_c(t)$  across the capacitor. [2 marks]
- (c) Sketch a phasor diagram showing all the voltages and currents in the circuit. [2 marks]
- (d) Write an expression for the energy stored in the circuit, and determine its maximum value. [2 marks]
- (e) Determine the energy loss per cycle and the  $Q$  factor of the circuit. [2 marks]
- (f) Determine the resonance frequency of the circuit. [1 mark]

### Question 2

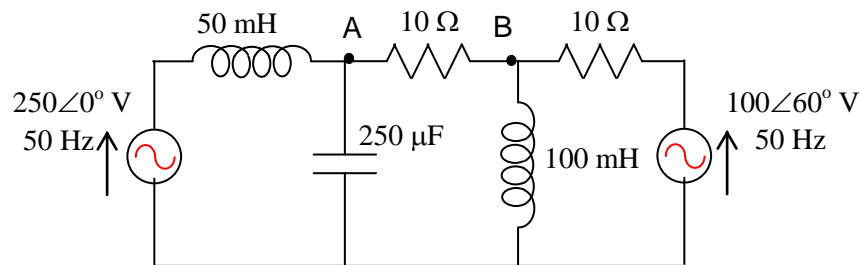


Figure Q2

- (a) For the circuit shown in Figure Q2, convert the voltage sources to equivalent current sources and redraw the circuit. [2 marks]
- (b) Write down the branch-node incidence matrix and the branch admittance matrix for the redrawn circuit. [2 marks]
- (c) Write down the steps in determining the nodal admittance matrix. [2 marks]
- (d) Using nodal matrix analysis, determine the voltages at nodes A and B. [4 marks]

**Question 3**

- (a) Figure Q3a shows the magnetic circuit of a certain inductor. If  $N$  is 100 turns, effective cross-section  $A$  of each limb is  $4 \text{ cm}^2$ , effective magnetic lengths are  $l_o = 15 \text{ cm}$  and  $l_m = 4 \text{ cm}$ ,  $\mu_r$  of magnetic material is 1000, Obtain an expression for the effective inductance of the coil. [3 marks]

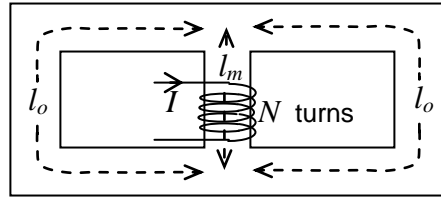


Figure Q3a

- (b) Express the circuit shown in figure Q2b, as an uncoupled circuit. Hence obtain the current supplied from the source, taking the supply voltage as reference. [3 marks]

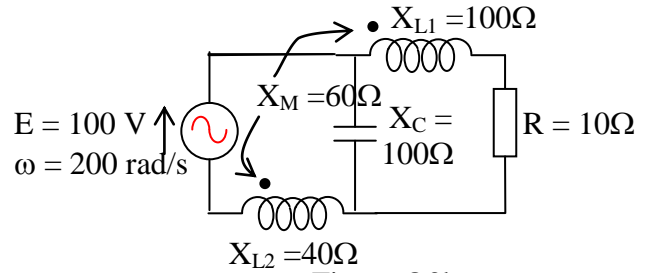


Figure Q3b

- (c) For the circuit shown in Figure Q3c, determine the potential of the star point  $S$  using Millmann's theorem. [4 marks]

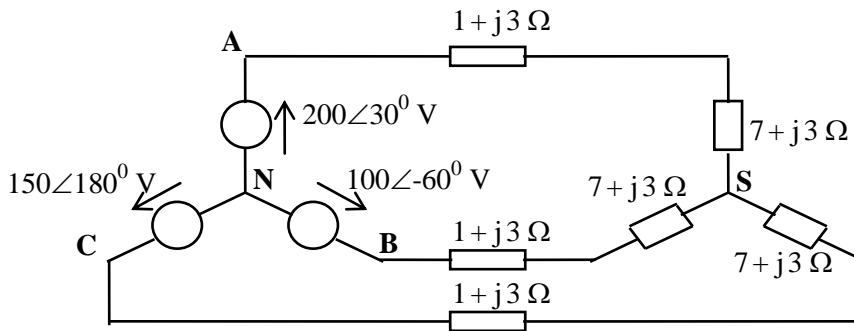


Figure Q3c

**Question 4**

The ABCD parameters of a certain two-port network are known to be  $A = D = (1 + j 0.1)$ ,  $B = j 10 \Omega$ , and  $C = (0.02 + j 0.001) \text{ S}$ .

- (a) Determine the corresponding impedance-parameters of the network. [3 marks]  
 (b) Determine the characteristic impedance  $Z_0$  of the network. [2 marks]

For the circuit shown in figure Q4b,

- (c) write down the Kirchoff's circuit equations [2 marks]  
 (d) determine the currents in all the branches [3 marks]

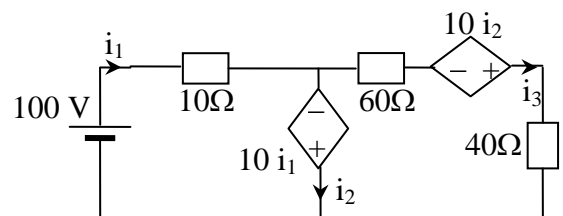


Figure Q4b

### Question 5

A 3 phase, 400 V, 50 Hz balanced supply feeds a balanced star connected load, each arm consisting of a resistance of  $100\ \Omega$  and an inductance of 150 mH in series.

- (a) Determine the line current, the power factor of the load and the total active power supplied to the load. [3 marks]
- (b) Determine the value of the 3 capacitors that must be connected across the load in delta in order to increase the overall power factor to 0.95 lag. [2 marks]

For a system with phase sequence ABC, the symmetrical component currents in phase A of a star connected system are  $I_{A0} = 1.0\angle 90^\circ\text{A}$ ,  $I_{A1} = 10.0\angle 0^\circ\text{A}$  and  $I_{A2} = 3.0\angle -90^\circ\text{A}$ , and the phase voltages are  $V_{AN} = 200\angle 0^\circ\text{V}$ ,  $V_{BN} = 100\angle -60^\circ\text{V}$  and  $V_{CN} = 200\angle 120^\circ\text{V}$ .

- (c) Determine the Symmetrical Components of the phase “A” voltage. [3 marks]
- (d) Determine the power associated with each sequence component. [2 marks]

### Question 6

- (a) Determine the rms value of the half-wave-rectified sinusoidal current  $i(t)$ , with peak value  $I_m$ , shown in figure Q6(a). [2 marks]
- (b) Determine the first 3 significant terms of the Fourier series of the current  $i(t)$ . [4 marks]
- (c) Determine an expression for the supply voltage  $E_s(t)$ , when the current  $i(t)$  flows in the load, as shown in figure Q6(b). [3 marks]
- (d) Determine the average power supplied from the source. [1 mark]

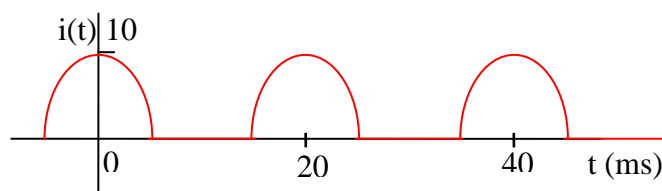


Figure Q6(a)

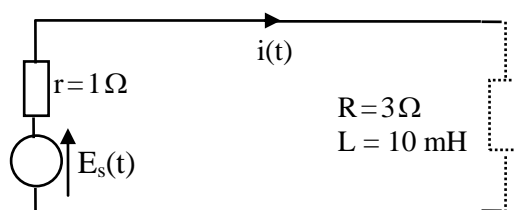


Figure Q6(b)

### Question 7

(a) Determine from first principles the Laplace transform of the causal waveform  $\cos(\omega t + \phi)$ .

[3 marks]

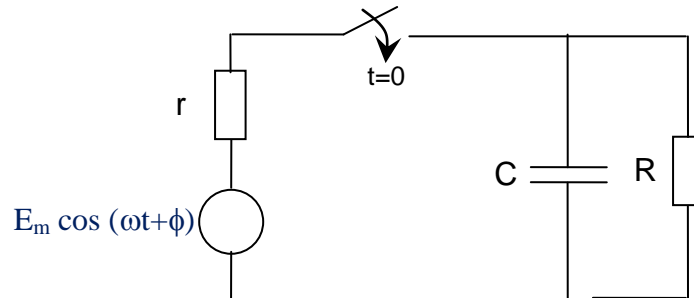


Figure Q7

Figure Q7 shows a circuit in which the capacitor  $C$  has an initial charge  $q_0 = 2$  coulomb. If  $E_m = 100$  kV,  $f = 50$  Hz,  $r = 10 \Omega$ ,  $R = 100 \Omega$ ,  $C = 40 \mu\text{F}$ , and switch  $S$  is closed at time  $t = 0$ ,

(b) draw the equivalent circuit in the Laplace domain,

[3 marks]

(c) determine the Laplace expression for the current supplied from the source,

[2 marks]

(d) determine the time domain solutions for the current through the Resistor  $R$ .

[2 marks]

[END OF QUESTION PAPER]