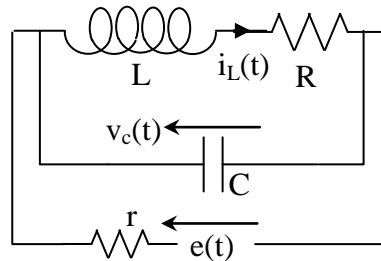




EE 2010 - THEORY OF ELECTRICITY – Short Answers

Level 2 Semester 1 Examination - August 2010

1. (a)

Impedance at angular frequency $\omega = r + 1/j\omega C // (R + j\omega L)$

$$Z = r + \frac{\frac{1}{j\omega C} \times (R + j\omega L)}{\frac{1}{j\omega C} + R + j\omega L} = r + \frac{R + j\omega L}{1 + j\omega C(R + j\omega L)}$$

1 mark

(b) $L=10$ mH, $R=100 \Omega$, $C = 100 \mu\text{F}$, $r = 1 \Omega$ and $e(t) = 100 \sin 1000t$
Calculating with peak values instead of with rms values,

$$I_m = E / \left(r + \frac{R + j\omega L}{1 + j\omega C(R + j\omega L)} \right) = \frac{E(1 + j\omega C(R + j\omega L))}{R + r - \omega^2 LCr + j\omega(CrR + L)}$$

$$I_m = \frac{100(1 + j1000 \times 100 \times 10^{-6}(100 + j1000 \times 0.01))}{100 + 1 - 1000^2 \times 0.01 \times 100 \times 10^{-6} \times [1 + j1000 \times (100 \times 10^{-6} \times 1 \times 100 + 0.01)]}$$

$$= \frac{(100 + j1000 - 100)}{100 + j(10 + 10)} = \frac{j1000}{101 + j20} = \frac{1000 \angle 90^\circ}{101.98 \angle 11.31^\circ} = 9.806 \angle 78.69^\circ$$

$$I_{Lm} = I_m \times \frac{\frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}} = I_m \times \frac{1}{1 + j\omega C(R + j\omega L)}$$

$$= \frac{j1000}{100 + j20} \times \frac{1}{1 + j1000 \times 100 \times 10^{-6} \times (100 + j1000 \times 0.01)}$$

$$I_{Lm} = \frac{j1000}{100 + j20} \times \frac{1}{j10} = \frac{100}{101.98 \angle 11.31^\circ} = 0.9806 \angle -11.31^\circ$$


$$i_L(t) = 0.980 \sin(1000t - 11.31^\circ)$$

$$V_{Cm} = I_{Lm}(R + j\omega L) = \frac{j100}{100 + j20} \times (100 + j1000 \times 0.01)$$

$$= 0.9806 \angle -11.31^\circ \times 100.5 \angle 5.71^\circ = 98.55 \angle -5.60^\circ$$

$$v_C(t) = 98.55 \sin(1000t - 5.60^\circ)$$

(c)

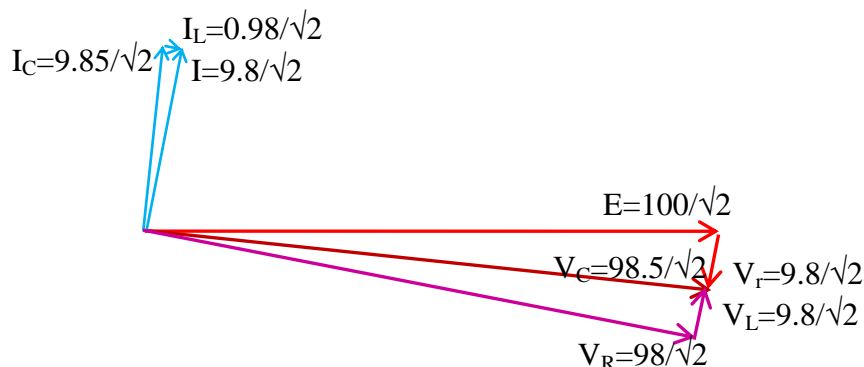

1 mark

1 mark

2 marks



EE 2010 - THEORY OF ELECTRICITY – Short Answers

(d) Energy stored $W = \frac{1}{2} L i^2 + \frac{1}{2} C v^2$

$= \frac{1}{2} \times 0.01 \times 0.9806^2 \times \sin^2(1000t - 11.31^\circ) + \frac{1}{2} \times 10^{-4} \times 98.55^2 \times \sin^2(1000t - 5.59^\circ)$

Maximum occurs at $t = 1.67$ ms when the two terms have values 0.00476 and 0.48560

Maximum Energy stored = 0.490 J

1 mark

1 mark

1 mark

(e) Energy loss per cycle = $[(9.8/\sqrt{2})^2 \times 1 + (0.98/\sqrt{2})^2 \times 100] \times 2\pi/1000 = 0.604$ J

Q-factor of circuit = $2\pi \times$ Maximum Energy stored/ Energy loss per cycle

$= 2\pi \times 0.49/0.604 = 5.1$

1 mark

(f) Resonance frequency = ω_0

$$Z = r + \frac{R + j\omega L}{1 + j\omega C(R + j\omega L)} = r + \frac{R + j\omega L}{1 - \omega^2 LC + j\omega CR}$$

Considering unity power factor resonance, imaginary part = 0

$$\therefore \frac{R}{1 - \omega^2 LC} = \frac{\omega L}{\omega CR} \text{ gives } 1 - \omega^2 LC = \frac{R^2 C}{L}, \quad \omega = \sqrt{\frac{L - R^2 C}{L^2 C}}$$

1 mark

$$\omega_o = \sqrt{\frac{0.01 - 100^2 \times 10^{-4}}{0.01^2 \times 10^{-4}}} = \sqrt{\frac{0.01 - 100^2 \times 10^{-4}}{0.01^2 \times 10^{-4}}} = \text{imaginary.}$$

Thus resonance does not occur for the particular values of components.

2. (a)

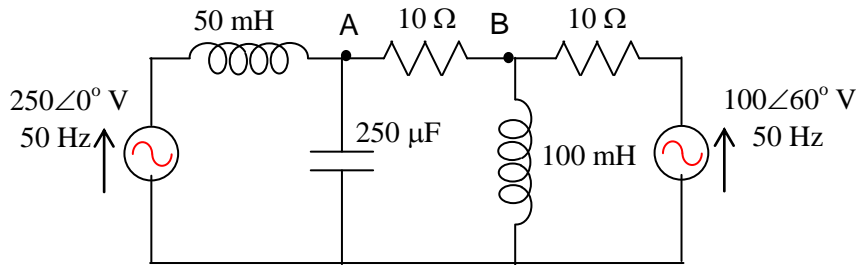



Figure Q2

$50 \text{ mH} \rightarrow 2\pi \times 50 \times 0.05 \rightarrow j 15.708 \Omega, 100 \text{ mH} \rightarrow j 31.416 \Omega$

$250 \mu\text{F} \rightarrow 1/(2\pi \times 50 \times 250 \times 10^{-6}) \rightarrow -j 12.732 \Omega$

Equivalent current sources are $250\angle 0^\circ / j15.708 = 15.915\angle -90^\circ \text{ A}$, $100\angle 60^\circ / 10 = 10\angle 60^\circ \text{ A}$

The converted circuit is as follows

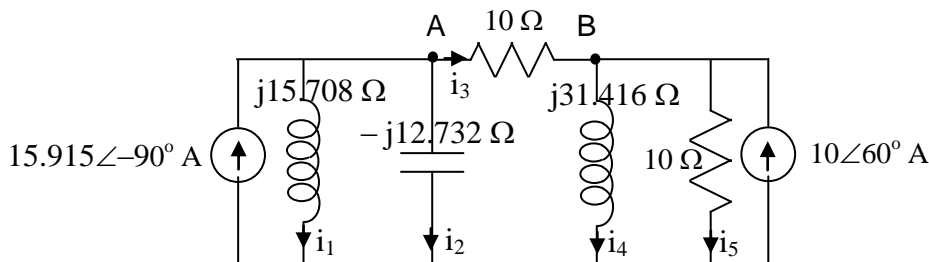

2 marks



EE 2010 - THEORY OF ELECTRICITY – Short Answers

(b) Taking the common node as reference and eliminating it from equations

The branch-node incidence matrix and the branch admittance matrix are given by

$$[1 \text{ mark}] \begin{bmatrix} 1 & 0 \\ 1 & 0 \\ 1 & -1 \\ 0 & 1 \\ 0 & 1 \end{bmatrix}, \quad [Y_b] = \begin{bmatrix} -j0.0637 & 0 & 0 & 0 & 0 \\ 0 & j0.0785 & 0 & 0 & 0 \\ 0 & 0 & 0.1 & 0 & 0 \\ 0 & 0 & 0 & -j0.0318 & 0 \\ 0 & 0 & 0 & 0 & 0.1 \end{bmatrix} \quad [1 \text{ mark}]$$

(c) The nodal admittance matrix is given by

$$\begin{bmatrix} 1 & 1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 1 \end{bmatrix} \begin{bmatrix} -j0.0637 & 0 & 0 & 0 & 0 \\ 0 & j0.0785 & 0 & 0 & 0 \\ 0 & 0 & 0.1 & 0 & 0 \\ 0 & 0 & 0 & -j0.0318 & 0 \\ 0 & 0 & 0 & 0 & 0.1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & 0 \\ 1 & -1 \\ 0 & 1 \\ 0 & 1 \end{bmatrix} = \quad [1 \text{ mark}]$$

$$[Y_N] = \begin{bmatrix} -j0.0637 + j0.0785 + 0.1 & -0.1 \\ -0.1 & 0.1 - j0.0318 + 0.1 \end{bmatrix} \quad [1 \text{ mark}]$$

(d) The nodal current vector is given by

$$[I_N] = \begin{bmatrix} 15.915 \angle -90^\circ \\ 10 \angle 60^\circ \end{bmatrix}$$

$$\begin{bmatrix} 15.915 \angle -90^\circ \\ 10 \angle 60^\circ \end{bmatrix} = \begin{bmatrix} -j0.0637 + j0.0785 + 0.1 & -0.1 \\ -0.1 & 0.01 - j0.0318 + 0.1 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix}$$

$$\begin{bmatrix} 15.915 \angle -90^\circ \\ 10 \angle 60^\circ \end{bmatrix} = \begin{bmatrix} 0.1 + j0.0148 & -0.1 \\ -0.1 & 0.2 - j0.0318 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} \quad [2 \text{ marks}]$$

$$\text{Determinant} = 0.02 + 0.000470 - j0.00318 + j0.00296 - 0.01 = 0.010470 - j0.00022$$

$$\Delta = 0.0105 \angle -1.3^\circ$$

$$\begin{bmatrix} V_A \\ V_B \end{bmatrix} = \frac{1}{\Delta} \begin{bmatrix} 0.2 - j0.0318 & 0.1 \\ 0.1 & 0.1 + j0.0148 \end{bmatrix} \begin{bmatrix} 15.915 \angle -90^\circ \\ 10 \angle 60^\circ \end{bmatrix}$$

$$V_A = 221.2 \angle -89.0^\circ \quad [2 \text{ marks}]$$

$$V_B = 71.6 \angle -59.2^\circ$$



EE 2010 - THEORY OF ELECTRICITY – Short Answers

3. (a)

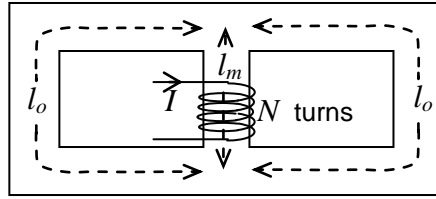


Figure Q3a

$N = 100$ turns, $A = 4 \text{ cm}^2$, $l_o = 15 \text{ cm}$, $l_m = 4 \text{ cm}$, $\mu_r = 1000$

Reluctance $S = l/\mu A$

$$S_o = \frac{0.15}{4\pi \times 10^{-7} \times 1000 \times 4 \times 10^{-4}} = 298.4 \times 10^3 \text{ H}^{-1}$$

$$S_m = \frac{0.04}{4\pi \times 10^{-7} \times 1000 \times 4 \times 10^{-4}} = 79.6 \times 10^3 \text{ H}^{-1}$$

Effective reluctance of magnetic circuit as seen from coil = $79.6 \times 10^3 + 298.4 \times 10^3 / 2$
 = $228.8 \times 10^3 \text{ H}^{-1}$

Thus, effective inductance = $N^2/S = 100^2/228.8 \times 10^3 = 0.0437 \text{ H} = 43.7 \text{ mH}$

3 marks

(b)


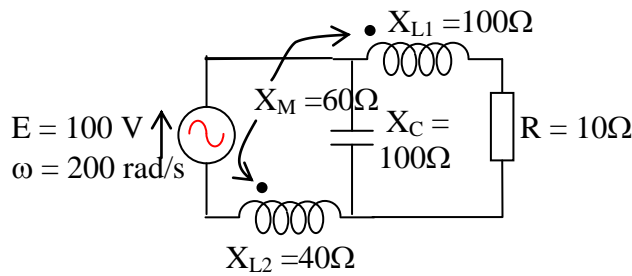


Figure Q3b

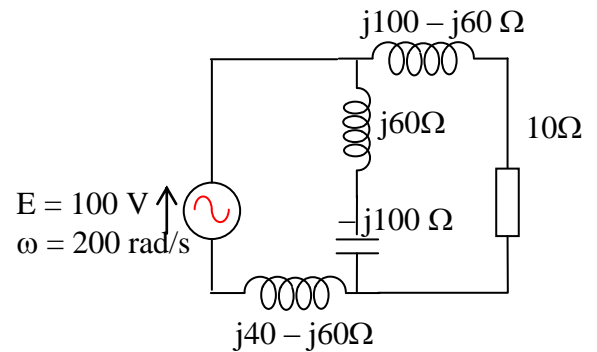The non-coupled equivalent circuit is as follows



The current supplied from the source is given as

$$I_s = \frac{100 \angle 0^\circ}{-j20 + (-j40) // (10 + j40)} \quad I_s = \frac{100 \angle 0^\circ}{-j20 + \frac{(-j40) \times (10 + j40)}{-j40 + 10 + j40}} = \frac{100 \angle 0^\circ}{-j20 - j40 + 160}$$

$$I_s = \frac{100 \angle 0^\circ}{160 - j60} = \frac{5 \angle 0^\circ}{8 - j3} = \frac{5 \angle 0^\circ}{8.544 \angle -20.556^\circ} = 0.585 \angle 20.556^\circ \text{ A}$$

3 marks

(c)

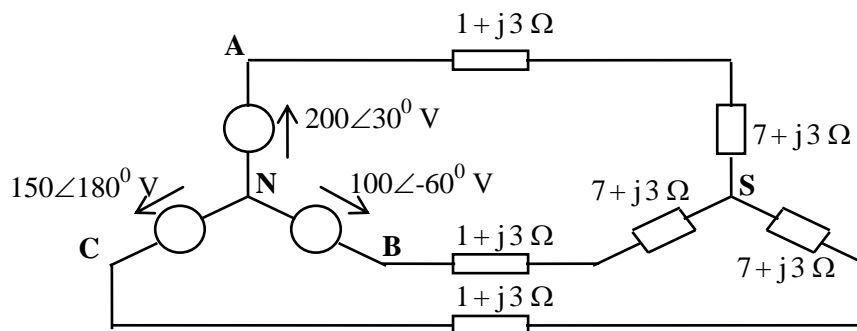


Figure Q3c

**EE 2010 - THEORY OF ELECTRICITY – Short Answers**

Considering the potential of the neutral N as zero, from Millmann's theorem

$$V_S = V_{SN} = \frac{\sum[Y][V]}{\sum[Y]} = \frac{\frac{1}{8+j6} \times 200 \angle 30^\circ + \frac{1}{8+j6} \times 100 \angle -60^\circ + \frac{1}{8+j6} \times 150 \angle 180^\circ}{\frac{1}{8+j6} + \frac{1}{8+j6} + \frac{1}{8+j6}}$$

$$V_S = \frac{200 \angle 30^\circ + 100 \angle -60^\circ + 150 \angle 180^\circ}{3} = \frac{173.2 + j100 + 50 - j86.6 - 150}{3} = 24.4 + j4.47$$

$$V_S = 24.8 \angle 10.4^\circ \text{ V}$$

4 marks

4. (a) $A = D = (1 + j0.1)$, $B = j10 \Omega$, and $C = (0.02 + j0.001) \text{ S}$.

Considering the direction of I_2 corresponding to impedance parameters,

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix} = \begin{bmatrix} 1+j0.1 & j10 \\ 0.02+j0.001 & 1+j0.1 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}, \text{ and } \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Expansion gives

$$V_1 = (1+j0.1)V_2 - j10 I_2, \quad I_1 = (0.02+j0.001)V_2 - (1+j0.1) I_2$$

Re-arranging gives

$$(0.02+j0.001)V_2 = I_1 + (1+j0.1) I_2$$

$$\text{Giving } z_{21} = 1/C = 1/(0.02+j0.001) = 49.94 \angle -2.86^\circ,$$

$$z_{22} = D/C = (1+j0.1)/(0.02+j0.001) = 50.19 \angle 8.57^\circ$$

Also

$$V_1 = (1+j0.1)[1/(0.02+j0.001) \times I_1 + (1+j0.1)/(0.02+j0.001) \times I_2] - j10 I_2$$

$$\text{Giving } z_{11} = A/C = (1+j0.1)/(0.02+j0.001) = 50.19 \angle 8.57^\circ,$$

$$z_{12} = -B + AD/C = 49.94 \angle -2.86^\circ$$

$$[Z] = \begin{bmatrix} 50.19 \angle 8.57^\circ & 49.94 \angle -2.86^\circ \\ 49.94 \angle -2.86^\circ & 50.19 \angle 8.57^\circ \end{bmatrix}$$

3 marks

- (b) For the characteristic impedance Z_0 , $V_1 = Z_0 \times I_1$, $V_2 = Z_0 \times (-I_2)$

$$\text{i.e. } \begin{bmatrix} Z_0 I_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1+j0.1 & j10 \\ 0.02+j0.001 & 1+j0.1 \end{bmatrix} \begin{bmatrix} -Z_0 I_2 \\ -I_2 \end{bmatrix}$$

$$\therefore \frac{Z_0 I_1}{I_1} = \frac{(1+j0.1)(-Z_0 I_2) + j10(-I_2)}{(0.02+j0.001)(-Z_0 I_2) + (1+j0.1)(-I_2)}$$

$$\text{i.e. } Z_0 = \frac{(1+j0.1)Z_0 + j10}{(0.02+j0.001)Z_0 + (1+j0.1)}$$

$$(0.02+j0.001)Z_0^2 + (1+j0.1)Z_0 = (1+j0.1)Z_0 + j10$$



EE 2010 - THEORY OF ELECTRICITY – Short Answers

$$Z_0^2 = \frac{1}{(0.0001 - j0.002)} = \frac{1}{0.0020025 \angle -87.14^\circ} = 499.4 \angle 87.14^\circ, Z_0 = 22.35 \angle 43.57^\circ \Omega$$

2 marks

(c)

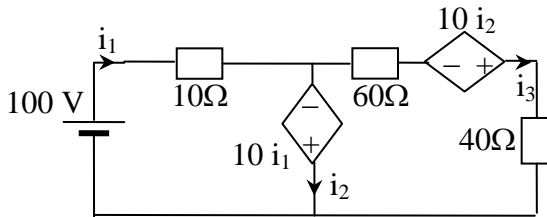


Figure Q4b

$$100 = 10 i_1 - 10 i_1, i_1 = i_2 + i_3, -10 i_1 = (60+40) i_3 - 10 i_2$$

2 marks

(d) Solution is not possible.

3 marks

5. 3 phase, 400 V, 50 Hz, balanced supply.

Balanced star connected load R= 100 Ω and L= 150 mH in series.

(a) 150 mH → 100π×0.15 → j 47.12 Ω

$$\text{Line current} = (400 \angle 0^\circ / \sqrt{3}) / (100 + j47.12) = 230.9 / 110.55 \angle 25.23^\circ = 2.089 \angle -25.23^\circ \text{ A}$$

$$\text{Power factor of the load} = \cos 25.23^\circ = 0.905 \text{ lag}$$

$$\text{Total active power supplied to load} = \sqrt{3} \times 400 \times 2.089 \times 0.905 = 1310 \text{ W}$$

3 marks

(b) Value of 3 capacitors in delta to increase power factor 0.95 lag.

P remains unchanged at 1310 W

$$\text{Original } Q = \sqrt{3} \times 400 \times 2.089 \times \sin 25.23^\circ = 617 \text{ var}$$

$$\text{New power factor angle corresponding to } 0.95 \text{ lag} = \cos^{-1} 0.95 = 18.19^\circ$$

$$\text{New reactive power} = 1310 \times \tan 18.19^\circ = 430 \text{ kvar}$$

$$\therefore \text{reactive power supplied by capacitors} = 617 - 430 = 187 \text{ kvar}$$


$$\therefore 3 \times C \times 100\pi \times 400^2 = 187$$

$$C = 1.24 \mu\text{F in each arm of the delta}$$

Phase sequence ABC,

$$I_{A0} = 1.0 \angle 90^\circ \text{ A}, I_{A1} = 10.0 \angle 0^\circ \text{ A and } I_{A2} = 3.0 \angle -90^\circ \text{ A, and}$$
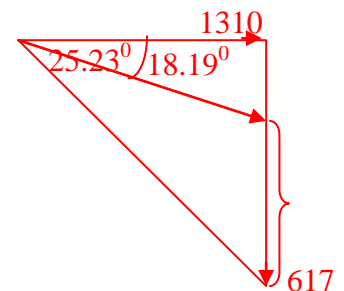
$$V_{AN} = 200 \angle 0^\circ \text{ V}, V_{BN} = 100 \angle -60^\circ \text{ V and } V_{CN} = 200 \angle 120^\circ \text{ V.}$$



2 marks



EE 2010 - THEORY OF ELECTRICITY – Short Answers

(c) The Symmetrical Components of the phase “A” voltage are given by

$$\begin{bmatrix} V_{A0} \\ V_{A1} \\ V_{A2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} 200\angle 0^\circ \\ 100\angle -60^\circ \\ 200\angle 120^\circ \end{bmatrix}$$

$$V_{A0} = 1/3 (200\angle 0^\circ + 100\angle -60^\circ + 200\angle 120^\circ) \\ = (200 + 50 - j 86.6 - 100 + j 173.2)/3 = 50 + j 28.87 = 57.74\angle 30^\circ \text{ V}$$

$$V_{A1} = 1/3 (200\angle 0^\circ + 100\angle (120^\circ - 60^\circ) + 200\angle (120^\circ + 240^\circ)) \\ = (200 + 50 + j 86.6 + 200)/3 = 150 + j 28.87 = 152.75\angle 10.89^\circ \text{ V}$$

$$V_{A2} = 1/3 (200\angle 0^\circ + 100\angle (240^\circ - 60^\circ) + 200\angle (120^\circ + 120^\circ)) \\ = (200 - 100 - 100 - j 173.2)/3 = -j 57.74 = 57.74\angle -90^\circ \text{ V}$$

3 marks

(d) Power associated with each sequence component.

$$P_0 = 3 \times 57.74 \times 1.0 \times \cos 60^\circ = 86.6 \text{ W}$$

$$P_1 = 3 \times 152.75 \times 10.0 \times \cos 10.89^\circ = 4500 \text{ W}$$

$$P_2 = 3 \times 57.74 \times 3.0 \times \cos 0^\circ = 519.6 \text{ W}$$

2 marks

6.

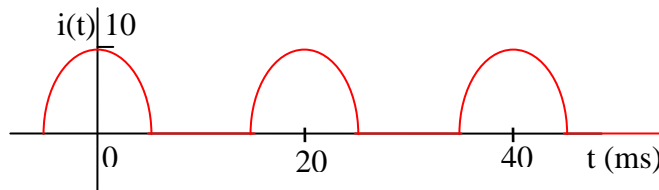


Figure Q6(a)

$$\text{Period} = 20 \text{ ms} = 0.02 \text{ s}, \omega = 2\pi/0.02 = 100\pi \text{ rad/s}$$

$$\begin{aligned} \text{(a) } i(t) &= 10 \cos 100\pi t & -5\text{ms} \leq t \leq 5 \text{ ms} \\ &= 0 & 10\text{ms} \leq t \leq 15 \text{ ms} \end{aligned}$$

$$\text{rms value} = \sqrt{\frac{2}{0.02} \int_0^{0.005} 10^2 \cos^2 100\pi t \cdot dt} = \sqrt{\frac{100^2}{2} \int_0^{0.005} (1 + \cos 200\pi t) \cdot dt}$$

$$= \sqrt{\frac{100^2}{2} \left(t + \frac{\sin 200\pi t}{200\pi} \right) \Big|_0^{0.005}} = \sqrt{\frac{100^2}{2} \left(0.005 + \frac{\sin \pi}{200\pi} \right)} = 5 \text{ A}$$

2 marks

$$\text{(b) } f(t) = A_0/2 + \sum A_n \cos n\omega t + B_n \sin n\omega t$$

$$\text{function } f(t) \text{ has mean value} = 10/\pi \rightarrow A_0/2 = 3.18 \text{ A}$$

$$f(t) \text{ is even} \rightarrow B_n = 0 \text{ for all } n$$

$$\therefore A_n = 2 \times \frac{2}{0.02} \int_0^{0.005} 10 \cos 100\pi t \cdot \cos n100\pi t \cdot dt + 0$$

$$= 1000 \int_0^{0.005} [\cos 100\pi(n+1)t + \cos n100\pi(n-1)t] \cdot dt$$

1 mark



EE 2010 - THEORY OF ELECTRICITY – Short Answers

$$A_n = 1000 \times \left[\frac{\sin 100\pi(n+1)t}{100\pi(n+1)} + \frac{\sin 100\pi(n-1)t}{100\pi(n-1)} \right]_0^{0.005}$$

$$= 10 \times \left[\frac{\sin(n+1)\frac{\pi}{2}}{(n+1)\pi} + \frac{\sin(n-1)\frac{\pi}{2}}{(n-1)\pi} \right]$$

2 marks

Cannot be calculated for $n = 1$.

$$A_1 = 2 \times \frac{2}{0.02} \int_0^{0.005} 10 \cos 100\pi t \cdot \cos 100\pi t \cdot dt = 1000 \int_0^{0.005} (1 + \cos 200\pi t) \cdot dt = 1000 \times \left[t + \frac{\sin 200\pi t}{200\pi} \right]_0^{0.005}$$

$$A_1 = 1000[0.005 + 0] = 5$$

$$A_2 = 10 \times \left[\frac{\sin \frac{3\pi}{2}}{3\pi} + \frac{\sin \frac{\pi}{2}}{\pi} \right] = \frac{10}{3\pi} (-1 + 3) = \frac{20}{3\pi} = 2.122,$$

$$A_3 = 10 \times \left[\frac{\sin \frac{4\pi}{2}}{4\pi} + \frac{\sin \frac{2\pi}{2}}{2\pi} \right] = 0,$$

$$A_4 = 10 \times \left[\frac{\sin \frac{5\pi}{2}}{5\pi} + \frac{\sin \frac{3\pi}{2}}{3\pi} \right] = \frac{10}{15\pi} (3 - 5) = -\frac{4}{3\pi} = -0.424$$

1 mark

$$\therefore i(t) = 3.18 + 5 \cos 25\pi t + 2.122 \cos 50\pi t - 0.424 \cos 100\pi t + \dots$$

(c)

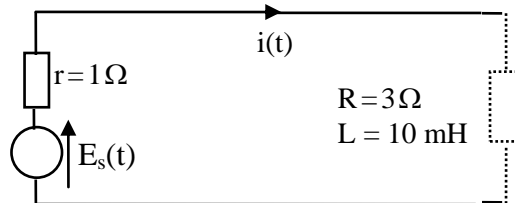


Figure Q6(b)

$$E_s(t) = 4 i(t) + 0.01 di(t)/dt$$

$$\therefore E_s(t) = 12.72 + 20 \cos 25\pi t + 8.488 \cos 50\pi t - 1.796 \cos 100\pi t + \dots$$

$$+ 1.25 \sin 25\pi t + 1.061 \sin 50\pi t - 0.424 \cos 100\pi t + \dots$$

3 mark

$$\text{Average power supplied} = 12.72 \times 3.18 + (20 \times 5 + 8.488 \times 2.122 + 1.796 \times 0.424 + \dots) / (\sqrt{2} \times \sqrt{2})$$

$$= 40.45 + 50 + 0.52 + 0.38 + \dots = 91.5 \text{ W}$$

1 mark




EE 2010 - THEORY OF ELECTRICITY – Short Answers

7. (a) Derivation from first principles of Laplace transform of causal waveform
- $\cos(\omega t + \phi)$

$$L[\cos(\omega t + \phi).H(t)] = \frac{s}{s^2 + \omega^2} \cos \phi - \frac{\omega}{s^2 + \omega^2} \sin \phi$$

3 marks

- (b)

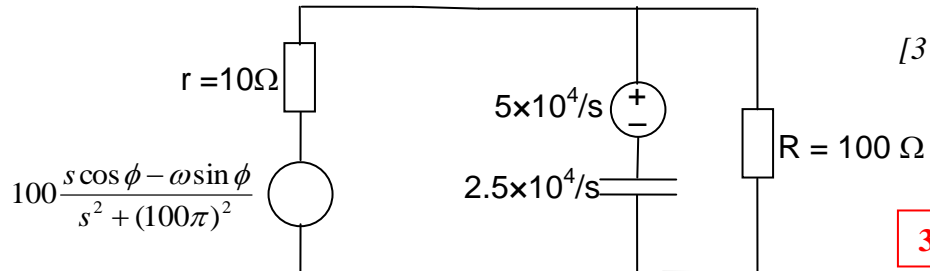

[3 marks]

3 marks

$q_0 = 2$ coulomb, $E_m = 100$ kV, $f = 50$ Hz, $r = 10 \Omega$, $R = 100 \Omega$, $C = 40 \mu\text{F}$

Since ϕ is not specified, assuming it as 0° , $\omega = 100\pi$

- (c) Laplace transform for the current supplied from the source can be obtained from superposition.

$$I(s) = \frac{100s}{s^2 + (100\pi)^2} - \frac{100 \times \frac{2.5 \times 10^4}{s}}{10 + \frac{2.5 \times 10^4}{s}} - \frac{\frac{100 \times 5 \times 10^4}{s}}{\frac{2.5 \times 10^4}{s} + \frac{100 \times 10}{100 + 10}}$$

$$I(s) = \frac{100s}{s^2 + (100\pi)^2} \times \frac{100s + 2.5 \times 10^4}{10(100s + 2.5 \times 10^4) + 250 \times 10^4} - \frac{500 \times 10^4}{275 \times 10^4 + 1000s} - \frac{10s^2 + 2500s - 5000s^2 - 50 \times 10^6 \pi^2}{(s^2 + 100^2 \pi^2)(s + 2750)} = \frac{9.10s - 29.1}{(s^2 + 100^2 \pi^2)} - \frac{4999}{(s + 2750)}$$

2 marks

- (d) Time domain solutions for the current through the Resistor R

$$i(t) = 9.10 \cos 100\pi t - (29.1/100\pi) \sin 100\pi t - 4999 e^{-2750t}$$

$$i(t) = 9.10 \cos 100\pi t - 0.093 \sin 100\pi t - 4999 e^{-2750t}$$

2 marks