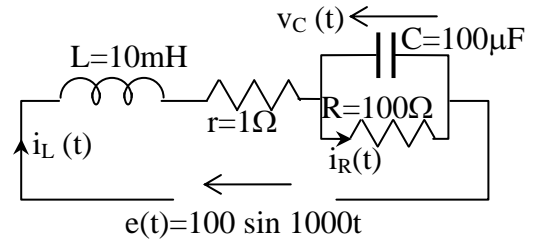




Level 2 Semester 1 Examination - January 2009

1. (a) $Z = j\omega L + r + \frac{R \times \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = j\omega L + r + \frac{R}{1 + j\omega CR}$ [1 mark]



(b) $\omega = 1000 \text{ rad/s}$

$L\omega = 0.01 \times 1000 = 10\Omega$, $1/C\omega = 1/0.0001 \times 1000 = 10\Omega$

$Z = j10 + 1 + \frac{100}{1 + j10} = (1.9901 + j0.0990) = 1.9926 \angle 2.85^\circ \Omega$

Working with peak values instead of rms values,

$I_{Lm} = 100/1.9926 \angle 2.85^\circ = 50.186 \angle -2.85^\circ \text{ A} = 50.186 \angle -0.0497 \text{ A}$

$i_L(t) = \underline{50.186 \sin(1000t - 2.85^\circ)} \text{ A}$ [1 mark]

$V_{Cm} = 100 - (1 + j10) \times 50.186 \angle -2.85^\circ = 100 - 10.0499 \angle 84.29^\circ \times 50.186 \angle -2.85^\circ$
 $= 100 - 504.36 \angle 81.44^\circ = 100 - (75.08 + j498.74) = 24.92 - j498.74$
 $= 499.36 \angle -87.14^\circ \text{ V} = 499.36 \angle -1.5209 \text{ V}$

$v_C(t) = \underline{499.36 \sin(1000t - 87.14^\circ)} \text{ A}$ [1 mark]

(c) Energy stored = $\frac{1}{2}Li^2 + \frac{1}{2}Cv^2$

$W = 0.5 \times 0.01 \times 50.186^2 \times \sin^2(1000t - 2.85^\circ) + 0.5 \times 0.0001 \times 499.36^2 \times \sin^2(1000t - 87.14^\circ)$
 $= 12.593 \sin^2(1000t - 2.85^\circ) + 12.468 \sin^2(1000t - 87.14^\circ)$ [1 mark]

For maximum energy stored, $dW/dt = 0$

$dW/dt = 12593 \times \sin(2000t - 5.70^\circ) + 12468 \times \sin(2000t - 174.28^\circ) = 0$

i.e. $12531 \sin 2000t - 1251 \cos 2000t - 12406 \sin 2000t - 1242.6 \cos 2000t = 0$

$125 \sin 2000t = 2494 \cos 2000t$

$\tan 2000t = 19.952$, $2000t = 1.5207 \text{ rad or } 4.6623 \text{ rad}$ giving $t = 0.7604 \text{ ms OR } t = 2.3312 \text{ ms}$

\therefore maximum energy stored = $12.593 \times \sin^2(0.7604 - 0.0497) + 12.468 \times \sin^2(0.7604 - 1.5209)$
 $= 5.359 + 5.924 = 11.28 \text{ J}$

OR maximum energy stored = $12.593 \times \sin^2(2.3312 - 0.0497) + 12.468 \times \sin^2(2.3312 - 1.5209)$
 $= 7.234 + 6.544 = \underline{13.78 \text{ J}}$ [1 mark]


(d) Power loss in the circuit = $(50.186/\sqrt{2})^2 \times 1 + (499.36/\sqrt{2})^2 / 100 = 2506 \text{ W}$

Energy loss per cycle = $5012 \times 2\pi / 1000 = \underline{15.75 \text{ J}}$ [1 mark]

Q factor of circuit = $2\pi \times 13.78 / 15.75 = \underline{5.50}$ [1 mark]



(e)

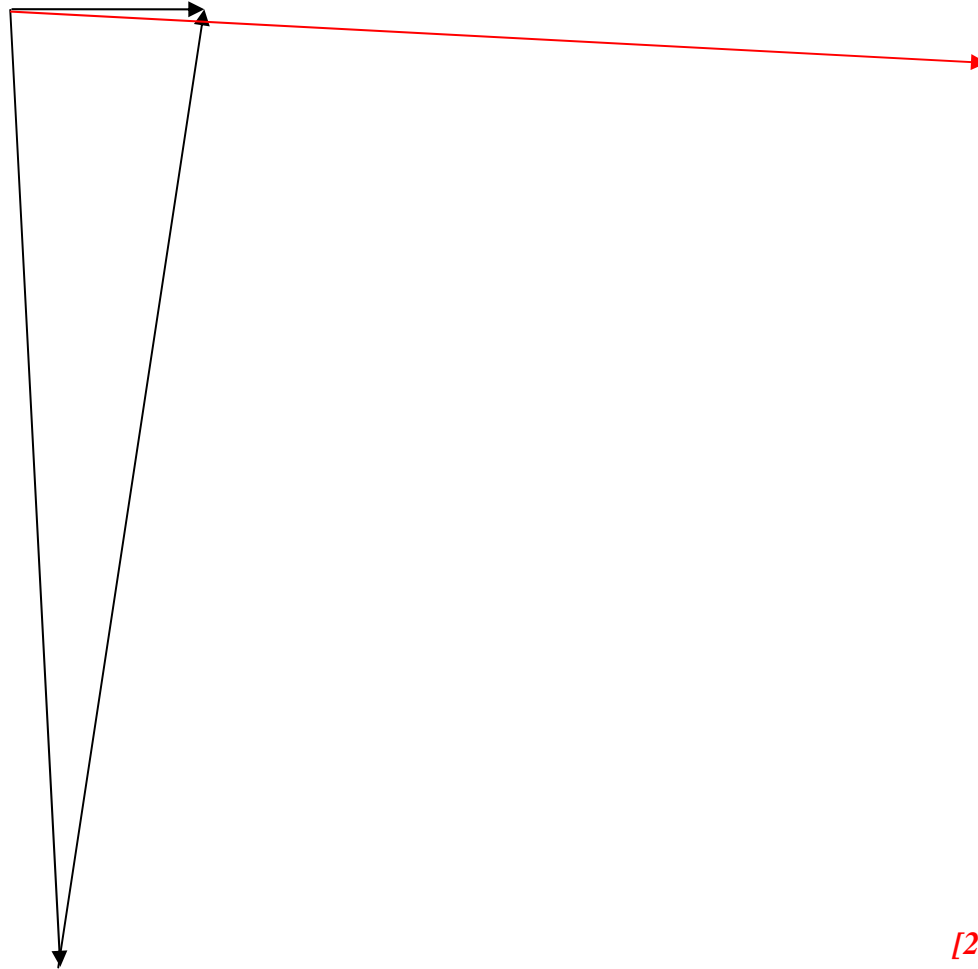

[2 mark]

(f) Resonance frequency (when power factor is unity)

$$j\omega L + r + \frac{R}{1 + j\omega CR} = j\omega L + r + \frac{R(1 - j\omega CR)}{1 + \omega^2 C^2 R^2}$$

i.e. $\omega L = \frac{\omega CR^2}{1 + \omega^2 C^2 R^2}$ or $L + \omega^2 LC^2 R^2 = CR^2$, giving $\omega = \sqrt{\frac{CR^2 - L}{LC^2 R^2}}$ OR

$$\omega = \sqrt{\frac{10^{-4} \times 100^2 - 0.01}{0.01 \times 10^{-8} \times 100^2}} = \sqrt{\frac{0.99}{10^{-6}}} = \underline{\underline{995.0 \text{ rad/s}}} \text{ (or 158.4 Hz)}$$

[1 mark]



2. (a) Reluctance = $l/\mu A$

outer limb reluctance $S_o = l_o / \mu_o \mu_r A$

middle limb reluctance $S_m = l_m / \mu_o \mu_r A$

effective reluctance seen by coil = $S_o + S_m // S_o$

$$= S_o + \frac{S_m S_o}{S_m + S_o} = \frac{l_o}{\mu_o \mu_r A} + \frac{l_o l_m}{\mu_o \mu_r A (l_o + l_m)}$$

$$= \frac{0.2}{4\pi \times 10^{-7} \times 1000 \times 4 \times 10^{-4}} + \frac{0.2 \times 0.06}{4\pi \times 10^{-7} \times 1000 \times 4 \times 10^{-4} \times (0.2 + 0.06)}$$

$$= 397,887 + 91,820 = \underline{489,707 \text{ H}^{-1}}$$

[3 marks]

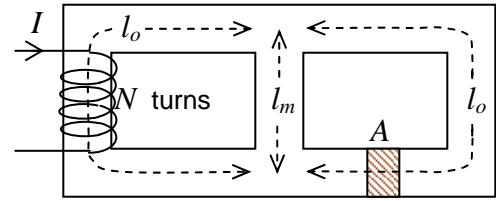


Figure Q2a

(b) at 50 Hz, $P_e = P_h = 50 \text{ W}$, with $t = 0.5 \text{ mm}$

When operated at 60 Hz,

$P_h \propto f$,

Hysteresis loss $P_h = 50 \times 60 / 50 = \underline{60 \text{ W}}$

$P_e + P_h = 100$

Eddy current loss $P_e = \underline{40 \text{ W}}$

[1 mark]

$$P_e \propto f^2 t^2, \quad t \propto \frac{\sqrt{P_e}}{f},$$

$$\text{Required thickness } t = 0.5 \times \frac{50}{60} \times \sqrt{\frac{40}{50}} = \underline{0.373 \text{ mm}}$$

[1 mark]

(c) $r_1 = 2 \text{ mm}$ and $r_2 = 3 \text{ mm}$, $l = 25 \text{ mm}$, $\epsilon_r = 4.5$, $W = 1 \text{ mJ}$

$$\text{Capacitance } C = \frac{2\pi \epsilon l}{\ln[r_2/r_1]} = \frac{2 \times \pi \times 4.5 \times 8.854 \times 10^{-12} \times 0.025}{\ln(3/2)} = 15.435 \text{ pF}$$

$$\text{Energy stored } W = 1 \times 10^{-3} = \frac{1}{2} \times 15.435 \times 10^{-12} \times V^2$$

$$\text{Required voltage } V = \sqrt{129,575,639} = \underline{11,383 \text{ V}}$$

[2 marks]

(d) Voltage in absence of load $V_{oc} = 230 \text{ V}$

Short circuit current $I_{sc} = 10 \text{ kA}$

$$\therefore \text{ internal impedance} = 230 / 10 \times 10^3 = 0.023 \Omega$$

$$\text{Theoretical maximum power deliverable} = V^2 / 4r = 230^2 / 4 \times 0.023 = 575 \text{ kW}$$

[2 marks]

Internal impedance is purely resistive is assumed.

The two reasons that make this value unachievable are

(i) Source impedance is not purely resistive

(ii) A load voltage of half value is not acceptable.

[1 mark]



3. (a) The two port admittance matrix is given by

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

$$z_{11}|_{V_2=0} = 1+j3+(-j50)/(1+j3) = 1+j3 + \frac{-j50 \times (1+j3)}{-j50+(1+j3)} = 1+j3 + \frac{150-j50}{1-j47} = 1+j3 + \frac{158.11 \angle -18.43^\circ}{47.01 \angle -88.78^\circ}$$

$$= 1+j3+3.363 \angle 70.35^\circ = 1+j3+1.1309+j3.1672 = 2.1309+j6.1672 = 6.525 \angle 70.94^\circ$$

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{1}{z_{11}} = 0.1532 \angle -70.94^\circ \text{ S (or } 0.0500 - j 0.1449)$$

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = \frac{I_2}{V_1} \times \frac{I_1}{I_1} \bigg|_{V_2=0} = -0.153 \angle -70.94^\circ \times \frac{-j50}{1-j47} = -0.153 \angle -70.94^\circ \times \frac{50 \angle -90^\circ}{47.01 \angle -88.78^\circ}$$

$$y_{21} = \frac{7.65 \angle 19.06^\circ}{47.01 \angle -88.78^\circ} = 0.163 \angle 107.84^\circ \text{ S or } (-0.0499 + j 0.1549)$$

$$y_{12} = y_{21} = 0.163 \angle 107.84^\circ \text{ S}$$

$$y_{22} = y_{11} = 0.153 \angle -70.940^\circ \text{ S}$$

The two port admittance matrix is

$$[Y] = \begin{bmatrix} 0.153 \angle -70.9^\circ & 0.163 \angle 107.8^\circ \\ 0.163 \angle 107.8^\circ & 0.153 \angle -70.9^\circ \end{bmatrix}$$

[2 marks]

(b) Characteristic impedance Z_0 is given when

$$V_1/I_1 = Z_0 = V_2/(-I_2)$$

i.e. using two port admittance parameters,

$$I_1 = y_{11}Z_0I_1 - y_{12}Z_0I_2$$

$$I_2 = y_{21}Z_0I_1 - y_{22}Z_0I_2$$

$$\therefore \frac{I_2}{I_1} = \frac{y_{11}Z_0 - 1}{y_{12}Z_0} = \frac{y_{21}Z_0}{y_{22}Z_0 + 1}$$

Since $y_{22} = y_{11}$, and $y_{12} = y_{21}$

$$y_{11}^2 Z_0^2 - 1 = y_{12}^2 Z_0^2$$

$$Z_0 = \sqrt{\frac{1}{y_{11}^2 - y_{12}^2}} = \sqrt{\frac{1}{0.1532^2 \angle -70.94 \times 2^\circ - 0.1630^2 \angle 107.84 \times 2^\circ}}$$

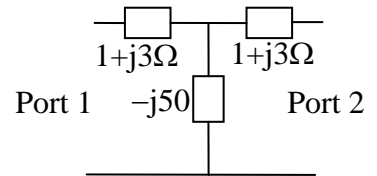


Figure Q3a



$$= \sqrt{\frac{1}{0.0235 \angle -141.87^\circ - 0.0266 \angle 215.69^\circ}} = \sqrt{\frac{1}{0.00310 - j0.0010}} = \sqrt{\frac{1}{0.00326 \angle 17.88^\circ}}$$

$$Z_0 = \underline{17.51 \angle -8.9^\circ \Omega}$$

[2 marks]

Alternate Solution

$$Z_0 = 1 + j3 + \frac{(-j50)(1 + j3 + Z_0)}{-j50 + 1 + j3 + Z_0}$$

$$Z_0^2 + (1 + j3)Z_0 - j50Z_0 = (1 + j3)Z_0 + (1 + j3)^2 - j50(1 + j3) - j50Z_0$$

$$Z_0^2 = 292 - j94$$


$$Z_0 = 17.51 \angle -8.92^\circ \Omega$$

(c) Kirchoff's law equations

$$i_1 = i_2 + i_3$$

$$100 = -10 i_1 + 10 i_1 + 50 i_2 \rightarrow 100 = 50 i_2$$
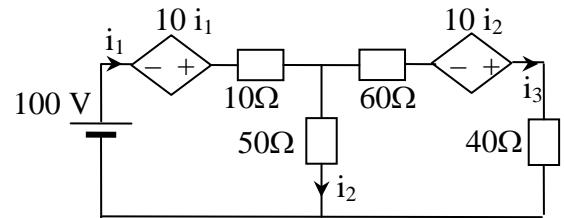
$$0 = 60 i_3 - 10 i_2 + 40 i_3 - 50 i_2 \rightarrow 6 i_2 = 10 i_3 \quad [2 \text{ marks}]$$



(d) $i_2 = 2 \text{ A}$

$$i_3 = 1.2 \text{ A}$$

$$i_1 = i_2 + i_3 = 3.2 \text{ A}$$

[2 marks]

(e) $Z_s = 1 + j3 \Omega$, $Z_{load} = 40 + j30 \Omega$, $I_{load} = 10.5 \angle 30^\circ \text{ A}$

For new current $I_{load} = 10 \angle 30^\circ \text{ A}$, load impedance = $Z_{load} + \Delta Z_{load}$

Using compensation theorem,

$$\Delta I = 10.5 \angle 30^\circ - 10 \angle 30^\circ = -0.5 \angle 30^\circ \text{ A}$$



$$I \cdot \Delta Z = - [Z_s + (Z_{load} + \Delta Z_{load})] \Delta I$$

i.e. $10.5 \angle 30^\circ \Delta Z_{load} = - [1 + j3 + (40 + j30 + \Delta Z_{load})] (-0.5 \angle 30^\circ)$

i.e. $21 \Delta Z_{load} = [41 + j33 + \Delta Z_{load}]$

$$20 \Delta Z_{load} = 41 + j33 \rightarrow \Delta Z_{load} = 2.05 + j1.65$$
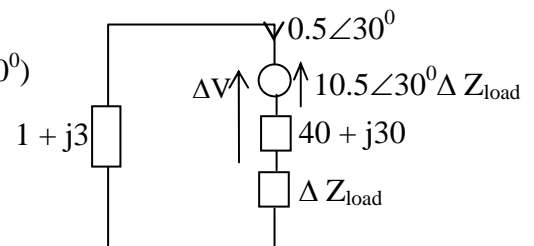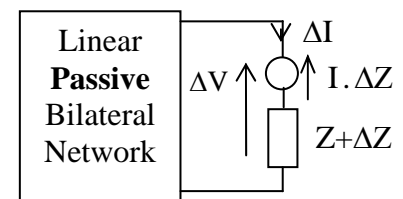
$$Z_{load} = 42.05 + j31.65 = \underline{52.63 \angle -36.97^\circ} \quad [2 \text{ marks}]$$





4. (a) $E = 100V$, $\omega = 250 \text{ rad/s}$,

$$R_1 = R_2 = 10 \Omega, Y_{R1} = 0.1, E/R_1 = 10A$$

$$L = 10\text{mH}, X_L = 250 \times 0.01 = 2.5 \Omega,$$

$$Y_{LR2} = 1/(10 + j2.5) = 0.09411 - j0.02353$$

$$C = 100\mu\text{F}, Y_C = j250 \times 10^{-4} = j0.025 \text{ S}$$

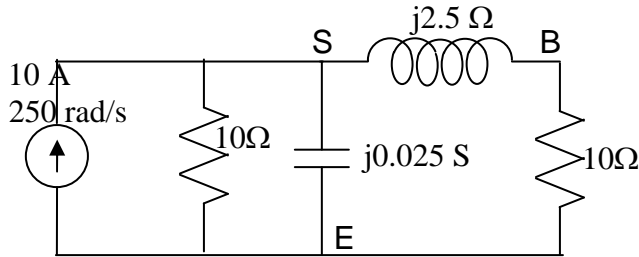


Figure Q4

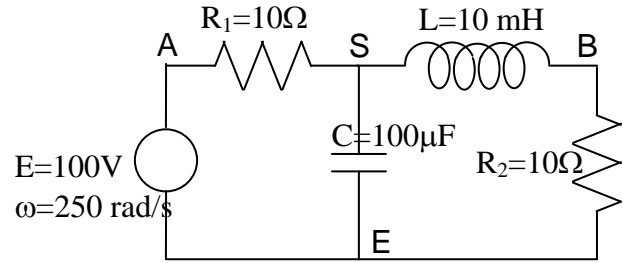


Figure Q4

$$\frac{1}{10 + j2.5} = 0.0941 - j0.02353$$

[1 mark]

(b) Selecting node E as reference, and S as node 1 and combining L and R_2 into 1 branch

$$[Y_N] = [0.1 + j0.025 + 0.09411 - j0.02353] = [0.19411 + j0.00147] = 0.19412 \angle 0.434^\circ \quad [1 \text{ mark}]$$

$$[I_{gN}] = [10] \quad [1 \text{ mark}]$$

(c) using nodal analysis, $[I_{gN}] = [Y_N] [V_N]$

$$\text{i.e. } V_S = [0.19412 \angle 0.434^\circ]^{-1} \times 10 = 51.51 \angle -0.434^\circ$$

$$\therefore I_{AS} = [100 - 51.51 \angle -0.434^\circ] / 10 = [10 - 5.151 + j0.039] = 4.849 + j0.039 = 4.849 \angle 0.46^\circ \text{ A} \quad [1 \text{ mark}]$$

$$I_{SE} = 51.51 \angle -0.434^\circ \times j0.025 = 1.288 \angle 89.57^\circ \text{ A} \quad [1 \text{ mark}]$$

$$I_{SBE} = 51.51 \angle -0.434^\circ \times (0.09411 - j0.02353) = 51.51 \angle -0.434^\circ \times 0.0970 \angle -14.04^\circ \\ = 4.996 \angle -14.47^\circ \text{ A} \quad [1 \text{ mark}]$$

$$(d) Y_{AE} = \frac{0.1 \times j0.025}{0.1 + j0.025 - j0.4} = \frac{j0.0025}{0.1 - j0.375}$$

$$Z_{AE} = -150 - j40 \Omega = 155.24 \angle -165.07^\circ \Omega \quad [1 \text{ mark}]$$

$$Y_{AB} = \frac{0.1 \times (-j0.4)}{0.1 + j0.025 - j0.4} = \frac{-j0.04}{0.1 - j0.375}$$


$$Z_{AB} = 9.375 + j2.5 \Omega = 9.703 \angle 14.93^\circ \Omega \quad [1 \text{ mark}]$$

(e) $I_{AE} = 100 / 155.24 \angle -165.07^\circ = 0.644 \angle 165.07^\circ \text{ A}$

$$I_{AB} = (100 - 49.96 \angle -14.47^\circ) / 9.703 \angle 14.93^\circ = (51.62 + j12.48) / 9.703 \angle 14.93^\circ \\ = 53.11 \angle 13.59^\circ / 9.703 \angle 14.93^\circ = 5.474 \angle -1.34^\circ \text{ A} \quad [1 \text{ mark}]$$

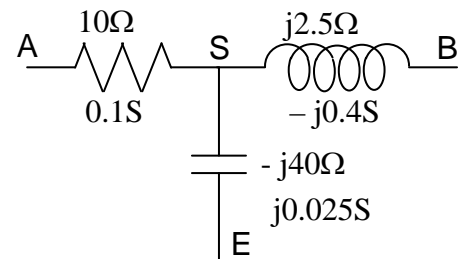(f) Thus $I_{AS} = 5.474 \angle -1.34^\circ \text{ A} + 0.644 \angle 165.07^\circ \text{ A} = 5.473 - j0.128 - 0.6223 + j0.1659$

$$I_{AS} = 4.850 + j0.038 = 4.850 \angle 0.45^\circ \text{ A} \quad [1 \text{ mark}]$$





5. Load (i) = star connected, resistive, 40 Ω each

Load (ii) = 2 kW, 0.7 lag, 3 phase motor

(a) Line current of load (i) = $400/(\sqrt{3} \times 80) = 2.886 \angle 0^\circ \text{ A}$

Line current of load (ii) = $2000/(\sqrt{3} \times 400 \times 0.7) = 4.124 \angle -45.57^\circ \text{ A}$

∴ total line current = $2.886 + 4.124 \angle -45.57^\circ = 2.886 + 2.887 - j2.945 = 5.873 - j2.945$
 $= \underline{6.48 \angle -27.02^\circ \text{ A}}$ *[2 mark]*

(b) Supply power factor = $\cos 27.32 = \underline{0.891 \text{ lag}}$ *[1 mark]*

(c) Total active power of load = $\sqrt{3} \times 400 \times 6.48 \times \cos(27.02^\circ) = 4000 \text{ W}$

Total reactive power of load = $\sqrt{3} \times 400 \times 6.48 \times \sin(27.02^\circ) = 2040 \text{ var}$

Total reactive power supplied by capacitor = 2040 var

∴ $3 \times 400^2 \times C \times 100\pi = 2040$

Each capacitor C of delta = $\underline{13.53 \mu\text{F}}$ *[2 mark]*

(d) $I_{A0} = 1.0 \angle 90^\circ \text{ A}$, $I_{A1} = 10.0 \angle 0^\circ \text{ A}$ and $I_{A2} = 3.0 \angle -90^\circ \text{ A}$

Since supply is balanced, only positive sequence voltage is present

$V_{A0} = 0 \text{ V}$, $V_{A1} = 230 \angle 0^\circ \text{ V}$ and $V_{A2} = 0 \text{ V}$

Power associated with zero sequence = $\underline{0 \text{ W}}$

Power associated with positive sequence = $\sqrt{3} \times 400 \times 10.0 \times \cos 0^\circ = \underline{6928 \text{ W}}$

Power associated with negative sequence = $\underline{0 \text{ W}}$ *[2 mark]*

(e) Phase currents are given by

$$\begin{bmatrix} I_A \\ I_B \\ I_C \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha^2 & \alpha \\ 1 & \alpha & \alpha^2 \end{bmatrix} \begin{bmatrix} 1 \angle 90^\circ \\ 10 \angle 0^\circ \\ 3 \angle -90^\circ \end{bmatrix}$$

$I_A = j1 + 10 - j3 = 10 - j2 = \underline{10.20 \angle -11.31^\circ \text{ A}}$

$I_B = j1 + 10 \angle 240^\circ + 3 \angle 30^\circ = j1 - 5 - j 8.660 + 2.598 + j1.5 = -2.402 - j 6.160$
 $= \underline{6.612 \angle -111.3^\circ \text{ A}}$

$I_C = j1 + 10 \angle 120^\circ + 3 \angle 150^\circ = j1 - 5 + j 8.660 - 2.598 + j1.5 = -7.598 + j 11.160$
 $= \underline{13.5 \angle 124.2^\circ \text{ A}}$ *[3 marks]*



6. $5 \cos 6\omega_0 t$ in the region $-T_1$ to T_1

$$5 \cos 6\omega_0 T_1 = 0 \text{ gives } 6\omega_0 T_1 = \pi/2$$

$$\text{i.e. } 6 \times 2\pi/T \times T_1 = \pi/2, \text{ or } 24 T_1 = T$$

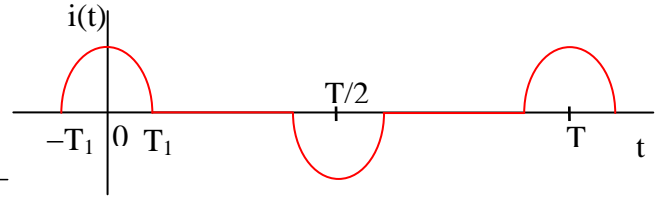


Figure Q6(a) $\omega_0 T = 2\pi$

$$(a) \text{ rms current} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt} = \sqrt{\frac{4}{T} \int_0^{T_1} i^2(t) dt}$$

$$\begin{aligned} \text{i.e. } I_{\text{rms}} &= \sqrt{\frac{4}{T} \int_0^{T_1} 25 \cos^2 6\omega_0 t dt} = \sqrt{\frac{4}{T} \int_0^{T_1} 12.5(1 + \cos 12\omega_0 t) dt} = \sqrt{\frac{4}{T} \left[12.5t + \frac{\sin 12\omega_0 t}{12\omega_0} \right]_0^{T/24}} \\ &= \sqrt{\frac{4}{T} \left[12.5 \left(\frac{T}{24} + \frac{\sin \frac{\omega_0 T}{2}}{12\omega_0} \right) \right]} = \sqrt{50 \left(\frac{1}{24} + \frac{\sin \pi}{24\pi} \right)} = \underline{\underline{1.4433 \text{ A}}} \end{aligned} \quad [2 \text{ mark}]$$

(b) waveform is even-symmetric, half-wave symmetric and mean value is zero.

$$\therefore B_n = 0 \text{ for all } n, A_n = 0 \text{ for even harmonics, } A_0 = 0$$

$$\text{and } A_n = \frac{4 \times 2}{T} \int_0^{T/24} 5 \cos 6\omega_0 t \cdot \cos n\omega_0 t \cdot dt = \frac{20}{T} \int_0^{T/24} [\cos(6-n)\omega_0 t + \cos(6+n)\omega_0 t] \cdot dt$$

$$A_n = \frac{20}{T} \left[\frac{\sin(6-n)\omega_0 t}{(6-n)\omega_0} + \frac{\sin(6+n)\omega_0 t}{(6+n)\omega_0} \right]_0^{T/24} = \frac{20}{\omega_0 T} \left[\frac{\sin \frac{(6-n)\omega_0 T}{24}}{(6-n)} + \frac{\sin \frac{(6+n)\omega_0 T}{24}}{(6+n)} \right]$$

$$= \frac{10}{\pi} \left[\frac{\sin \frac{(6-n)\pi}{12}}{(6-n)} + \frac{\sin \frac{(6+n)\pi}{12}}{(6+n)} \right]$$

$$A_1 = 1.0542$$

$$A_3 = 1.0003$$

$$A_5 = 0.8987$$

[4 marks]

$$\text{Thus } i(t) = 1.0542 \cos \omega_0 t + 1.0003 \cos 3\omega_0 t + 0.8987 \cos 5\omega_0 t$$

$$(c) v(t) = 100 \cos(\omega_0 t + \pi/12) - 1 \times (1.0542 \cos \omega_0 t + 1.0003 \cos 3\omega_0 t + 0.8987 \cos 5\omega_0 t + \dots)$$

$$v(t) = (96.5926 - 1.0542) \cos \omega_0 t - 25.8819 \sin \omega_0 t - 1.0003 \cos 3\omega_0 t - 0.8987 \cos 5\omega_0 t + \dots$$

$$= 98.98 \cos(\omega_0 t - 15.16^\circ) - 1.0003 \cos 3\omega_0 t - 0.8987 \cos 5\omega_0 t + \dots$$

$$(d) \text{ power supplied} = 98.98 \times 1.0542 \times \cos 15.16^\circ$$

$$= \underline{\underline{100.7 \text{ W}}}$$

[2 marks]

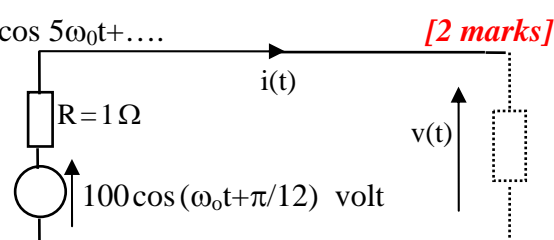


Figure Q6(b)



7. (a) Determination of Laplace transform of the causal sinusoidal waveform

[2 marks]

(b) $E_m = 100 \text{ V}$, $f = 50 \text{ Hz} \rightarrow \omega = 100\pi \text{ rad/s}$,

$R = 100 \Omega$, $C = 40 \mu\text{F}$, $L = 1.8 \text{ H}$

With switch S open,

$$V_C = \frac{1}{100 + \frac{1}{j100\pi \times 40 \times 10^{-6}}} E$$

$$= \frac{1}{100 \times j100\pi \times 40 \times 10^{-6} + 1} E$$

$$= \frac{1}{1 + j0.4\pi} E = 0.6227 \angle 51.49^\circ \times E \rightarrow \text{gives } v_c(t) = 62.27 \sin(100\pi t + 51.49^\circ)$$


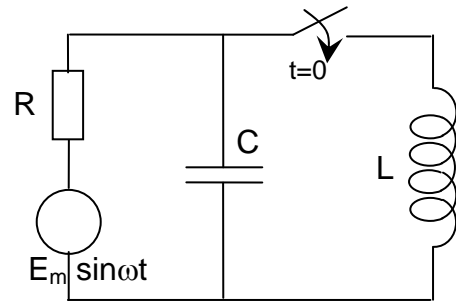


Figure Q7

At $t = 0$, initial value of voltage across $C = V_c(0) = 62.27 \sin 51.49^\circ = 48.72 \text{ V}$

[2 marks]

(c)

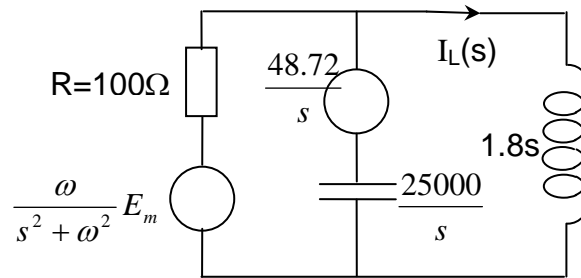

[2 marks]

(d)

$$I_L(s) = \frac{\omega}{s^2 + \omega^2} \cdot E_m \cdot \frac{1}{100 + \frac{1.8s \times 25000/s}{1.8s + 25000/s}} \times \frac{25000/s}{1.8s + 25000/s} + \frac{48.72}{s} \times \frac{1}{\frac{25000}{s} + \frac{100 \times 1.8s}{100 + 1.8s}} \times \frac{100}{100 + 1.8s}$$

$$= E_m \cdot \frac{\omega}{s^2 + \omega^2} \times \frac{25000/s}{180s + \frac{2500000}{s} + 1.8 \times 25000} + \frac{48.72}{s} \times \frac{100s}{25000 \times 100 + 25000 \times 1.8s + 180s^2}$$

$$= E_m \cdot \frac{\omega}{s^2 + \omega^2} \times \frac{2500}{18s^2 + 4500s + 250000} + \frac{487.2}{18s^2 + 4500s + 250000}$$

$$= \frac{2500}{18s^2 + 4500s + 250000} \times \left[100 \frac{100\pi}{s^2 + (100\pi)^2} + 487.2 \right]$$

$$= \frac{138.889}{(s + 244.315)(s + 5.685)} \times \left[\frac{31415.9}{s^2 + (314.159)^2} + 487.2 \right]$$



(e)