
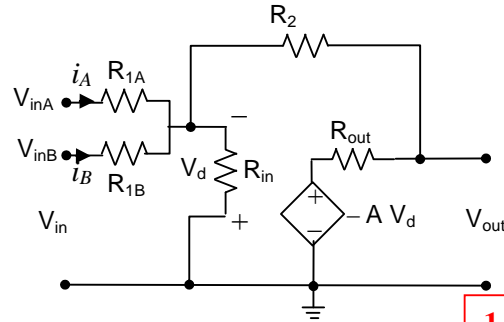


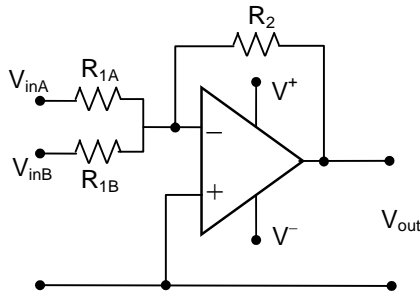

EE 2010 - THEORY OF ELECTRICITY – Short Answers

Level 2 Semester 1 Examination - January 2010

1. (a)



1 mark

$$i = i_A + i_B = \frac{V_{inA} - V_d}{R_{1A}} + \frac{V_{inB} - V_d}{R_{1B}} = \frac{V_d}{R_{in}} + \frac{V_d - V_{out}}{R_2}$$

$$\frac{V_d - V_{out}}{R_2} = \frac{V_{out} + AV_d}{R_{out}}$$

1 mark

for an ideal Op Amp, $R_{out} = 0$, and $R_{in} = \infty$, $A \rightarrow \infty$,

$$V_{out} = -A V_d$$


$$V_d = -V_{out}/A \rightarrow 0$$

$$\frac{V_{inA} - 0}{R_{1A}} + \frac{V_{inB} - 0}{R_{1B}} = 0 + \frac{0 - V_{out}}{R_2}$$

giving $V_{out} = -R_2 \left(\frac{V_{inA}}{R_{1A}} + \frac{V_{inB}}{R_{1B}} \right)$

1 mark

(b)

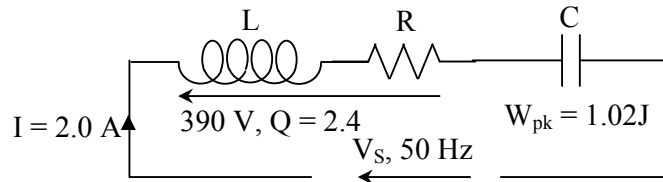

For the choke,

$$|R + j\omega L| = 390/2 = 195 \Omega, \quad \omega L/R = 2.4 \rightarrow \sqrt{(R^2 + 2.4^2 R^2)} = 195 \rightarrow R = 75 \Omega$$

1 mark

$$\omega L = 2.4 R = 180 \Omega \rightarrow L = 180/100\pi = 0.573 = 573 \text{ mH}$$

1 mark

$$\text{Peak energy stored in capacitor} = \frac{1}{2} C V_{Cm}^2 = C V_{Crms}^2 = C \times \left(I \times \frac{1}{C\omega} \right)^2 = \frac{2^2}{C \times (100\pi)^2} = 1.02$$


Giving $C = 39.73 \mu\text{F}$ and $1/C\omega = 80.1 \Omega$.

1 mark

Supply voltage $V_s = 2.0 \times (75 + j 180 - j80.1)$

$$= 2.0 \times (75 + j 99.9) = 249.84 \angle 53.1^\circ \text{ V}$$

1 mark

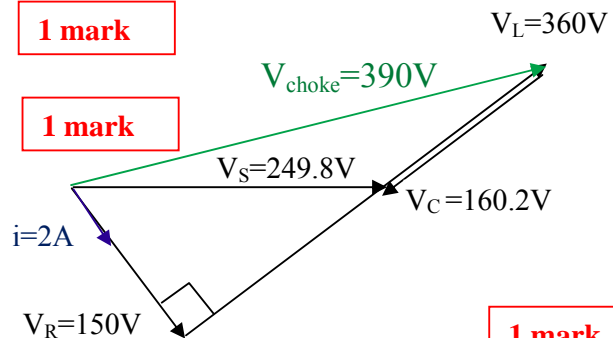

1 mark

**EE 2010 - THEORY OF ELECTRICITY – Short Answers**

Resonance frequency = $\omega_0 = 1/\sqrt{LC} = 1/\sqrt{(0.573 \times 39.73 \times 10^{-6})} = 209.59 \text{ rad/s} \rightarrow 33.36 \text{ Hz}$

Current at resonance = $249.84/75 = 3.331 \text{ A}$

1 mark

At half-power points, current $I_{1/2} = 3.331/\sqrt{2} = 2.356 \text{ A}$

And the half-power frequencies are obtained from

$$2.356 = \left| \frac{249.84}{75 + j\left(\omega \times 0.573 - \frac{1}{\omega \times 39.73 \times 10^{-6}}\right)} \right| \rightarrow \omega = 153.8, 284.0 \text{ rad/s}$$

$$f = 24.5, 45.2 \text{ Hz}$$

2. (a) For 50 Hz transformer, lamination thickness $t = 0.5 \text{ mm}$

Hysteresis loss $\propto B_m^{1.6} f$

Eddy current loss $\propto B_m^2 f^2 t^2$

If the alternating flux density peak value = B_m and the total core loss P are to be the same for a given size of transformer,

Hysteresis loss $P_h = K_h f$

Eddy current loss $P_e = K_e f^2 t^2$

at 50 Hz, $P_h = P_e \rightarrow 50 K_h = 50^2 \times 0.5^2 K_e \rightarrow K_h = 12.5 K_e$

total core loss = $P = P_h + P_e = K_h f + K_e f^2 t^2$ at both frequencies 50 Hz and 60 Hz.

i.e. $P = 50 K_h + 50^2 \times 0.5^2 K_e = 60 K_h + 60^2 \times t^2 K_e$

or $50 \times 12.5 K_e + 50^2 \times 0.5^2 K_e = 60 \times 12.5 K_e + 60^2 \times t^2 K_e$

i.e. $(625 + 625) K_e = (750 + 3600 t^2) K_e$

$t^2 = 500/3600 \rightarrow t = 0.373 \text{ mm}$ thick laminations are required at 60 Hz.

2 marks


- (b) voltages at A, B and C are $100 \angle 0^\circ \text{ V}$,

$70.7 \angle 45^\circ \text{ V}$ and 0 V respectively.

Thus using Millmann's theorem,

$$V_s = \frac{\sum Y \times V}{\sum Y}$$
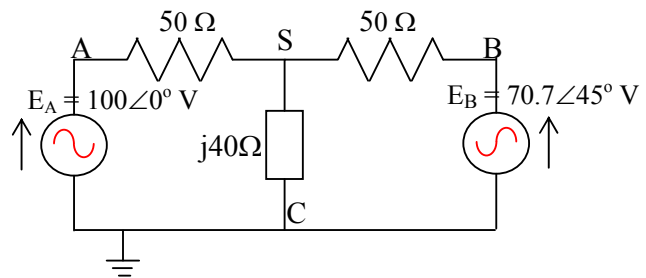
$$V_s = \frac{\frac{1}{50} \times 100 \angle 0^\circ + \frac{1}{50} \times 70.7 \angle 45^\circ + 0}{\frac{1}{50} + \frac{1}{50} + \frac{1}{j40}}$$



i.e. $V_s = \frac{2 + (1 + j1) + 0}{0.02 + 0.02 - j0.025} = \frac{3 + j1}{0.04 - j0.025} = \frac{3.162 \angle 18.43^\circ}{0.047 \angle -32.01^\circ} = 67.04 \angle 50.44^\circ$

3 marks

- (c) diameter = 50 mm, depth = 2m, soil resistivity 100 Ωm .

EE 2010 - THEORY OF ELECTRICITY – Short Answers

Consider an elemental cylinder of thickness dx .

The resistance dR of this can be calculated as follows.

$$\begin{aligned} \text{using } R &= \frac{\rho l}{A}, \quad dR = \frac{\rho \cdot dx}{2\pi x^2 + 2\pi x \cdot l} \\ &= \frac{\rho \cdot dx}{2\pi x(x+l)} = \frac{\rho}{2\pi l} \left[\frac{1}{x} - \frac{1}{x+l} \right] \cdot dx \\ \int_0^R dR &= \int_r^x \frac{\rho}{2\pi l} \left[\frac{1}{x} - \frac{1}{x+l} \right] dx \Rightarrow \\ R &= \frac{\rho}{2\pi l} \left[\ln\left(\frac{x}{r}\right) - \ln\left(\frac{x+l}{r+l}\right) \right] \end{aligned}$$

as x tends to infinity, that is as a large mass of the earth is taken into consideration, the limiting value of the electrode resistance would be

$$R = \frac{\rho}{2\pi l} \ln\left[\frac{r+l}{r}\right] = \frac{100}{2\pi \cdot 2} \ln\left[\frac{0.025+2}{0.025}\right] = 34.97 \Omega$$

3 marks

(d) Norton's equivalent impedance = $10+2 = 12 \Omega$



Norton's equivalent current source is determined as follows

$$10 = I_S + I_{SC}$$

$$10 I_S = 4I_S + 2I_{SC} \rightarrow I_{SC} = 3I_S$$


$$I_S = 2.5 \text{ A}, I_{SC} = 3 \times 2.5 \text{ A} = 7.5 \text{ A}$$

The Norton's equivalent circuit is

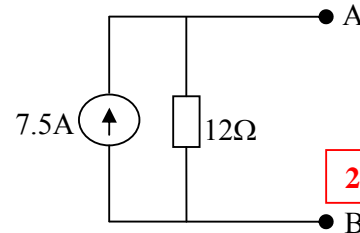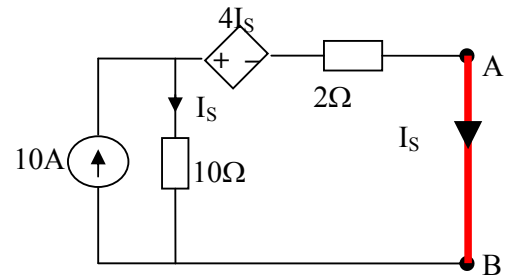


2 marks

3. (a)

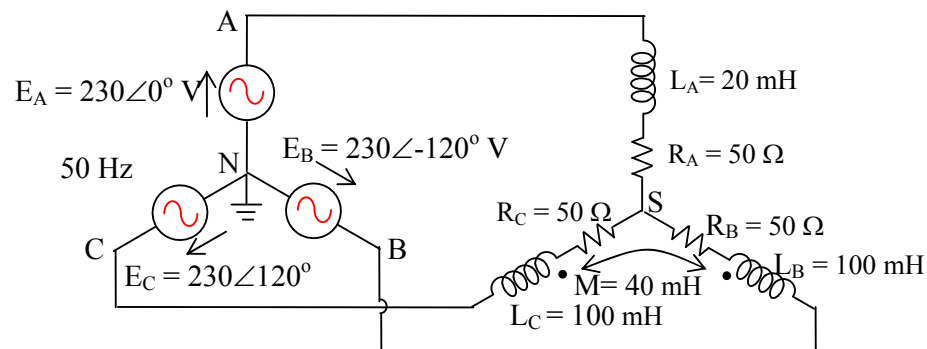

**EE 2010 - THEORY OF ELECTRICITY – Short Answers**

The uncoupled equivalent circuit may be drawn as follows

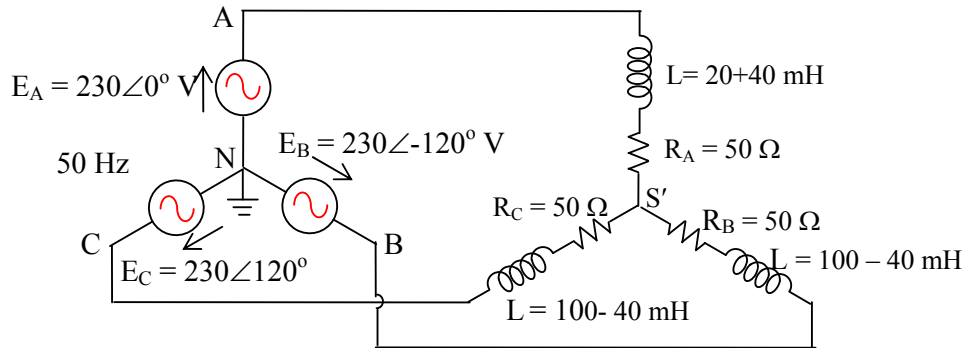**2 marks**

- (b) Note that S is no longer the star-point of the modified network. It is seen that the modified network is perfectly balanced, and hence the current in each phase is given by

$$I_A = 230\angle 0^\circ / (50 + j0.06 \times 100 \times \pi) = 230 / (50 + j18.85) = 4.30\angle -20.7^\circ \text{ A}$$

$$I_B = 4.30\angle -140.7^\circ \text{ A}, I_C = 4.30\angle 99.3^\circ \text{ A}$$

2 marks

- (c) The potential of the new star point S' is 0. The original star point S is located at a point 40 mH above S'.

$$\text{Potential of original star point S} = 0 - j0.04 \times 100 \times \pi \times 4.30\angle -20.7^\circ = 54.0\angle -110.7^\circ \text{ V}$$

2 marks


- (d)

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 40 + j30 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 40 + j30 & 1 \end{bmatrix} \begin{bmatrix} 1 & 40 + j30 \\ 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 40 + j30 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 40 + j30 \\ 1 & 2 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 2 & 120 + j90 \\ 1 & 40 + j30 \end{bmatrix}$$

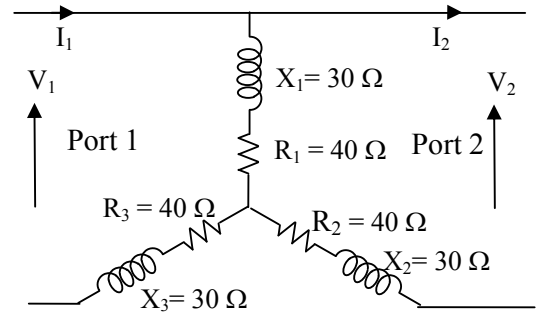**2 marks****Alternate Method**

$$\text{With port 2 on open circuit, } A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{80 + j60}{40 + j30} = 2,$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{1}{40 + j30} = 0.02\angle -36.87^\circ \text{ S}$$

$$\text{With port 2 on short circuit, } D = \left. \frac{I_1}{I_2} \right|_{V_2=0} = \frac{80 + j60}{40 + j30} = 2,$$

$$B = \left. \frac{V_1}{I_1} \times \frac{I_1}{I_2} \right|_{V_2=0} = (Z_1 \parallel Z_2 + Z_3) \times 2 = (20 + j15 + 40 + j30) \times 2 = 120 + j90 = 150\angle 36.87^\circ \Omega$$

giving the same ABCD matrix.

**EE 2010 - THEORY OF ELECTRICITY – Short Answers**

(e) When a resistive load of 100Ω is connected across port 2, $V_2 = 100 I_2$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 2 & 120 + j90 \\ \frac{1}{40 + j30} & 2 \end{bmatrix} \begin{bmatrix} 100 I_2 \\ I_2 \end{bmatrix}$$

$$\frac{V_1}{I_1} = \frac{(200 + 120 + j90)I_2}{\left(\frac{100}{40 + j30} + 2\right)I_2} = \frac{(320 + j90)}{(1.6 - j1.2 + 2)}$$

Thus Impedance seen from port 1 = $\frac{V_1}{I_1} = \frac{332.4 \angle 15.71^\circ}{3.795 \angle -18.43^\circ} = 87.59 \angle 34.14^\circ \Omega$

2 marks**Alternate Method**


$$V_1/I_1 = (40 + j30) + (40 + j30)/(140 + j30)$$

$$= (40 + j30) + \frac{(40 + j30)(140 + j30)}{180 + j60} = (40 + j30) + \frac{50 \angle 36.87^\circ \times 143.18 \angle 12.09^\circ}{189.74 \angle 18.43^\circ}$$

$$= (40 + j30) + \frac{7159 \angle 48.96^\circ}{189.74 \angle 18.43^\circ} = (40 + j30) + 37.73 \angle 30.53^\circ = 40 + j30 + 32.5 + j19.17$$

$$= 72.5 + j49.17 = 87.6 \angle 34.15^\circ \Omega = 72.5 + j49.2 \Omega$$

4. (a)

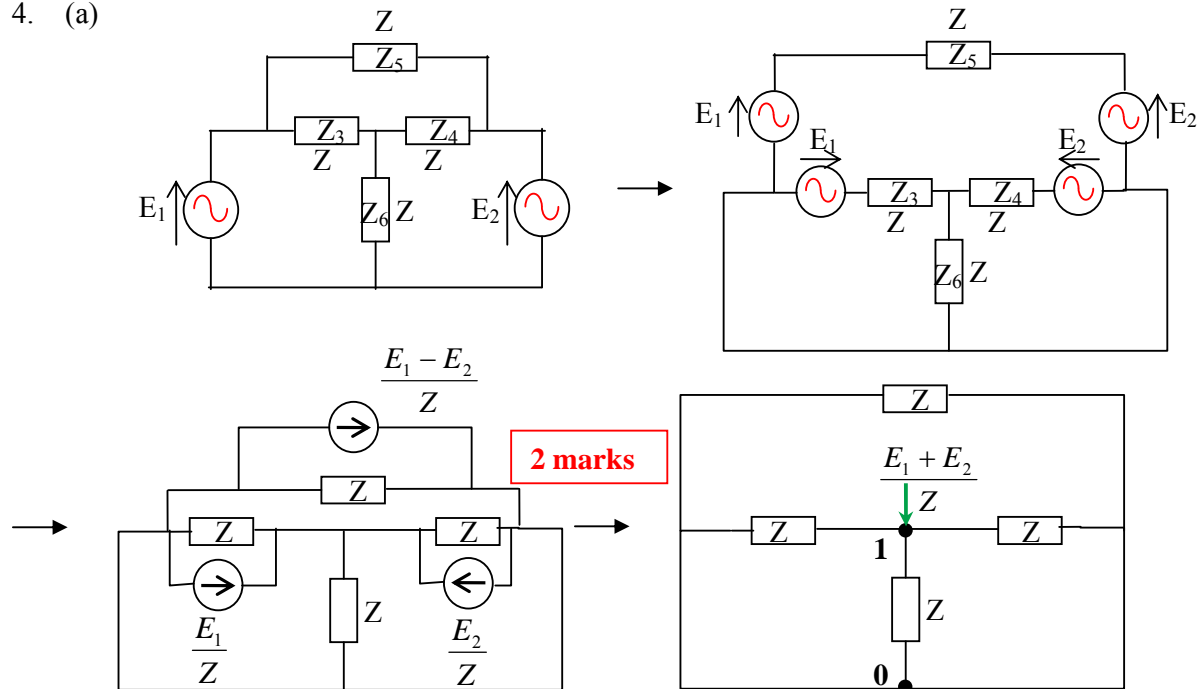

Taking node 0 as reference and eliminating it from equations

$$[Y_b] = \begin{bmatrix} 1/Z & 0 & 0 & 0 \\ 0 & 1/Z & 0 & 0 \\ 0 & 0 & 1/Z & 0 \\ 0 & 0 & 0 & 1/Z \end{bmatrix}, \tilde{I}_{sb} = \begin{bmatrix} E_1/Z \\ E_2/Z \\ (E_1 - E_2)/Z \\ 0 \end{bmatrix}$$

1 mark**1 mark**

**EE 2010 - THEORY OF ELECTRICITY – Short Answers**

The branch-node incidence matrix is given by

$$\begin{bmatrix} -1 \\ -1 \\ 0 \\ 1 \end{bmatrix}$$

1 mark

(c) The nodal admittance matrix is given by

$$[-1 \quad -1 \quad 0 \quad 1] \begin{bmatrix} 1/Z & 0 & 0 & 0 \\ 0 & 1/Z & 0 & 0 \\ 0 & 0 & 1/Z & 0 \\ 0 & 0 & 0 & 1/Z \end{bmatrix} \begin{bmatrix} -1 \\ -1 \\ 0 \\ 1 \end{bmatrix} = [3/Z]$$

2 marks

and the nodal current vector is given by

$$\begin{bmatrix} E_1 + E_2 \\ Z \end{bmatrix}$$

1 mark

(d) When $E_1 = E_2 = E$,

$$\begin{bmatrix} 2E \\ Z \end{bmatrix} = [3/Z][V_1] \rightarrow V_1 = \frac{2}{3}E$$

The currents in the original branches are

$$I_3 = (E - \frac{2}{3}E)/Z = E/3Z, I_4 = (E - \frac{2}{3}E)/Z = E/3Z, I_5 = (E - E)/Z = 0$$

$$I_1 = I_3 + I_5 = E/3Z, I_2 = I_4 - I_5 = E/3Z, I_6 = I_3 + I_4 = 2E/3Z$$

2 marks

Alternate Method convert delta containing Z, Z and Z to an equivalent star and proceed.

5. Mechanical output = 10.5 kW

Efficiency = 84%, \therefore Input electrical power = $10.5/0.84 = 12.5$ kW

Power factor = 0.70 lag. Terminal voltage = 400 V, line resistance = 0.2 Ω each phase

(a) Line current = $12500/(\sqrt{3} \times 400 \times 0.7) = 25.77$ A, phase angle = $\cos^{-1}0.7 = 45.57$ lag

Supply voltage = $400 + 0.2 \times \sqrt{3} \times 25.77 \angle -45.57^\circ = 400 + 6.25 - j6.37 = 406.30 \angle -0.90^\circ$ V

kVA input = $\sqrt{3} \times 406.3 \times 25.77 = 18.14$ kVA

reactive power taken by the motor = $18.14 \times \sin(-0.90^\circ + 45.57^\circ) = 12.75$ kvar

(b) Total active power = $18.14 \times \cos(-0.90^\circ + 45.57^\circ) = 12.90$ kW

[Alternate: Loss is the 3 wires = $3 \times 25.77^2 \times 0.2 = 0.398$ kW \rightarrow total = $12.5 + 0.398$]

New power factor = 0.96 $\rightarrow \phi = \cos^{-1}0.96 = 18.19^\circ$

Assuming the total active power remains constant and supply voltage remains unchanged, even after the connection of the capacitors,


New reactive power = $12.90 \times \tan 18.19^\circ = 4.24$ kvar

\therefore reactive power supplied by capacitors = $12.75 - 4.24 = 8.51$ kvar

$\therefore 3 \times C \times 100\pi \times 406.3^2 = 8510$

$C = 54.7$ μ F in each arm of the delta

2 marks

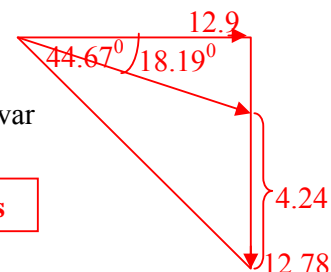

**EE 2010 - THEORY OF ELECTRICITY – Short Answers**(c) $I_{A0} = 1.0\angle-30^\circ\text{A}$, $I_{A1} = 2.0\angle0^\circ\text{A}$ and $I_{A2} = 1.0\angle30^\circ\text{A}$

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha^2 & \alpha \\ 1 & \alpha & \alpha^2 \end{bmatrix} \begin{bmatrix} 1.0\angle-30^\circ \\ 2.0\angle0^\circ \\ 1.0\angle30^\circ \end{bmatrix}$$

$$I_a = 1.0\angle-30^\circ + 2.0\angle0^\circ + 1.0\angle30^\circ = 0.866 - j0.5 + 2 + 0.866 + j0.5 = 3.732\angle0^\circ \text{ A}$$

$$I_b = 1.0\angle-30^\circ + 2.0\angle240^\circ + 1.0\angle150^\circ = 0.866 - j0.5 - 1.0 - j1.732 - 0.866 + j0.5 \\ = 2.0\angle240^\circ \text{ A}$$

$$I_c = 1.0\angle-30^\circ + 2.0\angle120^\circ + 1.0\angle270^\circ = 0.866 - j0.5 - 1.0 + j1.732 - j1.0 \\ = -0.134 + j0.232 = 0.268\angle120^\circ \text{ A}$$

2 marks

$$(d) [Z_p] = \begin{bmatrix} z_s & z_m & z_m \\ z_m & z_s & z_m \\ z_m & z_m & z_s \end{bmatrix}$$

the symmetrical component impedance matrix can be written as

$$[Z_s] = \frac{1}{3} [\Lambda]^* [Z_p] [\Lambda] = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} z_s & z_m & z_m \\ z_m & z_s & z_m \\ z_m & z_m & z_s \end{bmatrix} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha^2 & \alpha \\ 1 & \alpha & \alpha^2 \end{bmatrix} \\ = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} z_s + 2z_m & z_s + (\alpha + \alpha^2)z_m & z_s + (\alpha + \alpha^2)z_m \\ z_s + 2z_m & \alpha^2 z_s + (1 + \alpha)z_m & \alpha z_s + (1 + \alpha^2)z_m \\ z_s + 2z_m & \alpha z_s + (1 + \alpha^2)z_m & \alpha^2 z_s + (1 + \alpha)z_m \end{bmatrix}$$

which can be simplified using the property $1 + \alpha + \alpha^2 = 0$ as follows


$$[Z_s] = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} z_s + 2z_m & z_s - z_m & z_s - z_m \\ z_s + 2z_m & \alpha^2(z_s - z_m) & \alpha(z_s - z_m) \\ z_s + 2z_m & \alpha(z_s - z_m) & \alpha^2(z_s - z_m) \end{bmatrix} \\ = \frac{1}{3} \begin{bmatrix} 3(z_s + 2z_m) & 0 & 0 \\ 0 & (1 + \alpha^3 + \alpha^3)(z_s - z_m) & 0 \\ 0 & 0 & (1 + \alpha^3 + \alpha^3)(z_s - z_m) \end{bmatrix} \\ \text{i.e. } [Z_s] = \begin{bmatrix} (z_s + 2z_m) & 0 & 0 \\ 0 & (z_s - z_m) & 0 \\ 0 & 0 & (z_s - z_m) \end{bmatrix} = \begin{bmatrix} Z_0 & 0 & 0 \\ 0 & Z_1 & 0 \\ 0 & 0 & Z_2 \end{bmatrix}$$

2 marks



EE 2010 - THEORY OF ELECTRICITY – Short Answers

6.

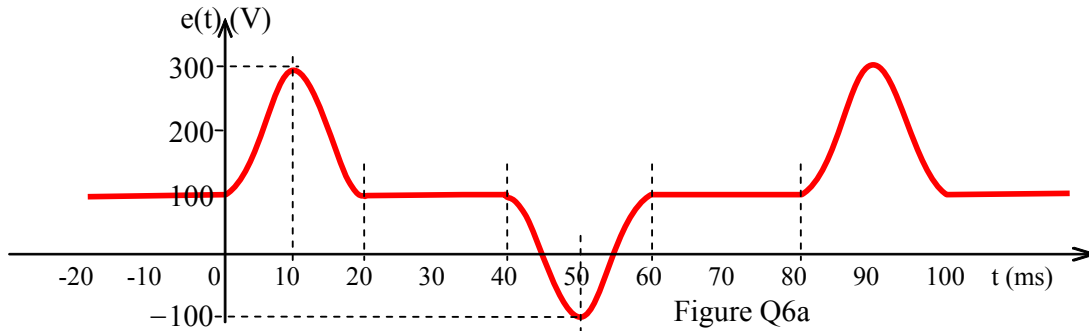

$$\begin{aligned} e(t) &= 200 - 100 \cos 100\pi t & 0 \leq t \leq 20 \text{ ms} \\ &= 100 & 20 \leq t \leq 40 \text{ ms} \\ &= 100 \cos 100\pi t & 40 \leq t \leq 60 \text{ ms} \\ &= 100 & 60 \leq t \leq 80 \text{ ms} \end{aligned}$$

$$\text{Period} = 80 \text{ ms} = 0.08 \text{ s}, \omega = 2\pi/0.08 = 25\pi \text{ rad/s}$$

(a) waveform may be shifted as follows to obtain a more symmetrical waveform

where $e(t) = f(t - 0.01) + 100$, or $f(t) = e(t + 0.01) - 100$

$$\begin{aligned} f(t) &= 100 - 100 \cos(100\pi t + \pi) = 100 + 100 \cos 100\pi t & 0 \leq t \leq 10 \text{ ms} \\ &= 0 & 10 \leq t \leq 20 \text{ ms} \end{aligned}$$

1 mark

$$f(t) = A_0/2 + \sum A_n \cos n\omega t + B_n \sin n\omega t$$

function $f(t)$ has mean value = 0 $\rightarrow A_0/2 = 0$ $f(t)$ is even $\rightarrow B_n = 0$ for all n $f(t)$ has half-wave symmetry \rightarrow even harmonics = 0

1 mark

$$\therefore A_n = 4 \times \frac{2}{T} \int_0^{0.02} f(t) \cdot \cos n\omega t \cdot dt =$$

$$\frac{8}{0.08} \left[\int_0^{0.01} (100 + 100 \cos 100\pi t) \cdot \cos n25\pi t \cdot dt + \int_{0.01}^{0.02} 0 \cdot \cos n\omega t \cdot dt \right]$$

$$A_n = 100 \times \left[(100 + 100 \cos 100\pi t) \cdot \frac{\sin n25\pi t}{n25\pi} \Big|_0^{0.01} - \int_0^{0.01} (100 \times (-100\pi \times \sin 100\pi t)) \cdot \frac{\sin n25\pi t}{n25\pi} \cdot dt + 0 \right]$$

$$= 100^2 \times \left[0 - 0 + \int_0^{0.01} \left(\frac{2}{n} [\cos(100\pi - 25n\pi)t - \cos(100\pi + 25n\pi)t] \right) dt \right]$$

$$= \frac{20000}{n} \times \left[\frac{\sin(100\pi - 25n\pi)t}{100\pi - 25n\pi} - \frac{\sin(100\pi + 25n\pi)t}{100\pi + 25n\pi} \right] \Big|_0^{0.01}$$

$$= \frac{800}{n} \times \left[\frac{\sin(\frac{n\pi}{4})}{(4-n)\pi} - \frac{\sin(\frac{n\pi}{4})}{(4+n)\pi} \right] = \frac{800 \sin(\frac{n\pi}{4})}{n} \times \frac{2n}{(4-n^2)\pi} = \frac{1600 \sin(\frac{n\pi}{4})}{(4-n^2)\pi}$$

2 marks

**EE 2010 - THEORY OF ELECTRICITY – Short Answers**

$$A_1 = 120.04, A_3 = 72.03, A_5 \dots = 17.14, -8.00, -4.68, \dots$$

$$\therefore f(t) = 120.04 \cos 25\pi t + 72.03 \cos 75\pi t + \dots$$

1 mark

$$\text{and } e(t) = f(t - 0.01) + 100 = 100 + 120.04 \cos (25\pi t - \pi/4) + 72.03 \cos (75\pi t - 3\pi/4) + \dots$$

(b) mean value = 100 V


$$\text{rms value} = \sqrt{100^2 + \frac{120.04^2}{2} + \frac{72.03^2}{2} + \dots} = 140.7 \text{ V}$$

2 marks

(limited accuracy due to low terms – actual value around 141.4 V)

(c) $I_n = E_n / (1 \times 10^4 + 1/jn25\pi \times 10 \times 10^{-6})$

$$I_n = \frac{10^{-4}}{1 - \frac{j}{2.5n\pi}} E_n$$

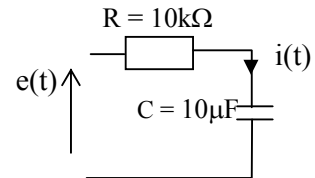1 mark

there will be no d.c. current flow due to the capacitance

$$I_1 = \frac{10^{-4}}{1 - j0.1273} E_1 = \frac{10^{-4}}{1.008 \angle -7.25^\circ} \times 120.04 = 0.0119 \angle 7.25^\circ$$

$$I_3 = \frac{10^{-4}}{1 - j0.0424} E_1 = \frac{10^{-4}}{1.0009 \angle -2.43^\circ} \times 72.03 = 0.0072 \angle 2.43^\circ$$

1 mark

$$\therefore i(t) = 0.0119 \cos (25\pi t - 45^\circ + 7.25^\circ) + 0.0072 \cos (75\pi t - 135^\circ + 2.43^\circ) + \dots$$


$$\text{i.e. } i(t) = 0.0119 \cos (25\pi t - 37.75^\circ) + 0.0072 \cos (75\pi t - 132.57^\circ) + \dots$$

1 mark

If value of R was 400 Ω instead of 10 kΩ

$$I_n = E_n / (400 + 1/jn25\pi \times 10 \times 10^{-6})$$

$$I_n = \frac{jn25\pi}{10^5 + j10000n\pi} E_n$$

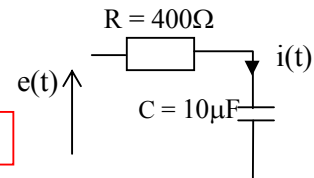1 mark

there will be no d.c. current flow due to the capacitance

$$I_1 = \frac{j25\pi}{10^5 + j10000\pi} E_1 = \frac{25\pi \angle 90^\circ}{104.8 \times 10^3 \angle 17.44^\circ} E_1 = 0.0007494 \angle 72.56^\circ E_1$$

$$I_3 = \frac{j75\pi}{10^5 + j30000\pi} E_3 = \frac{75\pi \angle 90^\circ}{137.4 \times 10^3 \angle 43.30^\circ} E_3 = 0.001715 \angle 46.70^\circ E_3$$

1 mark

$$\therefore i(t) = 0.090 \cos (25\pi t - 45^\circ + 72.56^\circ) + 0.124 \cos (75\pi t - 135^\circ + 46.70^\circ) + \dots$$


$$\text{i.e. } i(t) = 0.090 \cos (25\pi t + 27.56^\circ) + 0.124 \cos (75\pi t - 88.30^\circ) + \dots$$

1 mark



EE 2010 - THEORY OF ELECTRICITY – Short Answers

7. (a)

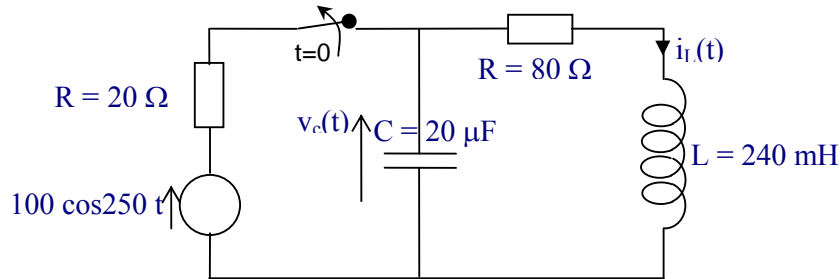

$$C \rightarrow 1/j 250 \times 20 \times 10^{-6} = -j 200 \Omega, L \rightarrow j 250 \times 240 \times 10^{-3} = j 50 \Omega$$

Working with peak values and complex numbers rather than with r.m.s. values to retain peak magnitudes

$$V_{C \max} = 100 \times \frac{-j200 // (80 + j60)}{20 - j200 // (80 + j60)}$$

$$V_{C \max} = 100 \times \frac{-j200 \times (80 + j60)}{20 \times (-j200 + 80 + j60) - j200 \times (80 + j60)}$$

$$V_{C \max} = \frac{1000 \angle -90^\circ \times 100 \angle 36.87^\circ}{-j200 + 80 + j60 - j800 + 600} = \frac{100000 \angle -53.13^\circ}{680 - j940} = \frac{100000 \angle -53.13^\circ}{1160 \angle -54.11^\circ}$$

$$= 86.2 \angle 0.98^\circ \text{ V}$$

$$v_c(t) = 86.2 \cos(250t + 0.98^\circ)$$

$$I_{L \max} = 86.2 \angle 0.98^\circ / (80 + j60) = 0.862 \angle -35.89^\circ \text{ A}$$

$$i_L(t) = 0.862 \cos(250t - 35.89^\circ)$$

Thus at $t = 0$, initial conditions

$$v_c(0) = 86.2 \cos(0.98^\circ) = 86.18 \text{ V}$$


$$i_L(0) = 0.862 \cos(-35.89^\circ) = 0.698 \text{ A}$$

4 marks

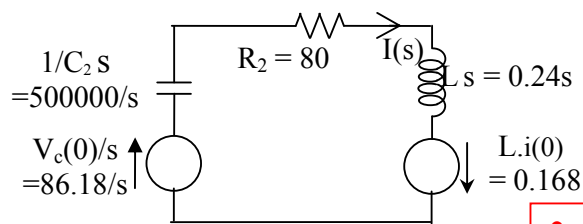(c) The transformed equivalent circuit, after the switch is opened, is given by

Thus the circuit current can be calculated as

$$I(s) = \frac{\frac{86.18}{s} + 0.168}{\frac{500000}{s} + 80 + 0.24s}$$



2 marks

$$I(s) = \frac{0.168s + 86.18}{0.24s^2 + 80s + 50000} = \frac{0.7s + 359.1}{s^2 + 333.3s + 20833} = \frac{0.7s + 359.1}{(s + 166.7)^2 + 424.9^2}$$

$$\text{i.e. } I(s) = \frac{0.7(s + 166.7) + 242.4}{(s + 166.7)^2 + 424.9^2} = 0.7 \frac{s + 166.7}{(s + 166.7)^2 + 424.9^2} + 0.57 \frac{424.9}{(s + 166.7)^2 + 424.9^2}$$

$$\therefore \text{ current is given by } i(t) = 0.7e^{-166.7t} \cos 424.9t + 0.57e^{-166.7t} \sin 424.9t$$

3 marks