



Level 2 Semester 2 Examination – June 2009

1. (a) i. Complete equivalent circuit as shown **[1 mark]**

$$\text{ii. } i = \frac{V_{in} - V_d}{R} = \frac{V_d}{R_{in}} + C \frac{d(V_d - V_{out})}{dt}$$

$$C \frac{d(V_d - V_{out})}{dt} = \frac{V_{out} + AV_d}{R_{out}} \quad \text{[2 marks]}$$

iii. With an ideal Operational amplifier,

$$R_{out} = 0, \text{ and } R_{in} = \infty, \quad V_{out} = -A V_d$$

$$\frac{V_{in} - V_d}{R} = 0 + C \frac{d(V_d - V_{out})}{dt}$$

$$\text{With } A \rightarrow \infty, V_d \rightarrow 0 \text{ giving } \frac{V_{in}}{R} = -C \frac{dV_{out}}{dt}$$

$$\text{Thus } V_{out} = -\frac{1}{CR} \int V_{in} dt \quad \text{[2 marks]}$$

$$\text{(b) } Z = j\omega L + r + \frac{R \times \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = j\omega L + r + \frac{R}{1 + j\omega CR}$$

$$\omega = 250 \text{ rad/s}$$

$$L\omega = 0.1 \times 250 = 25\Omega, \quad 1/C\omega = 1/0.0001 \times 250 = 40\Omega$$



$$Z = j25 + 10 + \frac{1000}{1 + j25} = (11.597 - j14.936) = 18.910 \angle -52.17^\circ \Omega$$

$$I = 200/18.910 \angle -52.17^\circ = 10.576 \angle 52.17^\circ \text{ A}$$

$$V_C = 200 - (10 + j25) \times 10.576 \angle 52.17^\circ = 200 - 26.926 \angle 68.20^\circ \times 10.576 \angle 52.17^\circ$$


$$= 200 - 284.77 \angle 120.37^\circ = 200 - (-143.98 + j245.69) = 343.98 - j245.69$$
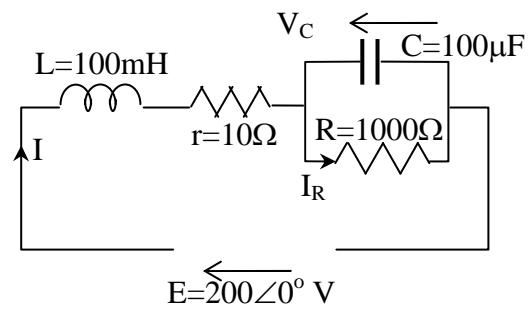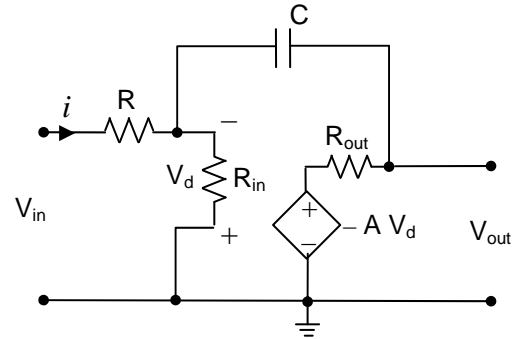
$$= 422.71 \angle -35.54^\circ \text{ V}$$



[1 mark]

[1 mark]

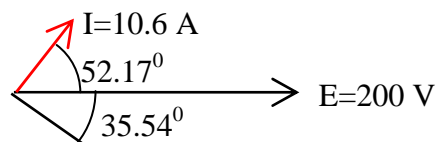

[1 mark]



(c) Resonance would occur when imaginary part of $\left[j\omega L + r + \frac{R}{1 + j\omega CR} \right]$ is equal to 0.

$$L = 100 \text{ mH}, r = 10 \Omega, C = 100 \mu\text{F}, R = 1000 \Omega$$

$$\text{i.e. } \omega L - \frac{\omega CR^2}{1 + \omega^2 C^2 R^2} = 0, 0.1\omega - \frac{\omega 0.0001 \times 1000^2}{1 + \omega^2 0.0001^2 1000^2} = 0$$

$$\text{i.e. } 1 + 0.01\omega^2 = 1000, \text{ since } \omega \neq 0$$

$$\text{i.e. } \omega^2 = 99900, \omega = 316.07 \text{ rad/s or } 50.30 \text{ Hz}$$

[1 mark]

$$\text{and circuit current at resonance} = \left[\frac{200}{10 + \frac{1000}{1 + (316.07 \times 0.0001 \times 1000)^2}} \right] = 18.18 \text{ A}$$

[1 mark]

2. (a) Reluctance = $l/\mu A$

$$A = 2 \text{ cm}^2, l_o = 20 \text{ cm}, l_m = 6 \text{ cm}, \mu_r = 2000$$

$$\text{outer limb reluctance } S_o = l_o / \mu_o \mu_r A$$

$$S_o = 0.2 / (4\pi \times 10^{-7} \times 2000 \times 2 \times 10^{-4}) = 0.3979 \times 10^6 \text{ H}^{-1}$$


$$\text{middle limb reluctance } S_m = l_m / \mu_o \mu_r A$$

$$S_m = 0.06 / (4\pi \times 10^{-7} \times 2000 \times 2 \times 10^{-4}) = 0.1194 \times 10^6 \text{ H}^{-1}$$

$$I_A = 20 \angle 0^\circ \text{ A}, N = 100$$

$$\mathfrak{F}_A = 2000 \angle 0^\circ \text{ A}, \mathfrak{F}_B = 2000 \angle -120^\circ \text{ A}, \mathfrak{F}_C = 2000 \angle 120^\circ \text{ A}$$

Equivalent circuit with values [4 marks]

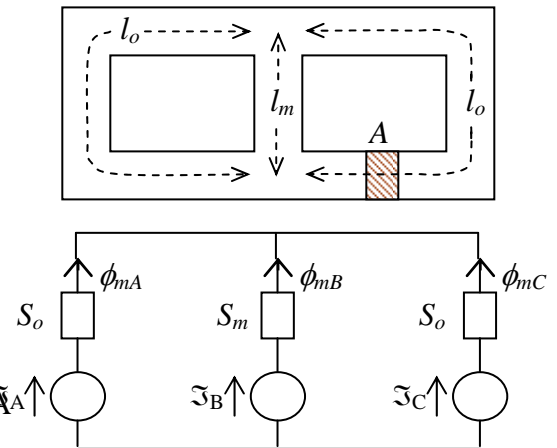

(b) Since the resistors on either side are equal,

$$V_{\text{Thevenin}} = (100 \angle 0^\circ + 70.7 \angle 45^\circ) / 2$$

$$= (100 + 50 + j 50) / 2 = 75 + j 25 \text{ V}$$

$$Z_{\text{Thevenin}} = 30 / 30 = 15 \Omega \quad [2 \text{ marks}]$$

i. for inductance, $Z = j 40 \Omega$

$$\text{current} = (75 + j 25) / (15 + j 40) = 79.057 \angle 18.43^\circ / 42.720 \angle 69.44^\circ$$

$$= 1.851 \angle -51.01^\circ \text{ A} \quad [1 \text{ mark}]$$

ii. for resistance, $Z = 40 \Omega$

$$\text{current} = (75 + j 25) / (15 + 40) = 79.057 \angle 18.43^\circ / 55 = 1.437 \angle -18.43^\circ \text{ A} \quad [1 \text{ mark}]$$

iii. for maximum power transfer, $Z = 15 \Omega$

$$\text{current in the circuit} = (75 + j 25) / (15 + 15) = 79.057 \angle 18.43^\circ / 30 = 2.635 \angle 18.43^\circ$$

$$\text{maximum power} = 2.635^2 \times 15 = 104 \text{ W} \quad [2 \text{ marks}]$$

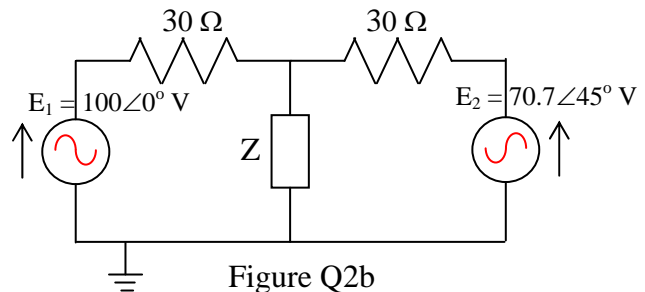


Figure Q2b



3. (a)


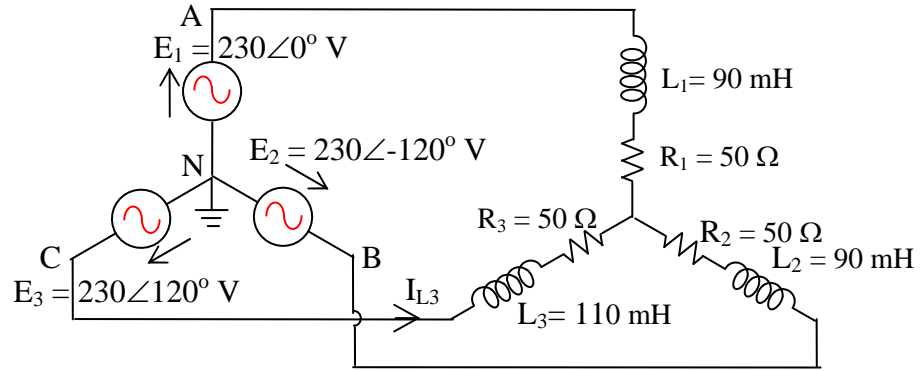
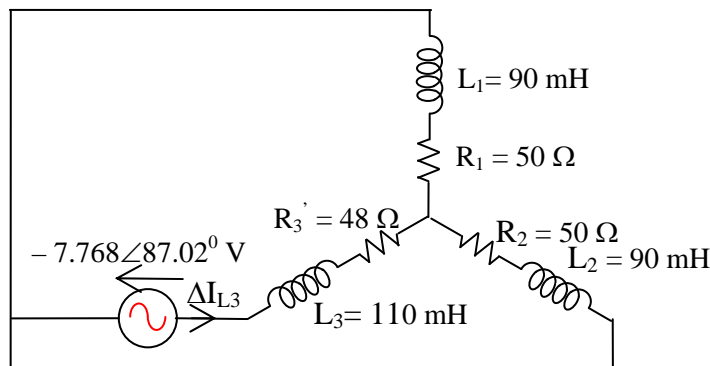


Figure Q3a

Using compensation theorem, changes can be obtained from

$$I = 3.884 \angle 87.02^\circ \text{ A}$$
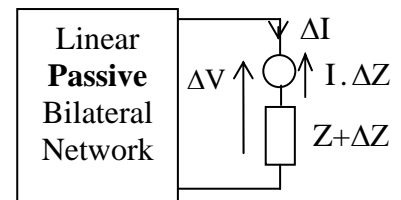
$$\Delta Z = -2 \Omega, I \cdot \Delta Z = -7.768 \angle 87.02^\circ \text{ V}$$





At 50 Hz, 90 mH → j28.27 Ω, 110 mH → j34.56 Ω

$$\Delta I_{L3} = -(-7.768 \angle 87.02^\circ) / (48 + j34.56 + 25 + j17.28) = 7.768 \angle 87.02^\circ / 89.53 \angle 35.38^\circ = 0.08676 \angle 51.64^\circ \text{ A}$$

$$\text{New } I_{L3} = 3.884 \angle 87.02^\circ + 0.08676 \angle 51.64^\circ = 0.202 + j3.879 + 0.054 + j0.068 = 0.256 + j3.947 = 3.955 \angle 86.29^\circ \text{ A}$$

[2 marks]

(b)

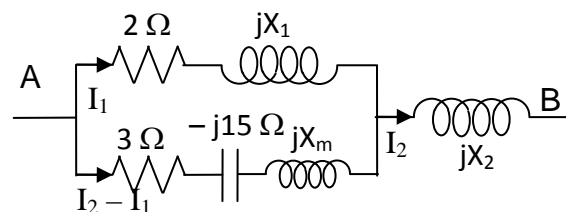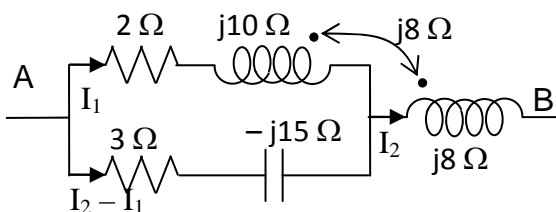

Consider the uncoupled equivalent circuit shown.

$$V_{AB} = 2 I_1 + (j10 I_1 - j8 I_2) + (j8 I_2 - j8 I_1) \equiv 2 I_1 + jX_1 I_1 + j X_2 I_2$$


Comparison of coefficients of I_1 gives $2 + j10 - j8 = 2 + j X_1$ or $X_1 = 2 \Omega$

Comparison of coefficients of I_2 gives $-j8 + j8 = j X_2$ or $X_2 = 0 \Omega$



Also, $V_{AB} = (3 - j15)(I_2 - I_1) + (j8 I_2 - j8 I_1) \equiv (3 - j15 + jX_m)(I_2 - I_1) + j X_2 I_2$

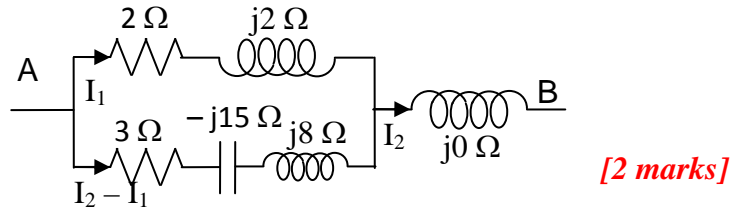Comparison of coefficients of I_1 gives $-3 + j15 - j8 = -3 + j15 - jX_m$ or $X_m = 8 \Omega$



(c) The two port admittance matrix is given by


$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

$$z_{11}|_{V_2=0} = 40 + j30 + (40 + j30) // (40 + j30) = 60 + j45 = 75 \angle 36.87^\circ$$

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{1}{z_{11}} = 0.01333 \angle -36.87^\circ \text{ S (or } 0.01066 - j0.008 \text{ S)}$$

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = \left. \frac{I_1}{V_1} \times \frac{I_2}{I_1} \right|_{V_2=0} = 0.01333 \angle -36.87^\circ \times \left(-\frac{1}{2} \right) = 0.00667 \angle 143.13^\circ \text{ S (or } -0.00533 + j0.004 \text{ S)}$$

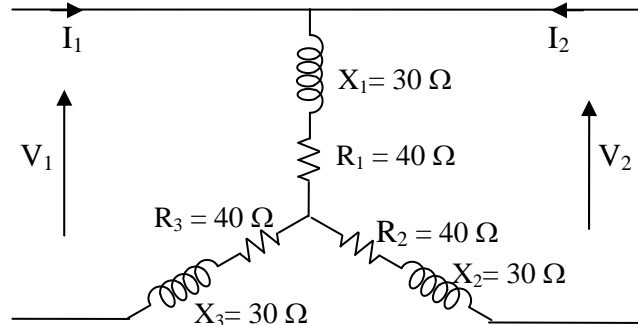

By symmetry

$$y_{12} = y_{21} = 0.00667 \angle 143.13^\circ \text{ S}$$

$$y_{22} = y_{11} = 0.01333 \angle -36.87^\circ \text{ S}$$

The two port admittance matrix is

$$[Y] = \begin{bmatrix} 0.0133 \angle -36.9^\circ & 0.0067 \angle 143.1^\circ \\ 0.0067 \angle 143.1^\circ & 0.0133 \angle -36.9^\circ \end{bmatrix}$$

[3 marks]

(b) Characteristic impedance Z_0 is given when

$$V_1/I_1 = Z_0 = V_2/(-I_2)$$

i.e. using two port admittance parameters,

$$I_1 = y_{11}Z_0I_1 - y_{12}Z_0I_2$$

$$I_2 = y_{21}Z_0I_1 - y_{22}Z_0I_2$$

$$\therefore \frac{I_2}{I_1} = \frac{y_{11}Z_0 - 1}{y_{12}Z_0} = \frac{y_{21}Z_0}{y_{22}Z_0 + 1}$$

Since $y_{22} = y_{11}$, and $y_{12} = y_{21}$


$$y_{11}^2 Z_0^2 - 1 = y_{12}^2 Z_0^2$$




$$\begin{aligned}
 Z_0 &= \sqrt{\frac{1}{y_{11}^2 - y_{12}^2}} = \sqrt{\frac{1}{0.01333^2 \angle -36.87^\circ - 0.00667^2 \angle 143.13^\circ}} \\
 &= \sqrt{\frac{1}{0.0001777 \angle -73.74^\circ - 0.00004444 \angle 286.26^\circ}} = \sqrt{\frac{1}{37.3 \times 10^{-6} - j128 \times 10^{-6}}} \\
 &= \sqrt{\frac{1}{1.33 \times 10^{-4} \angle -73.75^\circ}} \\
 Z_0 &= \underline{\underline{86.7 \angle 36.87^\circ \Omega}}
 \end{aligned}$$

[3 marks]

4. (a)

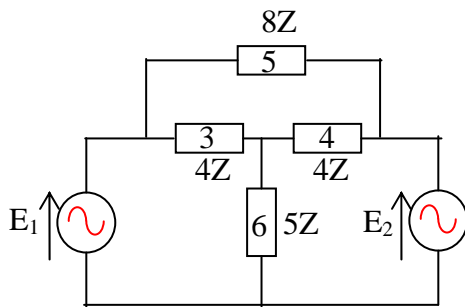

The oriented graph of the network is

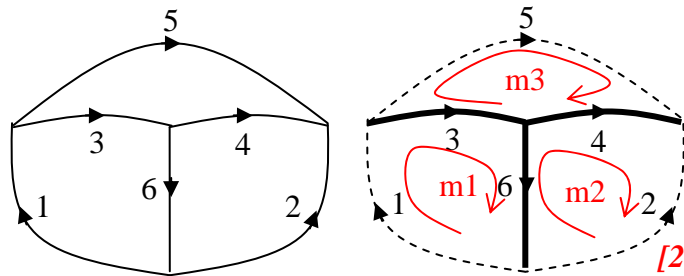

[2 marks]

The selected **tree** of the network is shown in a full line and those of the co-tree, forming the independent loops, are shown in a broken line.

(b) Branch impedance matrix $[Z_b]$, Branch source voltage vector \underline{E}_{gb} and the mesh-branch incidence matrix $[B]$ are as follows.

$$[Z_b] = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 4Z & 0 & 0 & 0 \\ 0 & 0 & 0 & 4Z & 0 & 0 \\ 0 & 0 & 0 & 0 & 8Z & 0 \\ 0 & 0 & 0 & 0 & 0 & 5Z \end{bmatrix}, \quad [E_{gb}] = \begin{bmatrix} E_1 \\ E_2 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}, \quad [B] = \begin{bmatrix} 1 & 0 & 0 \\ 0 & -1 & 0 \\ 1 & 0 & -1 \\ 0 & 1 & -1 \\ 0 & 0 & 1 \\ 1 & -1 & 0 \end{bmatrix} \quad [1+1+1 \text{ marks}]$$

$$[Z_m] = [B]^t [Z_b] [B] = \begin{bmatrix} 1 & 0 & 1 & 0 & 0 & 1 \\ 0 & -1 & 0 & 1 & 0 & -1 \\ 0 & 0 & -1 & -1 & 1 & 0 \end{bmatrix} \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 4Z & 0 & 0 & 0 \\ 0 & 0 & 0 & 4Z & 0 & 0 \\ 0 & 0 & 0 & 0 & 8Z & 0 \\ 0 & 0 & 0 & 0 & 0 & 5Z \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & -1 & 0 \\ 1 & 0 & -1 \\ 0 & 1 & -1 \\ 0 & 0 & 1 \\ 1 & -1 & 0 \end{bmatrix}$$

$$[Z_m] = \begin{bmatrix} 9Z & -5Z & -4Z \\ -5Z & 9Z & -4Z \\ -4Z & -4Z & 16Z \end{bmatrix}$$

[1 mark]



$$\underline{E}_{gm} = [B]^t \underline{E}_{gb} = \begin{bmatrix} 1 & 0 & 1 & 0 & 0 & 1 \\ 0 & -1 & 0 & 1 & 0 & -1 \\ 0 & 0 & -1 & -1 & 1 & 0 \end{bmatrix} \begin{bmatrix} E_1 \\ E_2 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} E_1 \\ -E_2 \\ 0 \end{bmatrix} \quad [1 \text{ mark}]$$

$$\begin{bmatrix} E \\ -E \\ 0 \end{bmatrix} = \begin{bmatrix} 9Z & -5Z & -4Z \\ -5Z & 9Z & -4Z \\ -4Z & -4Z & 16Z \end{bmatrix} \begin{bmatrix} I_{m1} \\ I_{m2} \\ I_{m3} \end{bmatrix}, \quad \begin{bmatrix} I_{m1} \\ I_{m2} \\ I_{m3} \end{bmatrix} = \begin{bmatrix} 9Z & -5Z & -4Z \\ -5Z & 9Z & -4Z \\ -4Z & -4Z & 16Z \end{bmatrix}^{-1} \begin{bmatrix} E \\ -E \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} I_{m1} \\ I_{m2} \\ I_{m3} \end{bmatrix} = \frac{1}{\Delta} \begin{bmatrix} 128Z^2 & 96Z^2 & 56Z^2 \\ 96Z^2 & 128Z^2 & 56Z^2 \\ 56Z^2 & 56Z^2 & 56Z^2 \end{bmatrix}^{-1} \begin{bmatrix} E \\ -E \\ 0 \end{bmatrix}, \quad \Delta = (128 \times 9 - 96 \times 5 - 56 \times 4)Z^3 = 448 Z^3$$

$$\begin{bmatrix} I_{m1} \\ I_{m2} \\ I_{m3} \end{bmatrix} = \frac{1}{Z} \begin{bmatrix} 0.2857 & 0.2143 & 0.125 \\ 0.2143 & 0.2857 & 0.125 \\ 0.125 & 0.125 & 0.2857 \end{bmatrix} \begin{bmatrix} E \\ -E \\ 0 \end{bmatrix}, \quad I_{m1} = 0.0714E/Z, I_{m2} = -0.0714E/Z, I_{m3} = 0$$

i.e. $I_1 = 0.0714E/Z, I_2 = 0.0714E/Z, I_3 = 0.0714E/Z, I_4 = 0.0714E/Z, I_5 = 0, I_6 = 0.1428E/Z$ [3 marks]

5. (a) 3-phase, 400 V, 50 Hz star-connected load, $(80 + j60) \Omega$ each arm.

current drawn = $(400/\sqrt{3})/(80 + j60) = 2.309 \angle -36.87^\circ$ A

active power consumed = $\sqrt{3} \times 400 \times 2.309 \times \cos(36.87^\circ) = 1.28$ kW (or $3 \times 2.309^2 \times 80$)

power factor of the load = $\cos(36.87^\circ) = 0.8$ lag

[2 marks]

(b) 3-phase motor, 1 kW, p.f. = 0.72 lag added.

line current supplied from motor = $1000/(\sqrt{3} \times 400 \times 0.72) = 2.005 \angle -43.95^\circ$ A

line current supplied from the source = $2.309 \angle -36.87^\circ + 2.005 \angle -43.95^\circ$
 $= 1.847 - j 1.385 + 1.443 - j 1.392 = 3.290 - j 2.777 = 4.305 \angle -40.2^\circ$ A

supply power factor = $\cos(40.2^\circ) = 0.764$ lag

[1 mark]

(c) Reactive power = $\sqrt{3} \times 400 \times 4.305 \times \sin(40.2^\circ) = 1925$ var, Active Power = $1 + 1.28 = 2.28$ kW

improve load power factor to 0.95 lag, power factor angle = 18.19°

New reactive power = $2280 \tan 18.19^\circ = 749.4$

Reactive power required to be supplied = $1925 - 749 = 1176$ var

Rating of each capacitor = $1176/3 = 392$ var

For delta connected capacitors, $C = 392/(400^2 \times 100\pi) = 7.80 \mu\text{F}$ each.

[2 marks]



(d) $I_A = 10.0\angle-30^\circ\text{A}$, $I_B = 4.0\angle-120^\circ\text{A}$ and $I_C = 6.0\angle115^\circ\text{A}$.

The symmetrical components of the currents in phase A are given by

$$\begin{bmatrix} I_{A0} \\ I_{A1} \\ I_{A2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} 10.0\angle-30^\circ \\ 4.0\angle-120^\circ \\ 6.0\angle115^\circ \end{bmatrix}$$

$$I_{A0} = (10.0\angle-30^\circ + 4.0\angle-120^\circ + 6.0\angle115^\circ)/3 = (2.887 - j1.667 - 0.667 - j1.155 - 0.845 + j1.813) \\ = 1.375 - j1.009 = 1.705\angle-36.3^\circ\text{ A}$$

$$I_{A1} = (10.0\angle-30^\circ + 4.0\angle0^\circ + 6.0\angle355^\circ)/3 = (2.887 - j1.667 + 1.333 + 1.992 - j0.174) \\ = 6.212 - j1.841 = 6.480\angle-16.5^\circ\text{ A}$$

$$I_{A2} = (10.0\angle-30^\circ + 4.0\angle120^\circ + 6.0\angle235^\circ)/3 = (2.887 - j1.667 - 0.667 + j1.155 - 1.147 - j1.638) \\ = 1.073 - j2.150 = 2.403\angle-63.5^\circ\text{ A} \quad [3\text{ marks}]$$

(e) Only positive sequence voltage of 230.9 V is present, and hence only positive sequence power will be present.


Power associated with zero sequence component = 0

Power associated with positive sequence component = $\sqrt{3} \times 400 \times 6.480 \times \cos(16.5) = 4305\text{ W}$

Power associated with negative sequence component = 0

[2 marks]

6.

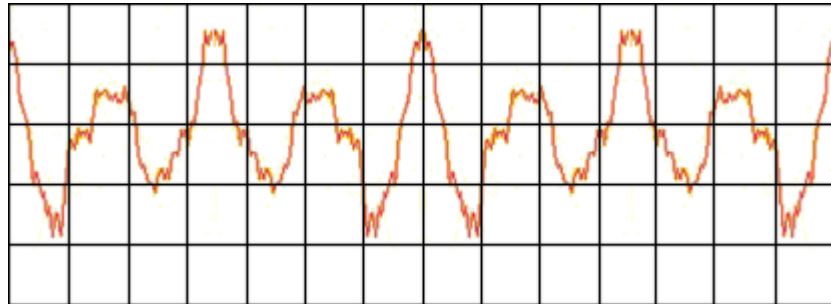

(a) 1 div = 2.5 ms

i. Period of the waveform $\rightarrow 7\text{ div} \rightarrow 7 \times 2.5 = 17.5\text{ ms}$

[1 mark]

ii. Has even symmetry. This gives only cosine terms in the Fourier series or $B_n = 0$

[1 mark]

iii. The most dominant harmonic frequency repeats itself 4 times within 1 cycle.

i.e. frequency = $4/17.5 \times 10^{-3} = 228.6\text{ Hz}$

[2 marks]

(b) $v(t) = 100 \sin 250 t$ volt, $i(t) = 20 + 10 \sin (250t + \pi/3) - 4 \sin (750t - \pi/6)$ ampere

i. rms value of $i(t) = \sqrt{20^2 + \frac{10^2}{2} + \frac{4^2}{2}} = 21.40\text{ A}$

[2 marks]

ii. Average power supplied = $\frac{100}{\sqrt{2}} \times \frac{10}{\sqrt{2}} \times \cos \frac{\pi}{3} = 250\text{ W}$

[2 marks]



- (c) $i(t) = 20 + 10 \sin(250t + \pi/3) - 4 \sin(750t - \pi/6)$ A, series $L = 10$ mH, $r = 1 \Omega$

$$\text{voltage drop} = L \frac{di}{dt} + r i = 0.01 \frac{di}{dt} + 1 \times i$$

$$= 0.01 \times [10 \times 250 \times \cos(250t + \pi/3) - 4 \times 750 \times \cos(750t - \pi/6)] + 20 + 10 \sin(250t + \pi/3) - 4 \sin(750t - \pi/6)$$

$$= 20 + 10 \sin(250t + \pi/3) + 25 \cos(250t + \pi/3) - 4 \sin(750t - \pi/6) - 15 \cos(750t - \pi/6)$$

Since the sine and cosine terms have the same phase angles, they can be easily combined to give

$$\text{rms voltage drop} = \sqrt{20^2 + \frac{10^2 + 25^2}{2} + \frac{4^2 + 30^2}{2}} = 34.94 \text{ V} \quad [2 \text{ marks}]$$

7. (a) Proof of the Laplace transform of


(i) unit step $h(t) \rightarrow \frac{1}{s}$ [1 mark]

(ii) unit ramp $r(t) \rightarrow \frac{1}{s^2}$ [1 mark]

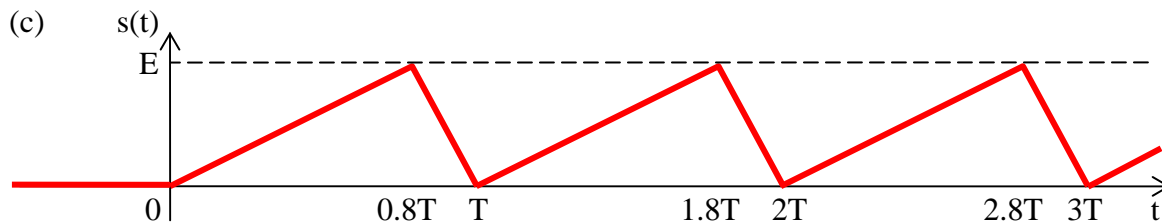
- (b) $f_1(t)$ defined for $0 < t \leq T$, Laplace transform $F_1(s)$.

Laplace transform $F(s)$ of repetitive waveform $f(t)$ with period T , where $f(t) = f_1(t)$ for $0 < t \leq T$

Proof of $F(s) = \frac{1}{1 - e^{-sT}} F_1(s)$ [2 marks]



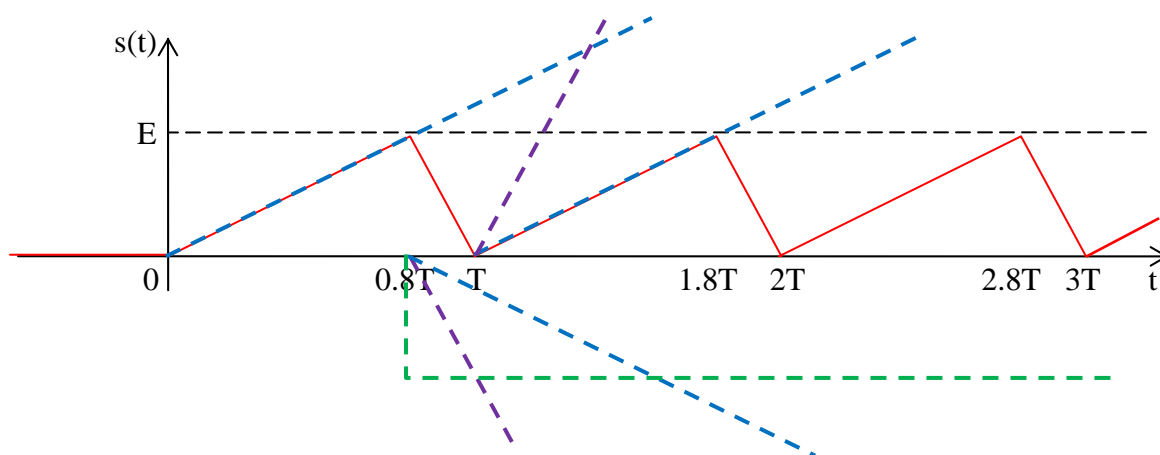Laplace transform of the causal repetitive sawtooth waveform $s(t)$ can be obtained by the superposition of ramp and step waveforms as follows.




$$s(t) = \frac{1.25E}{T} \cdot r(t) - E \cdot h(t - 0.8T) - \left(\frac{1.25E}{T} + \frac{5E}{T} \right) \cdot r(t - 0.8T) \cdot h(t - 0.8T) \quad \text{for } 0 < t < T$$


$$S(s) = \frac{1}{1 - e^{-sT}} \cdot \left[\frac{1.25E}{T} \cdot \frac{1}{s^2} - E \cdot \frac{1}{s + 0.8T} - \frac{6.25E}{T} \cdot \frac{1}{(s + 0.8T)^2} \right] \quad [4 \text{ mark}]$$



(d)

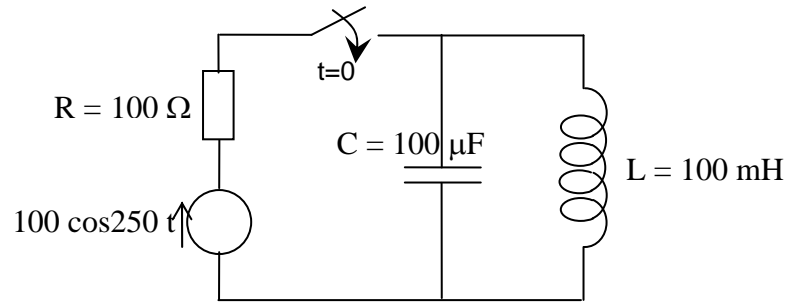

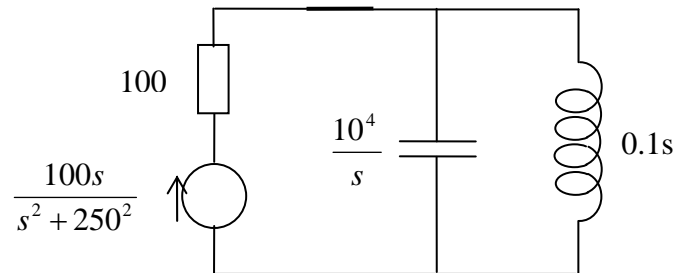The Laplace transformed equivalent circuit is shown



[2 marks]