



**University of Moratuwa, Sri Lanka**  
Faculty of Engineering  
Department of Electrical Engineering  
B. Sc. Engineering Honours Degree Course  
Level 2 – Semester 1 Examination  
**EE201 – THEORY OF ELECTRICITY**

Time Allowed: 3 Hours

August 2006

---

**Additional Material**

Graph Paper will be provided if required.

**Instructions to Candidates**

This paper contains 7 questions in 4 pages.

This examination accounts for 70% of the module assessment.

Total marks for the paper is 70 marks.

The maximum mark attainable for each part is indicated in square brackets.

Answer **All** Questions.

This is a closed book examination and only authorised Calculators will be permitted.

**Technical Information for candidates**

Permeability of free space  $\mu_0 = 4 \pi \times 10^{-7}$  H/m

Permittivity of free space  $\epsilon_0 = 8.854 \times 10^{-12}$  F/m

Velocity of light in free space =  $2.998 \times 10^8$  m/s

Question 1

- (a) A certain alternating voltage source has an internal emf of 240 V at 50 Hz, an internal impedance of  $(10+j10) \Omega$  and supplies a load of  $(R + jX)$ . If the terminal voltage is to be kept at 230 V, write down an equation to relate the magnitudes of the internal emf and the terminal voltage in terms of R and X. [2 marks]
- (b) Determine the value of the R and X required to transfer maximum power to the load. [5 marks]
- (c) Determine the values of this maximum power, and the load current under these conditions. [1 marks]
- (d) Draw the phasor diagram showing the internal emf, the load voltage, voltages across R and X and the current under these conditions. [2 marks]

Question 2

- (a) Briefly explain three significantly different methods of defining the resonance frequency of an R-L-C circuit. [2 marks]
- (b) Figure Q2bc shows a circuit which is mutually coupled. Using first principles, convert it to a non-coupled circuit. [3 marks]
- (c) Using the result of Q2(b) or otherwise, determine the resonance frequency and the current at resonance. [2 marks]
- (d) Determine the frequencies at the half-power points. [3 marks]

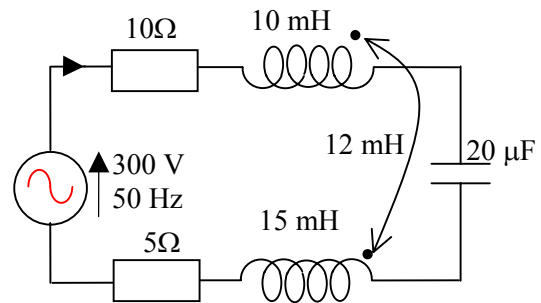


Figure Q2bc

Question 3

- (a) For the circuit shown in figure Q3-4, find the Thevenin's equivalent circuit at the broken line **B**. [4 marks]
- (b) Determine the z-parameter two-port matrix for the network shown in figure Q3-4 with the port 1 taken at the broken line at **A** and the port 2 taken at the broken line at **B**. [4 marks]

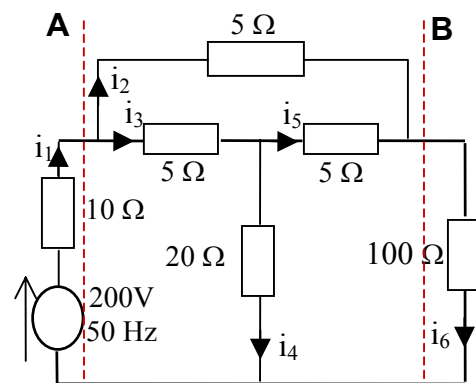


Figure Q3-4

#### Question 4

- (a) For the circuit shown in figure Q3-4, write down the branch-mesh incidence matrix and the branch impedance matrix. *[2 marks]*
- (b) Show how the mesh impedance matrix may be obtained from the branch-mesh incidence matrix and the branch impedance matrix. Hence or otherwise write down the mesh impedance matrix. *[2 marks]*
- (c) Using matrix mesh analysis, determine the mesh currents. *[3 marks]*
- (d) determine the currents in all the branches in figure Q3-4. *[3 marks]*

#### Question 5

A 3 phase, 50 Hz, 3-wire, balanced supply feeds, with a voltage of 400 V at the load end, (i) a balanced star connected load with each arm consisting of a series combination of an inductor  $L = 100 \text{ mH}$  and a resistor  $R = 50 \Omega$ , and (ii) a balanced three phase motor of rated at 1 kW running at full load at power factor 0.6 lag.

Determine

- (a) the total line current supplied from the source *[3 marks]*
- (b) the total reactive power supplied. *[1 marks]*

If each of the lines supplying the load has an impedance ( $l = 10 \text{ mH}$ ,  $r = 5 \Omega$ ), determine

- (c) the voltage at the supply end of the line, *[2 marks]*
- (d) the overall power factor at the source, and *[1 marks]*
- (e) the capacitances that must be connected across the combined load to improve the power factor to 0.9 lag when the load voltage is 400 V. *[3 marks]*

#### Question 6

- (a) Write down the matrix equation relating the phase voltages with the corresponding sequence components. *[1 marks]*
- (b) Determine the phase components corresponding to the sequence components. *[3 marks]*

$$\text{Positive sequence voltage} = 200\angle 0^\circ \text{ V}$$

$$\text{Negative sequence voltage} = 100\angle -30^\circ \text{ V}$$

$$\text{Zero sequence voltage} = 50\angle 90^\circ \text{ V}$$

- (c) Using the results obtained in 6(b), show graphically, how the positive sequence component may be determined. *[2 marks]*

Question 7

- (a) Very briefly explain the link between the Fourier Series, Fourier Transform and the Laplace Transform. [2 marks]
- (b) Determine the Fourier Series of the periodic waveform  $i(t)$  shown in figure Q7b to 3 significant terms. [6 marks]

$$i(t) = 100 \cos 314 t \quad \text{for } 0 < t \leq 0.005$$

$$i(t) = 100 - 20000.t \quad \text{for } 0.005 < t \leq 0.01$$

$$i(t) = 300 - 20000.t/ \quad \text{for } 0.01 < t \leq 0.015$$

$$i(t) = -100 \cos 314 t \quad \text{for } 0.015 < t \leq 0.02$$

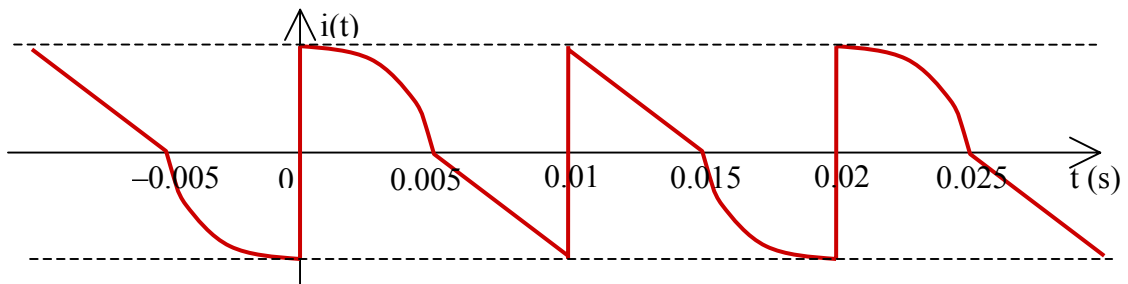


Figure Q7b

- (c) If a current  $i(t) = 10 \sin 314 t + 75 \sin 628 t - 15 \sin 942 t$  is supplied to a series RL circuit ( $R=10 \Omega$ ,  $L = 10 \text{ mH}$ ), determine an expression for the corresponding voltage across the circuit. [1 marks]
- (d) Determine the Laplace Transform of the following:
- causal ramp waveform  $t$  [1 marks]
  - causal step waveform  $h(t)$  [1 marks]
  - causal sine waveform  $\sin \omega t$  [1 marks]
  - causal waveform  $v(t)$  shown in figure Q7d. [3 marks]

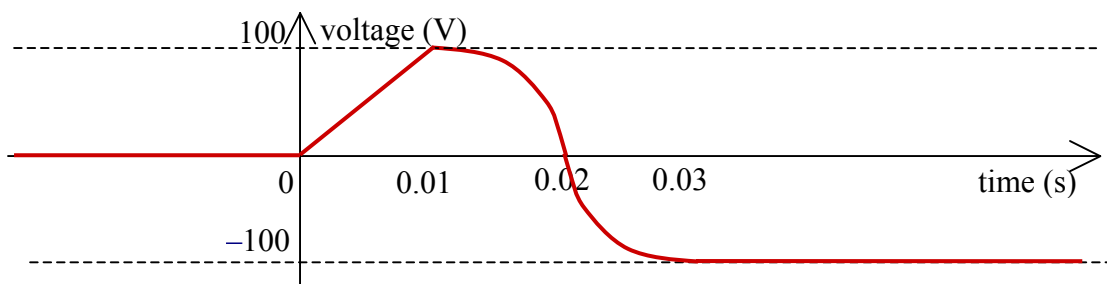


Figure Q7d

$$v(t) = 10000 t \quad \text{for } 0 < t \leq 0.01,$$

$$v(t) = 100 \sin 50\pi t \quad \text{for } 0.01 < t \leq 0.03$$

- (e) If the voltage waveform  $v(t)$  shown in figure Q7d is applied across a series RC circuit ( $R=10 \Omega$ ,  $C = 10 \mu\text{F}$ ), show how an expression for the Laplace transform of the corresponding current in the circuit is determined. [1 mark]

[END OF QUESTION PAPER]