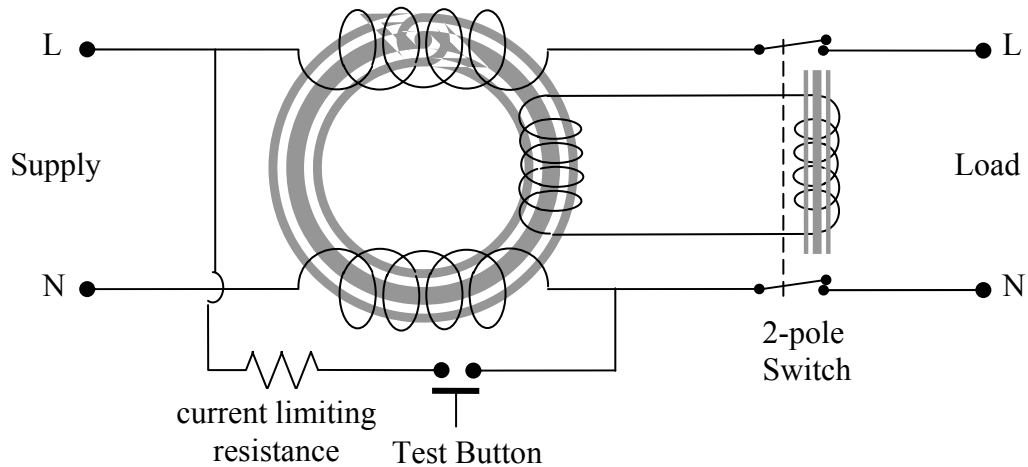




EE 201 - THEORY OF ELECTRICITY – Short Answers

Level 2 Examination - December 2002


1. (a)



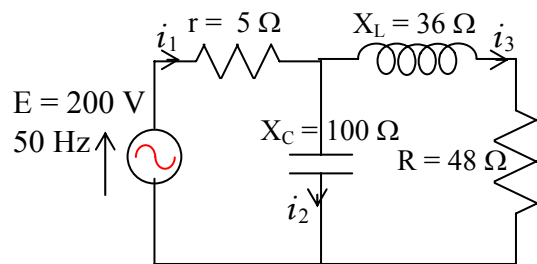(b) $-jX_c // (R + jX_L)$

$$= \frac{-j100(48 + j36)}{48 + j36 - j100}$$

$$= \frac{100 \angle -90^\circ \times 60 \angle 36.87^\circ}{80 \angle -53.13^\circ} = 75 \Omega$$




Total impedance = 5 + 75 = 80 Ω

$i_1 = 200 \angle 0^\circ / 80 = 2.5 \angle 0^\circ \text{ A,}$

$i_2 = 1.875 \angle 90^\circ \text{ A,}$

$i_3 = 3.125 \angle -36.9^\circ \text{ A}$

(c)

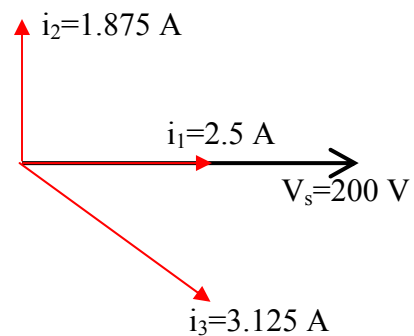

2. (a) $Z = 1/j\omega C + j\omega(L_1 + L_2 + 2M) + R$

$= -j 2 \times 10^5 / \omega + j\omega 0.032 + 10 \Omega$


(b) At resonance, power factor=1

$\omega = 2500 \text{ rad/s, } f = 397.9 \text{ Hz}$

$Q = 8$ at resonance

$I = 10 \angle 0^\circ \text{ A}$ at resonance

(c) $V_L = 425 \angle 90^\circ \text{ V}$ at resonance

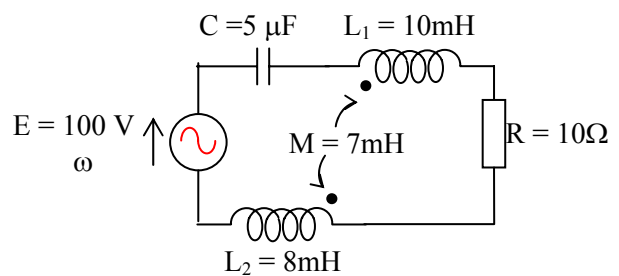



EE 201 - THEORY OF ELECTRICITY – Short Answers



3. (a) $120 \text{ mH} \rightarrow j 30 \Omega$, $100 \mu\text{F} \rightarrow -j40 \Omega$

with AB open, $i = 5 \angle -36.9^\circ \text{ A}$

$V_{th} = 200 \angle -36.9^\circ \text{ V}$




$Z_{th} = 19.2 + j15.6 = 24.74 \angle 39.1^\circ \Omega$

Thevenin's equivalent circuit

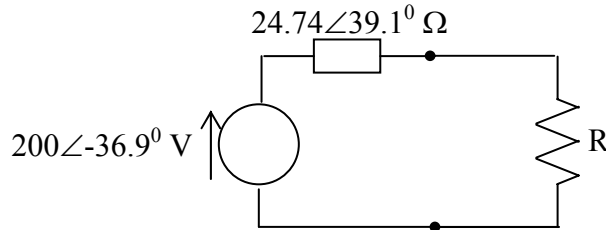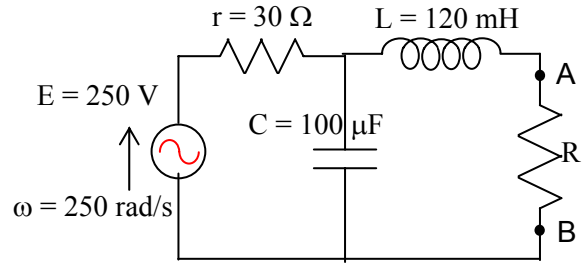


(b) $P = \frac{200^2 \cdot R}{(R + 19.2)^2 + 15.6^2}$, for maximum power $R = 24.74 \Omega$, $P_{max} = 455 \text{ W}$

4. (a) **Equivalent current sources**

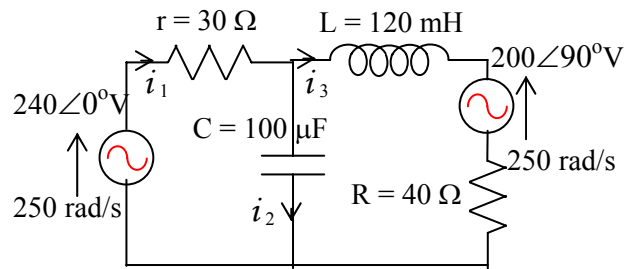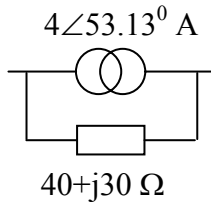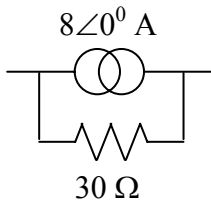

(b)

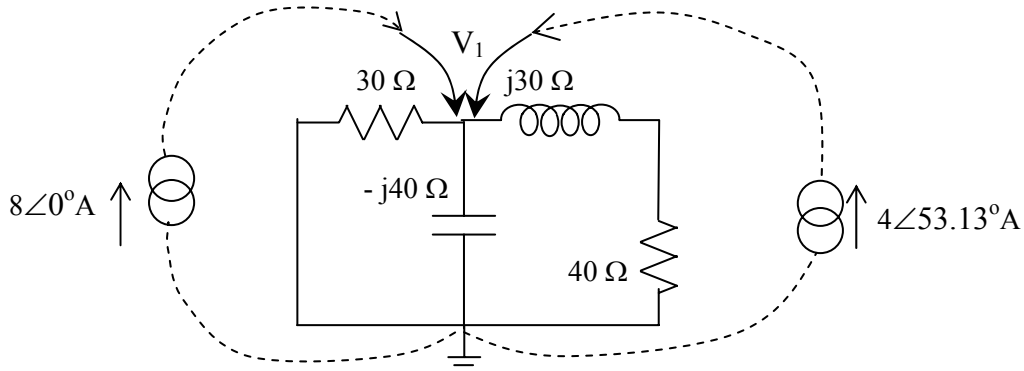

nodal admittance matrix $[Y_N] = \left[\frac{1}{30} + \frac{1}{-j40} + \frac{1}{40 + j30} \right] = [0.0510 \angle 14.76^\circ]$

nodal injected current source $I_N = 8 \angle 0^\circ \text{ A} + 4 \angle 53.13^\circ = 10.88 \angle 17.10^\circ \text{ A}$


(c) $i_1 = 0.897 - j 0.290 = 0.94 \angle -17.90 \text{ A}$

$i_2 = -0.214 + j 5.329 = 5.33 \angle 92.30 \text{ A}$


$i_3 = 1.111 - j 5.619 = 5.73 \angle -78.80 \text{ A}$

**EE 201 - THEORY OF ELECTRICITY – Short Answers**

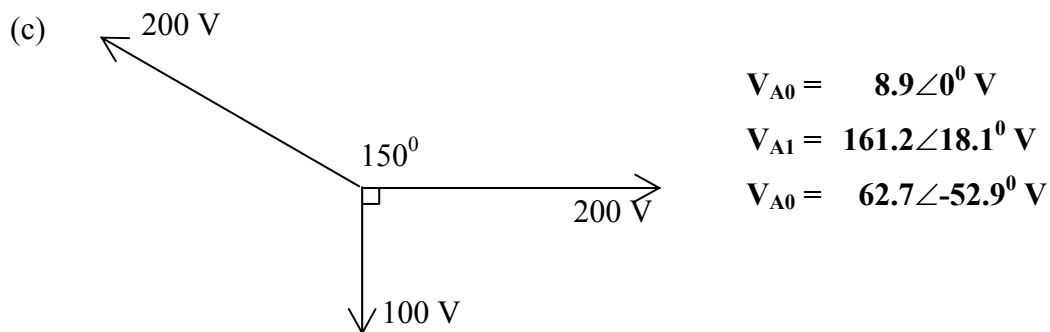5. (a) Phase voltage = $400/\sqrt{3} = 230.9\angle 0^\circ$ V, 200 mH $\rightarrow j 62.83 \Omega$
Line current = $230.9\angle 0^\circ / (100 + j 62.83) = 1.955\angle -32.10^\circ$ A
Load power factor = $\cos 32.1^\circ = 0.847$ lag
Active power supplied = $\sqrt{3} \times 400 \times 1.955 \times 0.847 = 1.147$ kW
- (b) $Q = \sqrt{3} \times 400 \times 1.955 \times \sin 32.1^\circ = 720.6$ var
 $Q_{\text{new}} = 1147 \times \tan 18.19^\circ = 377.0$ var
 Rating of each capacitor = $(720.6 - 377.0)/3 = 114.5$ var
 for delta connected capacitors ($V = 400$ V), **C = 2.28 μ F**



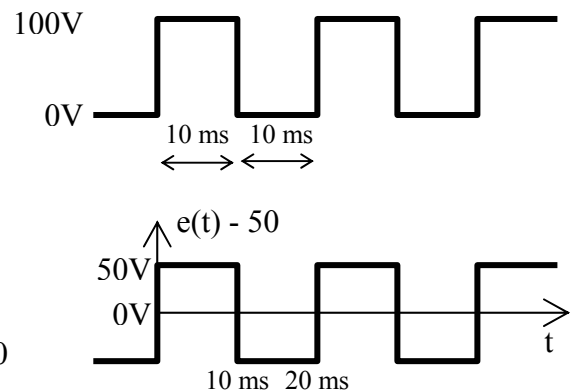6. (a) mean value = $a_0/2 = 100/2 = 50$ V
 Shift axis by 50 V as shown.
- $T = 20$ ms
 $e(t) - 50$ is an odd function.
 $\therefore a_n = 0$ for all $n \neq 0$
 b_n is the same for $e(t)$ and for $e(t) - 50$
 $b_n = 200/n\pi$
 $\therefore e(t) = 50 + 200/\pi [\sin 100\pi t + \frac{1}{3} \sin 300\pi t + \dots]$




- (b) **Peak value = 100 V**
average value = 50 V (rectified)
mean value = 50 V

$$\text{rms value} = \sqrt{\frac{1}{T} \int_0^{\frac{1}{2}T} 100^2 dt + \frac{1}{T} \int_{\frac{1}{2}T}^T 0^2 dt} = 70.7 \text{ V}$$

$$\text{form factor} = 70.7/50 = 1.414$$

- (c) $v(t) = \frac{10}{10 + j100n\pi \times 0.1} \cdot e(t)$

$$v(t) = 50 + 19.31 \sin(100\pi t - 72.34^\circ) + 2.24 \sin(300\pi t - 83.94^\circ) + \dots$$

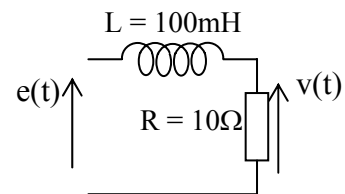




EE 201 - THEORY OF ELECTRICITY – Short Answers

7. (a) $E(s) = \frac{100}{s} \times \frac{1}{1 + e^{-0.01s}}$

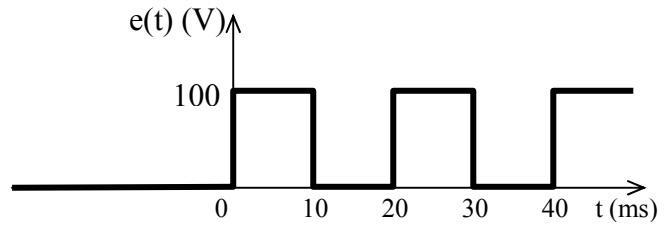(b) $\mathcal{L} [Ae^{-\alpha t}] = A/(s+\alpha)$



(c) $V(s) = \frac{100}{s} \times \frac{10}{10 + 0.1s}$

$v(t) = 100 (1 - e^{-100t})$ or $200 e^{-50t} \sinh 50t$

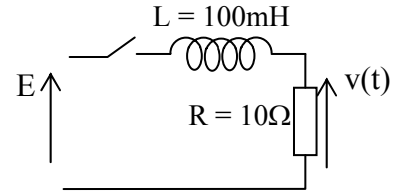


Figure Q7b