




EE 201 - THEORY OF ELECTRICITY – Short Answers

Level 2 Semester 1 Examination - March 2005

1. (a) volume = V , lamination thickness = t , alternating flux density peak value = B_m , frequency = f .
 total core loss = P , hysteresis loss P_h = eddy current loss $P_e = P/2$
 if changed to $0.6V$, $0.5t$, B_m , $1.2f$,
 new hysteresis loss = $P_h \times \text{volume ratio} \times \text{frequency ratio} = P/2 \times 0.6 \times 1.2 = 0.36 P$
 new eddy current loss = $P_e \times \text{volume ratio} \times \text{thickness ratio}^2 \times \text{frequency ratio}^2$
 = $P/2 \times 0.6 \times 0.5^2 \times 1.2^2 = 0.108 P$
 \therefore total loss in the core = $0.36 P + 0.108 P = \underline{\underline{0.468 P}}$


2 marks

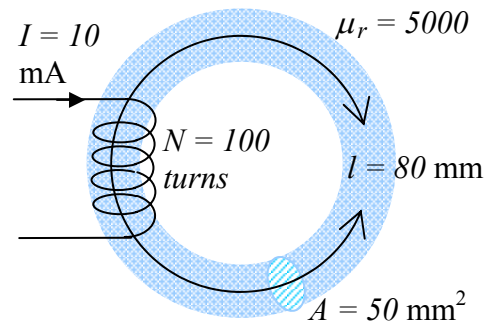(b) Reluctance $S = l/\mu A$
 $= \frac{80 \times 10^{-3}}{4\pi \times 10^{-7} \times 5000 \times 50 \times 10^{-6}} = \underline{\underline{254,648 H^{-1}}}$
 Inductance $L = N^2/S = 100^2/254648 = \underline{\underline{0.0393 H}}$
 $L I = N \phi$
 gives $\phi = L I/N = \frac{0.0393 \times 10 \times 10^{-3}}{100} = 3.93 \mu\text{Wb}$
 flux density $B = \phi/A = \frac{3.93 \times 10^{-6}}{50 \times 10^{-6}} = \underline{\underline{0.0786 T}}$



2 marks

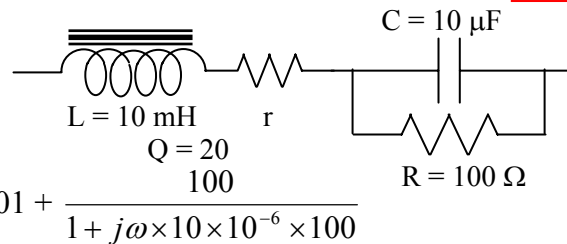(c) for the inductor, $Q = 20$ at 50 Hz
 $\therefore r = L\omega/Q = \frac{10 \times 10^{-3} \times 2\pi \times 50}{20} = 0.157 \Omega$
 i.e. $Z = r + j \omega L + \frac{R}{1 + j\omega CR} = 0.157 + j \omega 0.01 + \frac{100}{1 + j\omega \times 10 \times 10^{-6} \times 100}$



For unity power factor resonance condition, real part of Z must be zero.


$\therefore \omega 0.01 - j \frac{0.1\omega}{1^2 + 10^{-6} \omega^2} = 0$ gives $\omega = 0$, or $0.01 + 10^{-8} \omega^2 = 0.1$

Since $\omega \neq 0$, the resonant condition corresponds to $\omega = 3000 \text{ rad/s}$ or $f = \underline{\underline{477.5 \text{ Hz}}}$

Equivalent impedance at resonance = $0.157 + \frac{100}{1 + 10^{-6} \times 3000^2} = \underline{\underline{10.16 \Omega}}$

4 marks

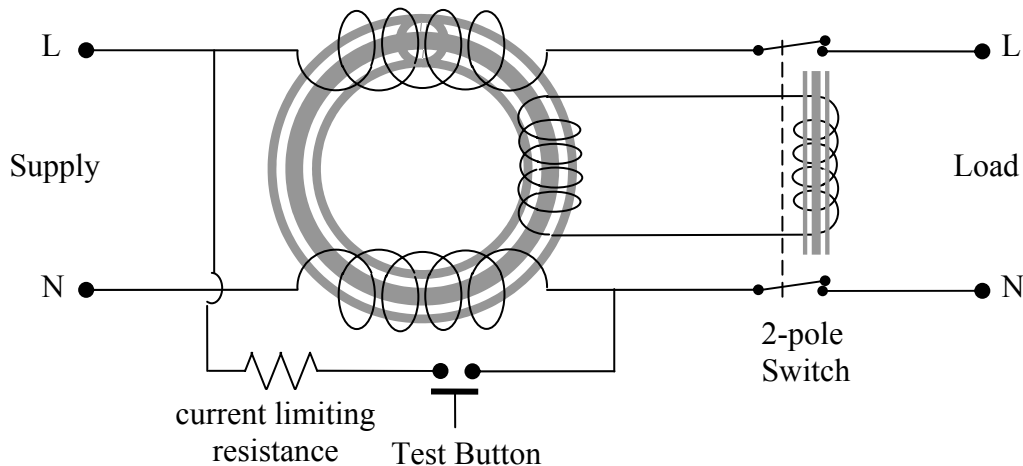- (d) Circuit diagram with brief explanation



2 marks

**EE 201 - THEORY OF ELECTRICITY – Short Answers**

2. (a) Applying Kirchoff's voltage law

$$E = R_1.i + (j\omega L_1.i - j\omega M.i) + (1/j\omega C).i + (j\omega L_2.i - j\omega M.i) + R_2.i$$

(b) $Z = E/i = R_1 + R_2 + j\omega L_1 + j\omega L_2 - j2\omega M + 1/j\omega C$

(c) $E = 230 \text{ V}$, $f = 50 \text{ Hz}$, $L_1 = 20 \text{ mH}$, $R_1 = 15 \Omega$, $R_2 = 10 \Omega$, $C = 50 \mu\text{F}$, $L_2 = 30 \text{ mH}$, $M = 20 \text{ mH}$

$$\omega = 2\pi \times 50 = 314.16 \text{ rad/s}$$

$$Z = 15 + 10 + j 314.16 \times (0.02 + 0.03 - 2 \times 0.02) - j / (314.16 \times 50 \times 10^{-6})$$

$$= 25 + j 3.142 - j 63.66 = \underline{25 - j 60.52 \Omega} \text{ or } \underline{65.48 \angle -67.6^\circ \Omega}$$

(d) $i = E/Z = 230 \angle 0^\circ / 65.48 \angle -67.6^\circ = \underline{3.51 \angle 67.6^\circ}$

(e) power factor = $\cos 67.6^\circ = \underline{0.38 \text{ lead}}$

$$\text{active power supplied} = 230 \times 3.51 \times 0.38 = \underline{307.6 \text{ W}}$$

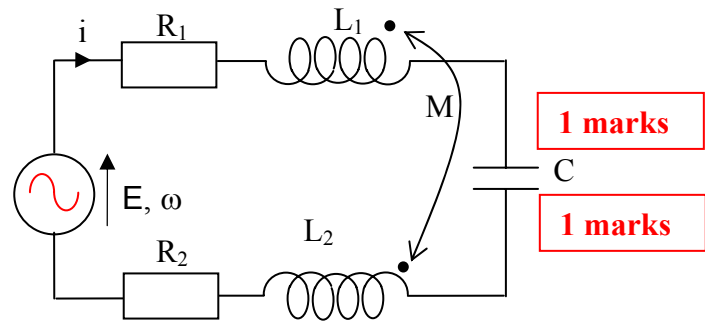


Figure Q2

1 marks


1 marks

2 marks

1 marks

1 marks

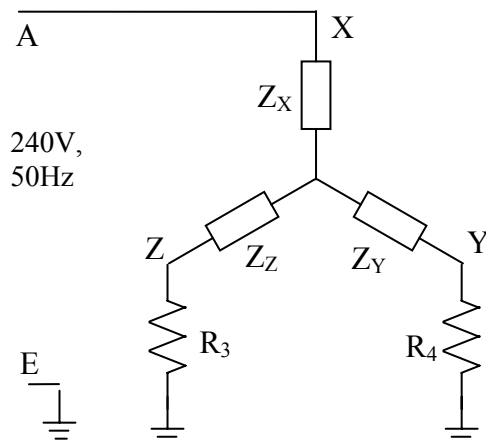3. (a) $L_1 = 100 \text{ mH}$, $C_2 = 50 \mu\text{F}$, $R = 10 \Omega$, $L = 30 \text{ mH}$, $R_3 = R_4 = 20 \Omega$



at 50 Hz,

$$L_1 \rightarrow j \times 100\pi \times 100 \times 10^{-3} = j31.416 \Omega,$$

$$L \rightarrow j \times 100\pi \times 30 \times 10^{-3} = j9.424 \Omega$$

$$C_2 \rightarrow 1/j \times 100\pi \times 50 \times 10^{-6} = -j 63.66 \Omega$$

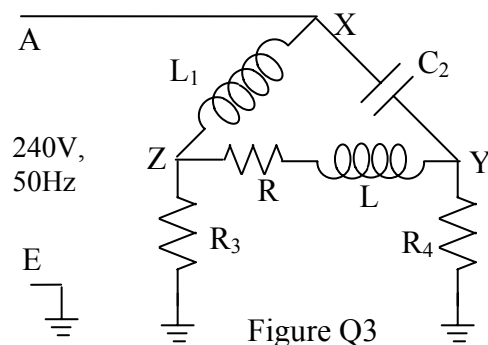


Figure Q3

Using the delta-star transformation theorem

$$Z_X = \frac{Z_{XY}Z_{XZ}}{Z_{XY} + Z_{XZ} + Z_{YZ}}, \text{ similarly } Z_Y, Z_Z$$

$$Z_X = \frac{(-j63.66)(j31.416)}{-j63.66 + 10 + j9.424 + j31.416} = \frac{2000}{10 - j22.82} = \frac{2000}{24.91 \angle -66.34^\circ} = \underline{80.29 \angle 66.3^\circ \Omega}$$

$$Z_Y = \frac{(-j63.66)(10 + j9.424)}{-j63.66 + 10 + j9.424 + j31.416} = \frac{63.66 \angle -90^\circ \times 13.74 \angle 43.30^\circ}{24.91 \angle -66.34^\circ} = \frac{874.68 \angle -46.70^\circ}{24.91 \angle -66.34^\circ}$$

$$= \underline{35.11 \angle 19.6^\circ \Omega}$$

$$Z_Z = \frac{(j31.416)(10 + j9.424)}{-j63.66 + 10 + j9.424 + j31.416} = \frac{31.416 \angle 90^\circ \times 13.74 \angle 43.30^\circ}{24.91 \angle -66.34^\circ} = \frac{431.66 \angle 133.30^\circ}{24.91 \angle -66.34^\circ}$$


$$= \underline{17.33 \angle 199.6^\circ \Omega}$$

3 marks



EE 201 - THEORY OF ELECTRICITY – Short Answers

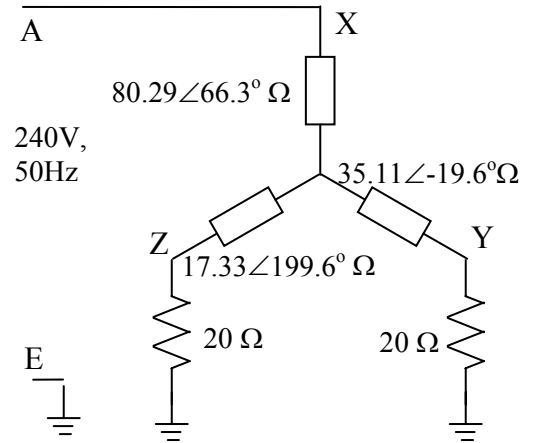
(b) Total impedance = $Z_X + (Z_Y + 20) // (Z_Z + 20)$
 $= 80.29 \angle 66.3^\circ + (35.11 \angle 19.6^\circ + 20) // (17.33 \angle 199.6^\circ + 20)$
 $= 32.28 + j 73.53 + (53.075 + j 11.777) // (3.674 - j 5.813)$
 $= 32.28 + j 73.53 + \frac{(53.075 + j 11.777) \times (3.674 - j 5.813)}{53.075 + j 11.777 + 3.674 - j 5.813}$
 $= 32.28 + j 73.53 + \frac{54.367 \angle 12.51^\circ \times 6.877 \angle -57.71^\circ}{57.062 \angle 6.00^\circ}$
 $= 32.28 + j 73.53 + \frac{373.88 \angle -45.20^\circ}{57.062 \angle 6.00^\circ}$
 $= 32.28 + j 73.53 + 6.552 \angle -51.20^\circ = 32.28 + j 73.53 + 4.11 - j 5.11 = 36.39 + j 68.42 = 77.50 \angle 62.0^\circ \Omega$



∴ current supplied = $240 \angle 0^\circ / 77.50 \angle 62.5^\circ = \underline{3.097 \angle -62.0^\circ \text{ A}}$


3 marks

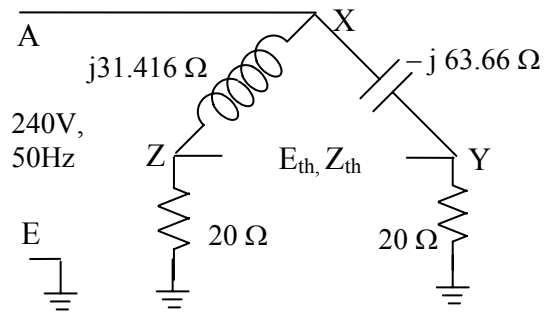(c)
 $Z_{th} = 20 // j31.416 + 20 // -j63.66$
 $= \frac{20 \times j31.416}{20 + j31.416} + \frac{20 \times (-j63.66)}{20 - j63.66}$
 $= \frac{628.32 \angle 90^\circ}{37.24 \angle 57.52^\circ} + \frac{1273.2 \angle -90^\circ}{66.73 \angle -72.56^\circ}$
 $= 16.872 \angle 32.48^\circ + 19.080 \angle -17.44^\circ$
 $= 14.233 + j 9.060 + 18.203 - j 5.718 = 32.436 + j 3.342 = 32.61 \angle 5.88^\circ \Omega$



$E_{th, ZY} = 240 \times \frac{20}{20 + j31.416} - 240 \times \frac{20}{20 - j63.66} = 240 \times \frac{20}{37.24 \angle 57.52^\circ} - 240 \times \frac{20}{66.73 \angle -72.56^\circ}$
 $= 128.89 \angle -57.52^\circ - 71.932 \angle 72.56^\circ = 69.215 - j 108.73 - 21.559 - j 68.625$
 $= 47.66 - j 177.36 = 183.65 \angle -74.96^\circ \text{ V}$

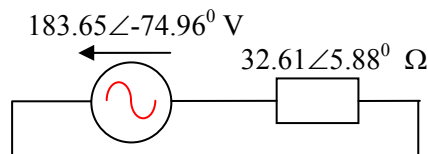Thus the Thevenin's equivalent circuit across ZY is





3 marks



EE 201 - THEORY OF ELECTRICITY – Short Answers

- 4 $I_s = 2\angle 0^\circ A$, $E = 100\angle 30^\circ V$, $\omega = 250$ rad/s
for both supplies, $R_1 = R_3 = R_4 = R_5 = 100 \Omega$,
 $R_2 = R_6 = 200 \Omega$

(a) Converted circuit is shown

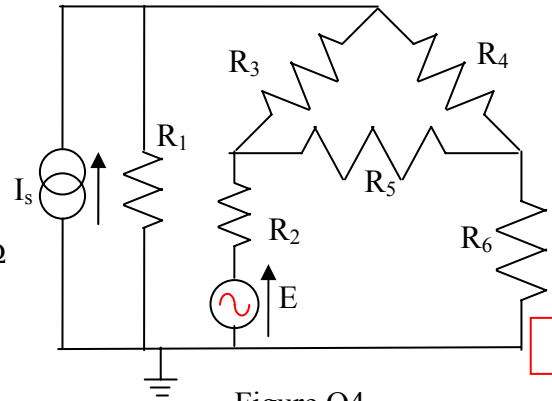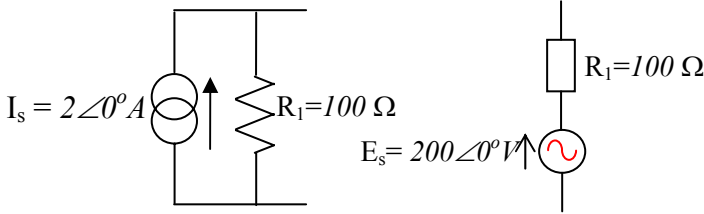

1 marks

Figure Q4

(b)

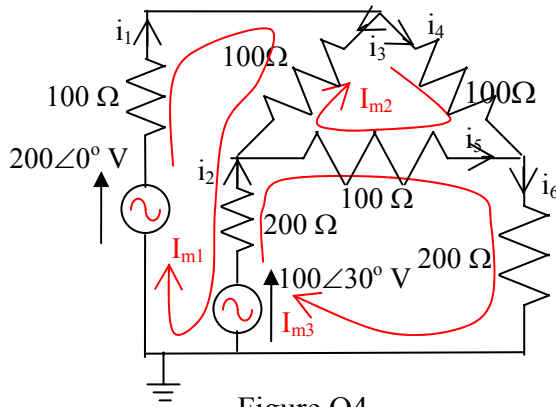


Figure Q4

branch impedance matrix

$$[Z_b] = \begin{bmatrix} 100 & 0 & 0 & 0 & 0 & 0 \\ 0 & 200 & 0 & 0 & 0 & 0 \\ 0 & 0 & 100 & 0 & 0 & 0 \\ 0 & 0 & 0 & 100 & 0 & 0 \\ 0 & 0 & 0 & 0 & 100 & 0 \\ 0 & 0 & 0 & 0 & 0 & 200 \end{bmatrix}$$

mesh-branch incidence matrix

$$= \begin{bmatrix} 1 & -1 & 1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 1 & -1 & 0 \\ 0 & 1 & 0 & 0 & 1 & 1 \end{bmatrix}$$

$$\text{mesh voltage source } [E_m] = \begin{bmatrix} 200\angle 0^\circ & -100\angle 30^\circ \\ 0 & 100\angle 30^\circ \end{bmatrix} = \begin{bmatrix} 113.40 - j50 \\ 0 \\ 100\angle 30^\circ \end{bmatrix} = \begin{bmatrix} 123.9\angle -23.8^\circ \\ 0 \\ 100\angle 30^\circ \end{bmatrix}$$

3 marks

(c) mesh impedance matrix $[Z_m]$

$$= \begin{bmatrix} 1 & -1 & 1 & 0 & 0 & 0 \\ 0 & 0 & -1 & 1 & -1 & 0 \\ 0 & 1 & 0 & 0 & 1 & 1 \end{bmatrix} \begin{bmatrix} 100 & 0 & 0 & 0 & 0 & 0 \\ 0 & 200 & 0 & 0 & 0 & 0 \\ 0 & 0 & 100 & 0 & 0 & 0 \\ 0 & 0 & 0 & 100 & 0 & 0 \\ 0 & 0 & 0 & 0 & 100 & 0 \\ 0 & 0 & 0 & 0 & 0 & 200 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ -1 & 0 & 1 \\ 1 & -1 & 0 \\ 0 & 1 & 0 \\ 0 & -1 & 1 \\ 0 & 0 & 1 \end{bmatrix}$$

$$\text{i.e. } [Z_m] = \begin{bmatrix} 400 & -100 & -200 \\ -100 & 300 & -100 \\ -200 & -100 & 500 \end{bmatrix}, [Z_m]^{-1} = \frac{1}{\Delta} \begin{bmatrix} 140000 & 70000 & 70000 \\ 70000 & 160000 & 60000 \\ 70000 & 60000 & 110000 \end{bmatrix}$$

3 marks

where $\Delta = 400 \times 140000 - 100 \times 70000 - 200 \times 70000 = 35000000$

$$(d) \text{ i.e. } \begin{bmatrix} 123.9\angle -23.8^\circ \\ 0 \\ 100\angle 30^\circ \end{bmatrix} = \begin{bmatrix} 400 & -100 & -200 \\ -100 & 300 & -100 \\ -200 & -100 & 500 \end{bmatrix} \begin{bmatrix} I_{m1} \\ I_{m2} \\ I_{m3} \end{bmatrix}$$

$$\text{i.e. } \begin{bmatrix} I_{m1} \\ I_{m2} \\ I_{m3} \end{bmatrix} = \begin{bmatrix} 0.004 & 0.002 & 0.002 \\ 0.002 & 0.00457 & 0.00171 \\ 0.002 & 0.00171 & 0.00314 \end{bmatrix} \begin{bmatrix} 123.9\angle -23.8^\circ \\ 0 \\ 100\angle 30^\circ \end{bmatrix}$$


$$\therefore \text{current in resistor } R_4 = i_4 = I_{m2} = (0.2267 - j 0.1000) + 0 + (0.1481 + j0.0855) = 0.3748 - j 0.0145 = \underline{0.375\angle -2.2^\circ A}$$

3 marks



EE 201 - THEORY OF ELECTRICITY – Short Answers

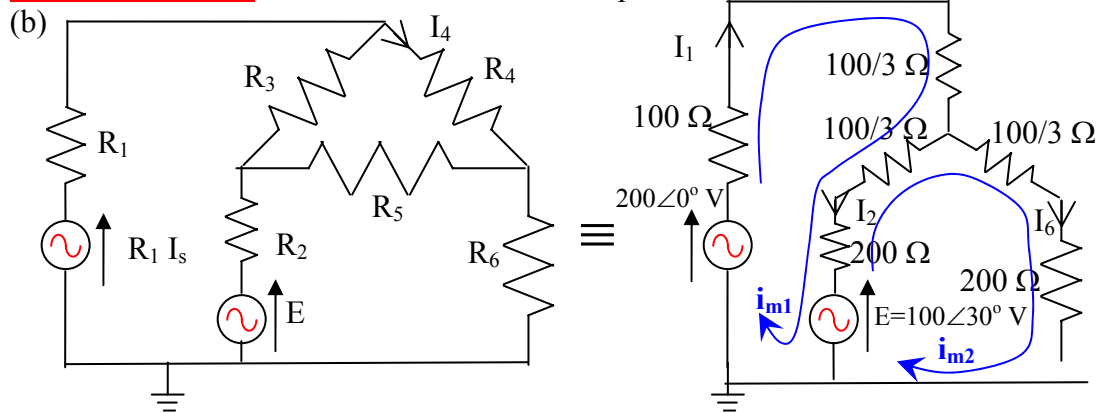Alternate Method which was considered acceptable



convert the delta connection of R_3 , R_4 and R_5 to an equivalent star as shown
write down branch impedance matrix and mesh-branch incidence matrix

$$[Z_b] = \begin{bmatrix} \frac{400}{3} & 0 & 0 \\ 0 & \frac{700}{3} & 0 \\ 0 & 0 & \frac{700}{3} \end{bmatrix}, [B]^T = \begin{bmatrix} 1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix} \text{ and}$$

$$\text{mesh voltage source } [E_m] = \begin{bmatrix} 200\angle 0^\circ & -100\angle 30^\circ \\ 100\angle 30^\circ & \end{bmatrix} = \begin{bmatrix} 113.40 - j50 \\ 100\angle 30^\circ \end{bmatrix} = \begin{bmatrix} 123.9\angle -23.8^\circ \\ 100\angle 30^\circ \end{bmatrix}$$

(c) mesh impedance matrix $[Z_m]$

$$= \begin{bmatrix} 1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} \frac{400}{3} & 0 & 0 \\ 0 & \frac{700}{3} & 0 \\ 0 & 0 & \frac{700}{3} \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & -1 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} \frac{1100}{3} & -\frac{700}{3} \\ -\frac{700}{3} & \frac{1400}{3} \end{bmatrix}$$

$$\Delta = 1100 \times 1400 / 9 - 700 \times 700 / 9 = 350000 / 3$$

$$[Z_m]^{-1} = \frac{1}{\Delta} \begin{bmatrix} \frac{1400}{3} & \frac{700}{3} \\ \frac{700}{3} & \frac{1100}{3} \end{bmatrix} = \begin{bmatrix} 0.004 & 0.002 \\ 0.002 & 0.00314 \end{bmatrix}$$

$$(d) \text{ i.e. } \begin{bmatrix} I_{m1} \\ I_{m2} \end{bmatrix} = \begin{bmatrix} 0.004 & 0.002 \\ 0.002 & 0.00314 \end{bmatrix} \begin{bmatrix} 123.9\angle -23.8^\circ \\ 100\angle 30^\circ \end{bmatrix} = \begin{bmatrix} 0.626 - j0.1 \\ 0.499 + j0.0573 \end{bmatrix}$$

The branch current I_4 may then be obtained from equating voltage drop across R_4

$$\text{i.e. } 100 I_4 = \frac{100}{3} i_{m1} + \frac{100}{3} I_{m2} = \frac{100}{3} (0.626 - j0.1 + 0.499 + j0.0573)$$

$$\text{i.e. } I_4 = 0.375 - j0.0142 = 0.375 \angle 2.2^\circ \text{ A}$$



EE 201 - THEORY OF ELECTRICITY – Short Answers

5

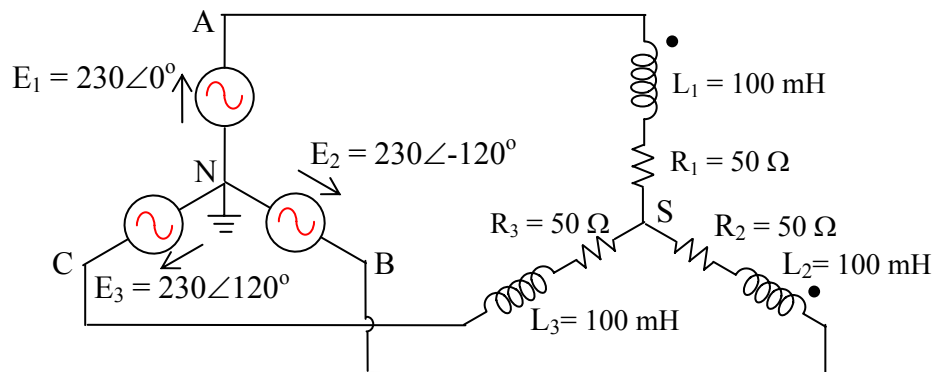


Figure Q5

- (a) If no mutual inductance exists, for a balanced source and balanced load, star point voltage is equal to the neutral voltage. Thus considering one phase only, $V = 400/\sqrt{3} = 230.9$ V

$$\text{phase A current} = \frac{230.9\angle 0^\circ}{50 + j0.10 \times 100\pi} = \frac{230.9\angle 0^\circ}{59.05\angle 32.14^\circ} = \underline{3.91\angle -32.14^\circ} \text{ A}$$

phase B and phase C currents are displaced by $\pm 120^\circ$

$$\text{phase B current} = \underline{3.91\angle -152.14^\circ} \text{ A}$$

$$\text{phase C current} = \underline{3.91\angle 87.86^\circ} \text{ A}$$


2 marks

- (b) power factor of load = $\cos 32.14^\circ = \underline{0.8467}$ lag

$$\text{active power supplied} = \sqrt{3} \times 400 \times 3.91 \times 0.8467 = \underline{2293} \text{ W (or } 3 \times 3.91^2 \times 50 = 2293 \text{ W)}$$

1 marks

- (c)

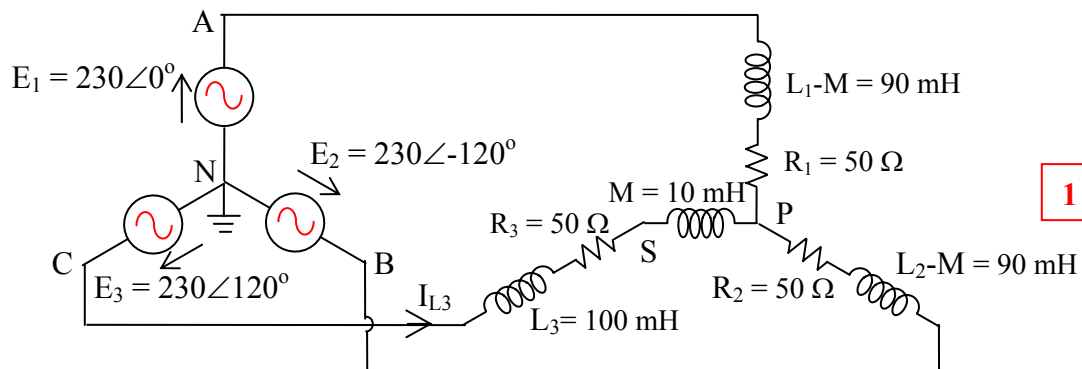

1 marks

- (d) $100 \text{ mH} \rightarrow 0.10 \times 100\pi = 31.416 \Omega$, $10 \text{ mH} \rightarrow 3.142 \Omega$, $90 \text{ mH} \rightarrow 28.274 \Omega$

Using Millmann's theorem

$$\begin{aligned} V_{PN} &= \frac{\sum Y.V}{\sum Y} = \frac{\frac{230.9\angle 0^\circ}{50 + j28.274} + \frac{230.9\angle -120^\circ}{50 + j28.274} + \frac{230.9\angle 120^\circ}{50 + j34.557}}{\frac{1}{50 + j28.274} + \frac{1}{50 + j28.274} + \frac{1}{50 + j34.557}} \\ &= \frac{\frac{230.9\angle 0^\circ}{57.440\angle 29.487^\circ} + \frac{230.9\angle -120^\circ}{57.440\angle 29.487^\circ} + \frac{230.9\angle 120^\circ}{60.780\angle 34.650^\circ}}{0.0174\angle -29.487^\circ + 0.0174\angle -29.487^\circ + 0.0165\angle -34.650^\circ} \end{aligned}$$



EE 201 - THEORY OF ELECTRICITY – Short Answers

$$\begin{aligned}
 &= \frac{4.020\angle -29.487^\circ + 4.020\angle -149.487^\circ + 3.799\angle 85.350^\circ}{0.0174\angle -29.487^\circ + 0.0174\angle -29.487^\circ + 0.0165\angle -34.650^\circ} \\
 &= \frac{3.500 - j1.979 - 3.463 - j2.041 + 0.3080 + j3.7865}{0.0151 - j0.00856 + 0.0151 - j0.00856 + 0.01357 - j0.00938} \\
 &= \frac{0.345 - j0.234}{0.0437 - j0.0265} = \frac{0.417\angle -34.14^\circ}{0.0511\angle -31.23^\circ} = \underline{8.16\angle -2.91^\circ \text{ V}}
 \end{aligned}$$

5 marks

$$\begin{aligned}
 I_{L3} &= (230.9\angle 120^\circ - 8.16\angle -2.91^\circ) \times 0.0165\angle -34.65^\circ = 0.309 + j3.797 - 0.1067 + j0.0821 \\
 &= 0.202 + j3.879 = \underline{3.884\angle 87.02^\circ \text{ A}}
 \end{aligned}$$

$$\begin{aligned}
 \text{(e) } V_{SN} &= V_{PN} + j\omega M \cdot I_{L3} = 8.16\angle -2.91^\circ + j100\pi \times 0.01 \times 3.884\angle 87.02^\circ \\
 &= 8.149 - j0.414 - 12.186 + j0.635 = -4.037 + j0.221 = \underline{4.04\angle 176.9^\circ \text{ V}}
 \end{aligned}$$

2 marks

6 (a) z-parameter matrix

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = 12Z // 4Z + 5Z = (12 \times 4 / 16 + 5)Z = 8Z$$

$$z_{22} = z_{11} = 8Z$$

when $I_2 = 0$, I_1 divides itself in the proportion of $12Z:4Z$ in the two branches

$$\therefore V_2 = V_1 - 8Z \times I_1 / 4 = 8Z \times I_1 - 8Z \times I_1 / 4 = 6Z \times I_1$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = 6Z, \text{ giving the z-parameter matrix as } \begin{bmatrix} 8Z & 6Z \\ 6Z & 8Z \end{bmatrix}$$

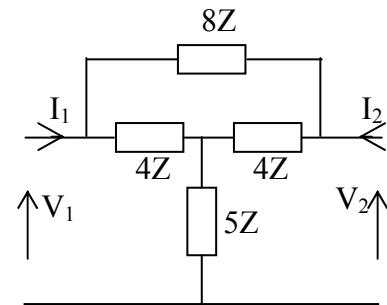


Figure Q6a

4 marks

(b)

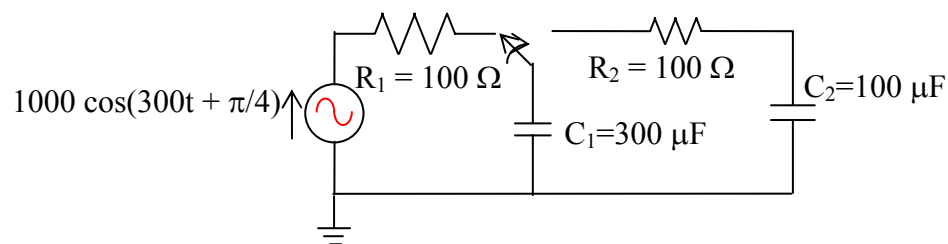


Figure Q6b

$$C_1 \rightarrow 1/j 300 \times 300 \times 10^{-6} = -j 11.1111 \Omega$$

$$\sqrt{2} \times \text{rms voltage across capacitor is } \frac{-j11.111 \times 1000}{100 - j11.11} = \frac{11111\angle -90^\circ}{100.615\angle -6.34^\circ} = 110.4\angle -83.66^\circ$$

$$\therefore \text{Voltage across capacitor is given by } 110.4 \cos(300t + 45^\circ - 83.66^\circ)$$

$$\text{or } v_c(t) = 110.4 \cos(300t - 38.66^\circ)$$

$$\therefore v_c(0) = 110.4 \cos 38.66^\circ = 86.2 \text{ V}$$

3 marks

**EE 201 - THEORY OF ELECTRICITY – Short Answers**

The transformed equivalent circuit is given by

Thus the circuit current can be calculated as


$$I(s) = \frac{\frac{86.2}{s}}{\frac{10000}{3s} + 100 + \frac{10000}{s}}$$

$$I(s) = \frac{258.6}{40000 + 300s}, \quad V(s) = \frac{1}{C_2 s} I(s) = \frac{10000}{s} \frac{258.6}{40000 + 300s} = \frac{8620}{s(s + 133.33)}$$


$$\text{i.e. } V(s) = \frac{64.65}{s} - \frac{64.65}{s + 133.33}$$

\therefore voltage across C_2 is given by $v(t) = 64.65(1 - e^{-133.33t})$

3 marks

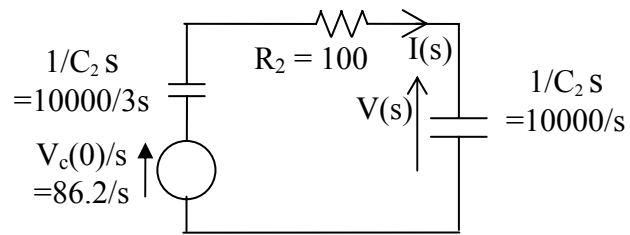


7

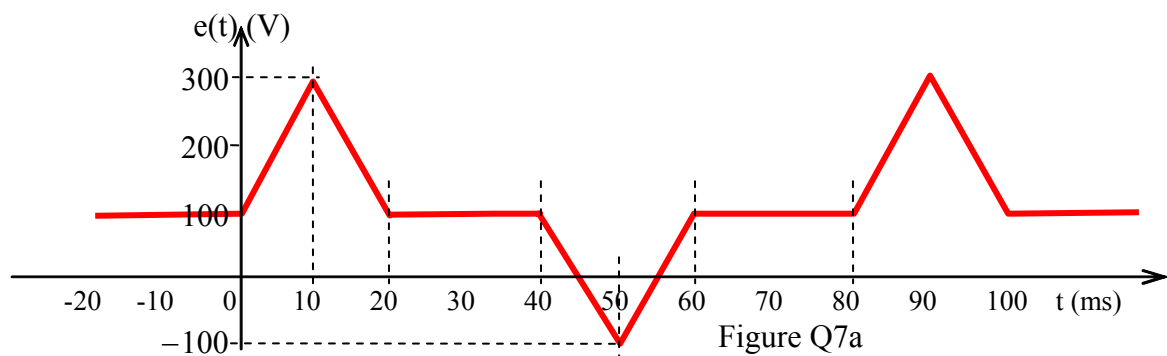

Period = 80 ms = 0.08 s, $\omega = 2\pi/0.08 = 25\pi$ rad/s

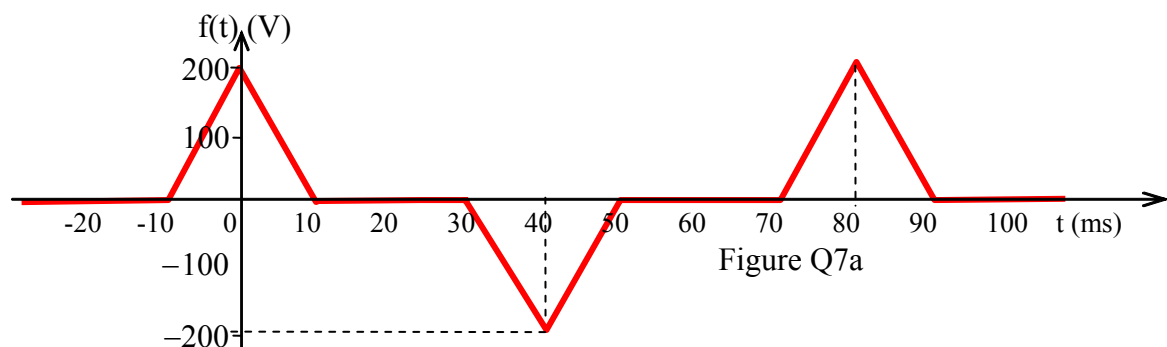(a) waveform may be shifted as follows to obtain a more symmetrical waveform



where $e(t) = f(t - 0.01) + 100$

$f(t) = A_0/2 + \sum A_n \cos n\omega t + B_n \sin n\omega t$

function $f(t)$ has mean value = 0 $\rightarrow A_0/2 = 0$

$f(t)$ is even $\rightarrow B_n = 0$ for all n

$f(t)$ has half-wave symmetry \rightarrow even harmonics = 0

$$\therefore A_n = 4 \times \frac{2}{T} \int_0^{0.02} f(t) \cdot \cos n\omega t \cdot dt = \frac{8}{0.08} \left[\int_0^{0.01} (200 - 20000t) \cdot \cos n25\pi t \cdot dt + \int_{0.01}^{0.02} 0 \cdot \cos n\omega t \cdot dt \right]$$



EE 201 - THEORY OF ELECTRICITY – Short Answers

$$\text{i.e. } A_n = 100 \times \left[(200 - 20000t) \cdot \frac{\sin n25\pi t}{n25\pi} \Big|_0^{0.01} + \int_0^{0.01} 20000 \cdot \frac{\sin n25\pi t}{n25\pi} dt \right]$$

$$= 100 \times [0 + (32/n^2\pi^2) \cdot (1 - \cos 0.25n\pi)]$$

$$A_1 = 100 \times [(32/\pi^2) \cdot (1 - \cos 0.25\pi)] = 94.96 \text{ V}$$

$$A_3 = 100 \times [(32/9\pi^2) \cdot (1 - \cos 0.75\pi)] = 61.5 \text{ V}$$

$$A_5 = \dots\dots\dots$$

$$\therefore f(t) = 94.96 \cos 25\pi t + 61.5 \cos 75\pi t + \dots$$

5 marks

$$\text{and } e(t) = f(t - 0.01) + 100 = 100 + 94.96 \cos (25\pi t - 0.25\pi) + 61.5 \cos (75\pi t - 0.75\pi) + \dots$$

(b) mean value = 100 V

$$\text{average value} = (200 \times 20 + 100 \times 20 + 50 \times 5 + 50 \times 10 + 50 \times 5 + 100 \times 20) / 80 = 112.5 \text{ V}$$

2 marks

$$\text{rms value} = \sqrt{100^2 + \frac{94.96^2}{2} + \frac{61.5^2}{2} + \dots} = 128 \text{ V (limited accuracy due to low terms)}$$

$$\text{form factor} = 128 / 112.5 = 1.14$$

(c) $I_n = E_n / (jn25\pi \times 0.2 + 1/jn25\pi \times 10 \times 10^{-6})$

$$I_n = \frac{jn25\pi}{10^5 - 125n^2\pi^2} E_n$$

there will be no d.c. current flow due to the capacitance

$$I_1 = \frac{j25\pi}{10^5 - 125\pi^2} E_1 = \frac{25\pi \angle 90^\circ}{10^5 - 125\pi^2} E_1 = 0.000795 \angle 90^\circ E_1$$

$$I_3 = \frac{j75\pi}{10^5 - 1125\pi^2} E_3 = 0.00265 \angle 90^\circ E_3$$

$$\therefore i(t) = 0.075 \cos (25\pi t - 0.25\pi) + 0.163 \cos (75\pi t - 0.75\pi) + \dots$$

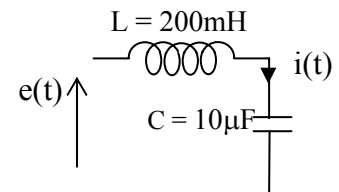


Figure Q7b

3 marks

(d) Laplace transform of the unit step $L[h(t)] = \int_0^\infty 1 \cdot e^{-st} dt = \frac{e^{-st}}{-s} \Big|_0^\infty = \frac{1}{s}$,

$$\text{and for unit ramp } r(t) = \int_0^\infty t \cdot e^{-st} dt = t \cdot \frac{e^{-st}}{-s} \Big|_0^\infty - \int_0^\infty \frac{e^{-st}}{-s} dt = -\frac{e^{-st}}{(-s)^2} \Big|_0^\infty = \frac{1}{s^2}$$

1 marks


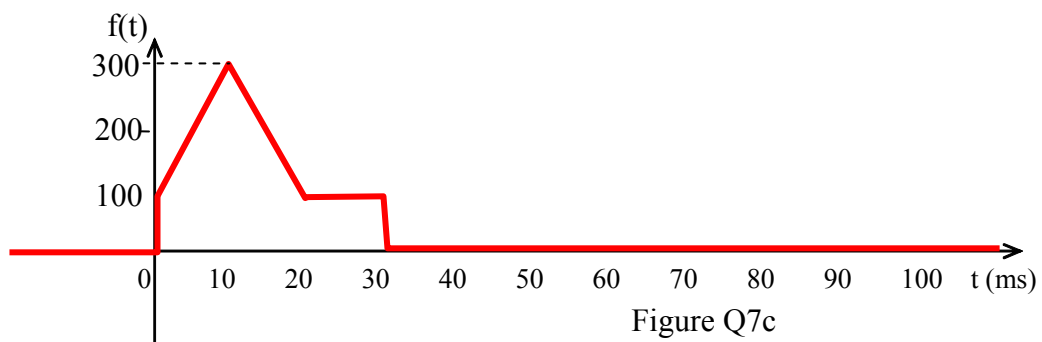


Figure Q7c


EE 201 - THEORY OF ELECTRICITY – Short Answers

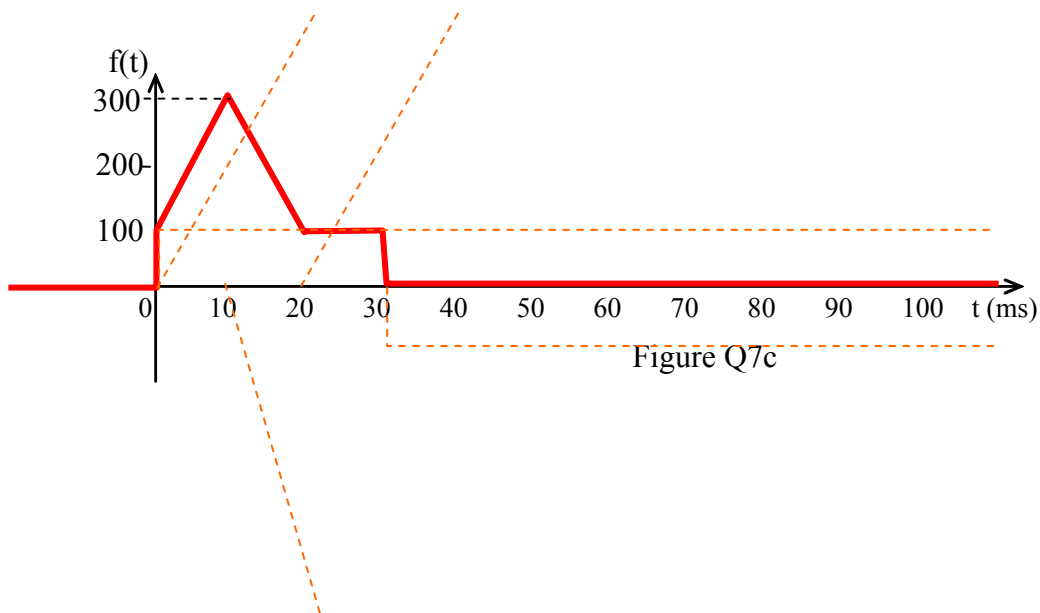(e) given waveform can be split into ramps and steps as follows



i.e. $f(t) = 100 h(t) + 20000 r(t) - 40000 r(t-0.01) + 20000 r(t-0.02) - 100 h(t-0.03)$

$$F(s) = \frac{100}{s} + \frac{20000}{s^2} - \frac{40000}{s^2} e^{-0.01s} + \frac{20000}{s^2} e^{-0.02s} - \frac{100}{s} e^{-0.03s}$$

3 marks