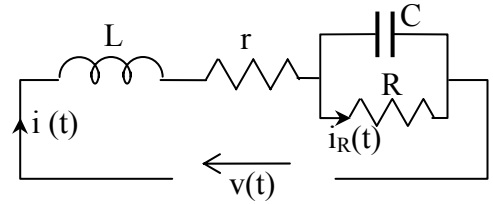




Level 2 Semester 2 Examination - March 2008

- 1 (a) For the circuit diagram shown on the right
 Using differential operator as $p = d/dt$



$$i(t) = \frac{1}{R \times \frac{1}{Cp} + Lp + r + \frac{R}{RCp + 1}} v(t) = \frac{v(t)}{Lp + r + \frac{R}{RCp + 1}}$$

$$= \frac{RCp + 1}{(Lp + r)(RCp + 1) + R} v(t)$$

$$\text{Also, } i_R(t) = \frac{\frac{1}{Cp}}{\frac{1}{Cp} + R} i(t) = \frac{1}{(Lp + r)(RCp + 1) + R} v(t) = \frac{1}{LRCp^2 + (L + rRC)p + r + R} v(t)$$


Giving the differential equation relationship as

$$v(t) = LRC \frac{d^2 i_R(t)}{dt^2} + (L + rRC) \frac{d i_R(t)}{dt} + (r + R) i_R(t) \quad [4 \text{ marks}]$$

- (b) For a sinusoidal voltage E the angular frequency ω , the differential operator p can be replaced by $j\omega$ to give the expression for the current. Thus

$$I_R = \frac{E}{(r + R - LRC\omega^2) + j\omega(L + rRC)} \quad [1 \text{ mark}]$$

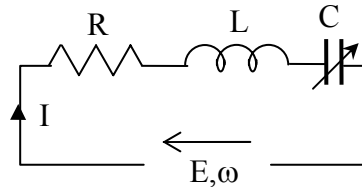- (c) (i) For the circuit shown, $Z = R + j\omega L + \frac{1}{j\omega C}$, and



$$\text{current } I = \frac{E}{R + j\omega L + \frac{1}{j\omega C}} \quad [1/2 \text{ mark}]$$

At resonance

(ii) $\omega = \frac{1}{\sqrt{LC_o}}$ giving $C_o = \frac{1}{L\omega^2}$ [1/2 mark]

(iii) $Q = \frac{L\omega}{R}$ [1/2 mark]

(iv) $I_{\max} = \frac{E}{R}$ [1/2 mark]

- (v) at the half-power points, power is half and the current $|I| = \frac{I_{\max}}{\sqrt{2}} = \frac{E}{\sqrt{2}R}$

$$\text{i.e. } \frac{E^2}{2R^2} = \frac{E^2}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}, \text{ giving } 2R^2 = R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2$$

$$\text{or } R^2 = \left(\omega L - \frac{1}{\omega C}\right)^2, \text{ or } \omega L - \frac{1}{\omega C} = \pm R \text{ giving } \frac{1}{\omega C} = \omega L \mp R$$




i.e. $\frac{1}{C} = \omega^2 L \mp R\omega = \frac{1}{C_o} \mp \frac{1}{C_o Q}$ giving $\mp \frac{1}{C_o Q} = \frac{1}{C} - \frac{1}{C_o}$ or $\frac{1}{Q} = \left| \frac{C_o - C}{C} \right|$
 $Q = \left| \frac{C}{C_o - C} \right|$ [3 marks]

2 (a) Consider the case of the inductances aiding each other

$$v_1 = L_1 \frac{di}{dt} + M \frac{di}{dt}, \quad v_2 = L_2 \frac{di}{dt} + M \frac{di}{dt}$$

[1 mark]

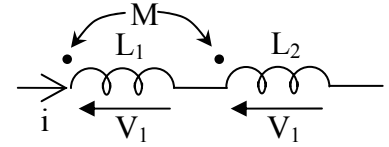

(for the opposing case, a negative sign would be associated with M)

(b) Total energy $W = \int v_1 \cdot i_1 \cdot dt + v_2 \cdot i_2 \cdot dt = \int \left(L_1 \frac{di}{dt} + M \frac{di}{dt} \right) i \cdot dt + \int \left(L_2 \frac{di}{dt} + M \frac{di}{dt} \right) i \cdot dt$
 $= \int (L_1 \cdot di + M \cdot di) i \cdot dt + (L_2 \cdot di + M \cdot di) i \cdot dt = \frac{1}{2}(L_1 + L_2 + 2M)i^2$ [½ mark]

Energy stored in equivalent inductance is $\frac{1}{2} L_{eq} i^2$

∴ Equivalent inductance = $L_1 + L_2 + 2M$ [½ mark]

(c) For the circuit shown in the figure on right

$$\text{Power factor of motor} = 0.8 = \frac{R}{\sqrt{R^2 + X^2}}$$


$$\text{so that } 0.64R^2 + 0.64X^2 = R^2$$

$$\text{giving } X = 0.75 R$$

[½ mark]

$$\text{Thus } I = \frac{200}{(R+1) + j(X+2)}$$

$$\text{and power delivered to load } P = |I|^2 R = \frac{200^2 \cdot R}{(R+1)^2 + (0.75R+2)^2}$$

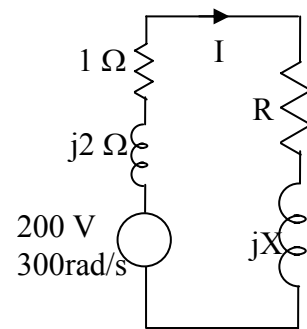

[½ mark]

$$\text{for maximum power transfer, } \frac{dP}{dR} = 0$$

$$\text{giving } [(R+1)^2 + (0.75R+2)^2] \cdot 1 - R \cdot [2(R+1) + 2(0.75R+2) \times 0.75] = 0$$

$$\text{i.e. } R^2 + 2R + 1 + (0.5625R^2 + 3R + 4 - 2R^2 - 2R - 2 \times 0.5625R^2 - 3R) = 0$$

$$\text{so that } 1.5625R^2 = 5$$

$$\text{i.e. } R = 1.78885 \Omega, X = 1.34164 \Omega$$

[1½ marks]

$$\therefore P_{\max} = \frac{200^2 \times 1.78885}{2.78885^2 + (0.75 \times 1.78885 + 2)^2} = 3777 \text{ W}$$

[1 mark]

$$I = \frac{200}{\sqrt{2.78885^2 + (0.75 \times 1.78885 + 2)^2}} = 45.95 \text{ A}$$

[½ marks]

Alternate Solution: $P_{\max} = 45.95^2 \times 1.78885 = 3777 \text{ W}$.

$$\text{voltage across load} = \sqrt{R^2 + X^2} \cdot I = \sqrt{1.78885^2 + 1.34164^2} \times 45.95 = 102.75 \text{ V}$$

[1 mark]



(d) Core loss $W = W_{\text{hyst}} + W_{\text{eddy}} = 100$ at 50 Hz, $t = 0.5$ mm

Hysteresis loss $W_{\text{hyst}} \propto B_m^{1.6} \cdot f$, $W_{\text{hyst}} = k_h \cdot f$ when B_m does not vary; and

Eddy current loss $W_{\text{eddy}} \propto B_m^2 \cdot f^2 \cdot t^2$, $W_{\text{eddy}} = k_e \cdot f^2 \cdot t^2$ when B_m does not vary

also at 50 Hz, $t = 0.5$ mm $W = 100 = k_h \times 50 + k_e \times 50^2 \times 0.5^2$

and at 60 Hz, $t = 0.4$ mm $W = 103.3 = k_h \times 60 + k_e \times 60^2 \times 0.4^2$

[1 mark]

eliminating k_h gives

$$1.2 \times 100 - 103.3 = 1.2 \times k_e \times 50^2 \times 0.5^2 - k_e \times 60^2 \times 0.4^2$$

re-arranging to leave k_e in the most convenient form to obtain desired results,


$$16.7 = k_e \times 50^2 \times 0.5^2 (1.2 - 1.2^2 \times 0.8^2)$$

[1 mark]

giving $W_{\text{eddy}} = k_e \times 50^2 \times 0.5^2 = 59.986$ W = 60 W

and $W_{\text{hyst}} = 100 - 60 = 40$ W

[1 mark]

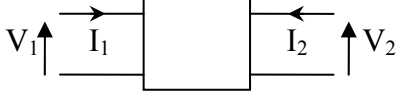3 (a) $[Y] = \begin{bmatrix} 0.0385 - j0.182 & -0.0385 + j0.192 \\ -0.0385 + j0.192 & 0.0385 - j0.182 \end{bmatrix} S$ 

for the ABCD matrix parameters, for the circuit shown

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}, \text{ giving } V_1 = A V_2 - B I_2 \quad \text{and} \quad I_1 = C V_2 - D I_2$$

and for the admittance matrix parameters, for the circuit shown

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix},$$

from which $I_2 = y_{21} V_1 + y_{22} V_2$

which may be re-arranged to give $V_1 = (I_2 - y_{22} V_2) / y_{21}$

by comparison of coefficients,

$$A = -\frac{y_{22}}{y_{21}} = \frac{0.0385 - j0.182}{0.0385 - j0.192} = \frac{0.1860 \angle -78.06^\circ}{0.1958 \angle -78.66^\circ} = 0.950 \angle 0.60^\circ$$

$$\text{and } B = -\frac{1}{y_{21}} = \frac{1}{0.0385 - j0.192} = \frac{1}{0.1958 \angle -78.66^\circ} = 5.107 \angle 78.66^\circ \Omega$$

Since the system is perfectly symmetric, $A = D$ and $A \cdot D - B \cdot C = 1$

$$\therefore D = 0.950 \angle 0.60^\circ$$


$$\text{and } C = \frac{A \cdot D - 1}{B} = \frac{0.950 \angle 0.60^\circ \times 0.950 \angle 0.60^\circ - 1}{5.107 \angle 78.66^\circ} = \frac{0.9025 + j0.0189 - 1}{5.107 \angle 78.66^\circ} = \frac{-0.0975 + j0.0189}{5.107 \angle 78.66^\circ}$$

$$\text{i.e. } C = \frac{-0.0975 + j0.0189}{5.107 \angle 78.66^\circ} = 0.0194 \angle 90.37^\circ S$$



Thus the ABCD matrix is given as $\begin{bmatrix} 0.950\angle 0.60^\circ & 5.107\angle 78.66^\circ \\ 0.0194\angle 90.37^\circ & 0.950\angle 0.60^\circ \end{bmatrix}$ [3 marks]

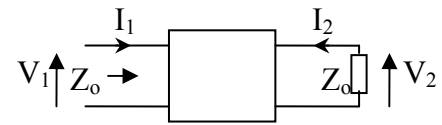(b) When loaded at port 2 with Z_o , $\frac{V_2}{-I_2} = Z_o$





Also at port 1 input impedance, $\frac{V_1}{I_1} = Z_o$

Thus, from the ABCD parameter matrix $\frac{V_1}{I_1} = Z_o = \frac{AV_2 - BI_2}{CV_2 - DI_2} = \frac{AZ_o + B}{CZ_o + D}$

i.e. $CZ_o^2 + DZ_o = AZ_o + B$

Since $A=D$, $CZ_o^2 = B$, giving $Z_o = \sqrt{\frac{B}{C}} = \sqrt{\frac{5.107\angle 78.66^\circ}{0.0194\angle 90.37^\circ}} = 16.22\angle -5.7^\circ$ [2 marks]

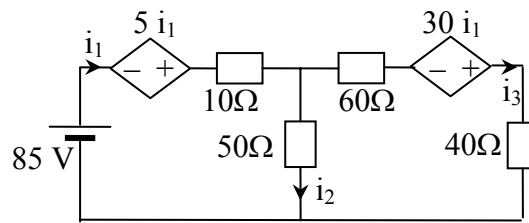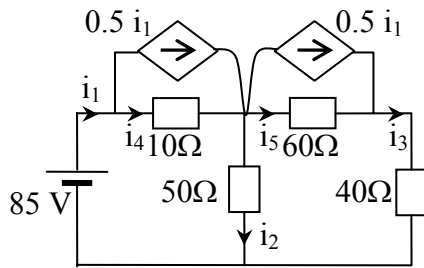(c) The current source can be distributed as shown and converted to voltage sources.



[2 marks]

(d) $85 + 5 i_1 = 10 i_1 + 50 i_2$

$30 i_1 = (60+40) (i_1 - i_2) - 50 i_2$

[1 mark]

(e) which may be reduced to

$5 i_1 + 50 i_2 = 85$ or $i_1 + 10 i_2 = 17$ and $15 i_2 = 7 i_1$

substitution gives $i_1 = 3$ A, $i_2 = 1.4$ A

and $i_3 = i_1 - i_2 = 1.6$ A, $i_4 = i_1 - 0.5i_1 = 1.5$ A, $i_5 = i_3 - 0.5i_1 = 0.1$ A


[2 mark]

4 (a) $E_{AB} + E_{BC} + E_{CA} = 0$

$E_{BC} = -E_{AB} - E_{CA} = -100\angle 0^\circ - 150\angle 90^\circ$

$= -100 - j150 = 180.28\angle 236.31^\circ$ [1 mark]

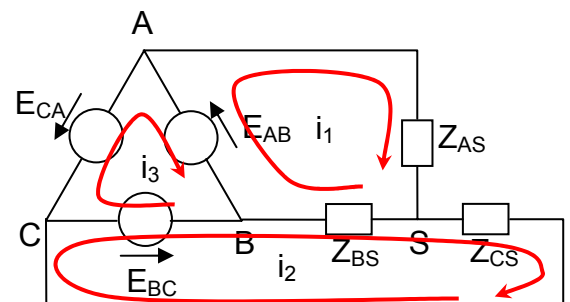(b) $[Z_m] = \begin{bmatrix} Z_{AS} + Z_{BS} & -Z_{BS} & 0 \\ -Z_{BS} & Z_{BS} + Z_{CS} & 0 \\ 0 & 0 & 0 \end{bmatrix}$, $[E_{gm}] = \begin{bmatrix} E_{AB} \\ E_{BC} \\ 0 \end{bmatrix}$



reduced equations eliminating zero column and zero row gives

$[Z_m] = \begin{bmatrix} Z_{AS} + Z_{BS} & -Z_{BS} \\ -Z_{BS} & Z_{BS} + Z_{CS} \end{bmatrix} = \begin{bmatrix} 50\angle 0^\circ + 50\angle 30^\circ & -50\angle 30^\circ \\ -50\angle 30^\circ & 50\angle 30^\circ + 50\angle 60^\circ \end{bmatrix}$



$$= \left[\begin{array}{c|c} 93.30 + j25 & -43.30 - j25 \\ \hline -43.30 - j25 & 68.30 + j68.30 \end{array} \right] \quad [1 \text{ mark}]$$

$$[E_{gm}] = \begin{bmatrix} E_{AB} \\ E_{BC} \end{bmatrix} = \begin{bmatrix} 100 \angle 0^\circ \\ 180.28 \angle 236.31^\circ \end{bmatrix} \quad [1 \text{ mark}]$$

$$(c) \begin{bmatrix} 100 \angle 0^\circ \\ 180.28 \angle 236.31^\circ \end{bmatrix} = \begin{bmatrix} 93.30 + j25 & -43.30 - j25 \\ -43.30 - j25 & 68.30 + j68.30 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 96.59 \angle 15^\circ & -50 \angle 30^\circ \\ -50 \angle 30^\circ & 96.59 \angle 45^\circ \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 96.59 \angle 15^\circ & -50 \angle 30^\circ \\ -50 \angle 30^\circ & 96.59 \angle 45^\circ \end{bmatrix}^{-1} \begin{bmatrix} 100 \angle 0^\circ \\ 180.28 \angle 236.31^\circ \end{bmatrix}$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \frac{1}{96.59^2 \angle 60^\circ - 50^2 \angle 60^\circ} \begin{bmatrix} 96.59 \angle 45^\circ & 50 \angle 30^\circ \\ 50 \angle 30^\circ & 96.59 \angle 15^\circ \end{bmatrix} \begin{bmatrix} 100 \angle 0^\circ \\ 180.28 \angle 236.31^\circ \end{bmatrix}$$

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \frac{1}{6829.6 \angle 60^\circ} \begin{bmatrix} 96.59 \angle 45^\circ & 50 \angle 30^\circ \\ 50 \angle 30^\circ & 96.59 \angle 15^\circ \end{bmatrix} \begin{bmatrix} 100 \angle 0^\circ \\ 180.28 \angle 236.31^\circ \end{bmatrix}$$

$$i_1 = 1.414 \angle -15^\circ + 1.3198 \angle 206.31^\circ = 1.366 - j 0.366 - 1.1831 - j 0.5850$$

$$I_{AS} = i_1 = 0.183 - j 0.951 = 0.968 \angle -79.1^\circ \text{ A}$$


$$i_2 = 0.7321 \angle -30^\circ + 2.5497 \angle 191.31^\circ = 0.6340 - j 0.3660 - 2.5 - j 0.5$$

$$I_{CS} = -i_2 = 1.866 - j 0.866 = 2.057 \angle -24.90^\circ$$

[3 marks]

$$(d) Y_{AB} = \frac{Y_{AS} \cdot Y_{BS}}{Y_{AS} + Y_{BS} + Y_{CS}}$$
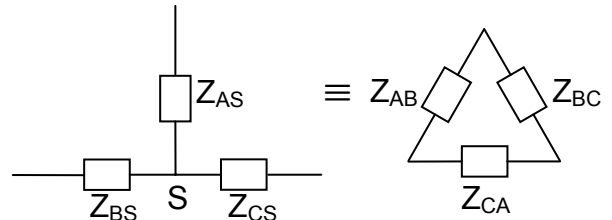
$$Y_{AB} = \frac{0.02 \angle 0^\circ \times 0.02 \angle -30^\circ}{0.02 \angle 0^\circ + 0.02 \angle -30^\circ + 0.02 \angle -60^\circ}$$



$$Y_{AB} = \frac{0.02 \angle -30^\circ}{1 + 0.866 - j0.5 + 0.5 - j0.866} = \frac{0.02 \angle -30^\circ}{2.366 - j1.366} = \frac{0.02 \angle -30^\circ}{2.732 \angle -30^\circ} = 0.00732 \angle 0^\circ$$

$$Y_{CA} = \frac{0.02 \angle -60^\circ \times 0.02 \angle 0^\circ}{0.02 \angle 0^\circ + 0.02 \angle -30^\circ + 0.02 \angle -60^\circ} = 0.00732 \angle -30^\circ$$

[2 marks]

$$(e) I_{AB} = 100 \angle 0^\circ \times 0.00732 \angle 0^\circ = 0.732 \angle 0^\circ$$

$$I_{CA} = 150 \angle 90^\circ \times 0.00732 \angle -30^\circ = 1.098 \angle 60^\circ$$

[1 mark]

$$(f) I_{AS} = I_{AB} - I_{AC} = 0.732 \angle 0^\circ - 1.098 \angle 60^\circ = 0.732 - 0.549 - j 0.951$$


$$= 0.183 - j 0.951 = 0.968 \angle -79.1^\circ$$

[1 mark]



5 (a) $P = \sqrt{3} V_L I_L \cos \phi$ 400 V, 50Hz
 $I_L = \frac{1500}{\sqrt{3} \times 400 \times 0.6} = 3.6084 A$  [1 mark]

(b) $Q = \sqrt{3} V_L I_L \sin \phi = P \tan \phi = 1500 \times \frac{0.8}{0.6} = 2000 \text{ var}$ [1 mark]

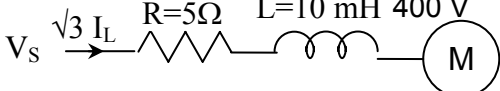(c) Using equivalent single phase circuit 
 $\sqrt{3} I_L = \sqrt{3} \times 3.6084 = 6.25 \angle -53.13^\circ$
 $V_S = 400 + 6.25 \angle -53.13^\circ \times (5 + j 10 \times 10^{-3} \times 100\pi) = 400 + 6.25 \angle -53.13^\circ \times 5.905 \angle 32.14^\circ$
 $= 400 + 36.906 \angle -21.0^\circ = 400 + 34.46 - j 13.21 = 434.66 \angle -1.74^\circ \text{ V}$ [2 marks]

(d) overall power factor at source = $\cos(-1.74^\circ + 53.13^\circ) = 0.624 \text{ lag}$ [1 mark]

(e) new power factor = 0.95 lag, $\phi_{\text{new}} = \cos^{-1}(0.95) = 18.19^\circ$
 new $Q = 1500 \tan 18.19^\circ = 493.0 \text{ var}$
 $Q \text{ required} = 2000 - 493 = 1507 \text{ var}$
 For 3 capacitors connected in delta, voltage = 400 V
 $3 \times 400^2 \times C \times 100\pi = 1507$
 $C = 9.994 \times 10^{-6} = 10 \mu\text{F}$ [2 marks]

(f) $I_A = 10 \angle 0^\circ \text{ A}$, $I_B = 10 \angle -120^\circ \text{ A}$ and $I_C = 50 \angle 90^\circ \text{ A}$

$$\begin{bmatrix} I_{A0} \\ I_{A1} \\ I_{A2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} I_A \\ I_B \\ I_C \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} 10 \angle 0^\circ \\ 10 \angle -120^\circ \\ 50 \angle 90^\circ \end{bmatrix}$$

$I_{A0} = \frac{1}{3} (10 \angle 0^\circ + 10 \angle -120^\circ + 50 \angle 90^\circ) = \frac{1}{3} (10 - 5 - j8.66 + j50) = \frac{1}{3} (5 + j41.34)$

i.e. $I_{A0} = I_{B0} = I_{C0} = 13.88 \angle 83.10^\circ \text{ A}$ [1 mark]

$I_{A1} = \frac{1}{3} (10 \angle 0^\circ + 10 \angle -120^\circ \times 1 \angle 120^\circ + 50 \angle 90^\circ \times 1 \angle -120^\circ) = \frac{1}{3} (10 + 10 + 43.3 - j25) = \frac{1}{3} (63.3 - j25)$


$I_{A1} = 22.69 \angle -21.55^\circ \text{ A}$, $I_{B1} = 22.69 \angle -141.55^\circ \text{ A}$, $I_{C1} = 22.69 \angle 98.45^\circ \text{ A}$ [1 mark]

$I_{A2} = \frac{1}{3} (10 \angle 0^\circ + 10 \angle -120^\circ \times 1 \angle -120^\circ + 50 \angle 90^\circ \times 1 \angle 120^\circ) = \frac{1}{3} (10 - 5 + j8.66 - 43.3 - j25)$
 $= \frac{1}{3} (-38.3 - j16.34)$

$I_{A2} = 18.85 \angle 203.10^\circ \text{ A}$, $I_{B2} = 18.85 \angle -36.90^\circ \text{ A}$, $I_{C2} = 18.85 \angle 83.10^\circ \text{ A}$ [1 mark]

6 (a) Period of waveform = $6T$, $\omega_0 \cdot 6T = 2\pi$ so that $\omega_0 = \frac{\pi}{3T}$ [1 mark]

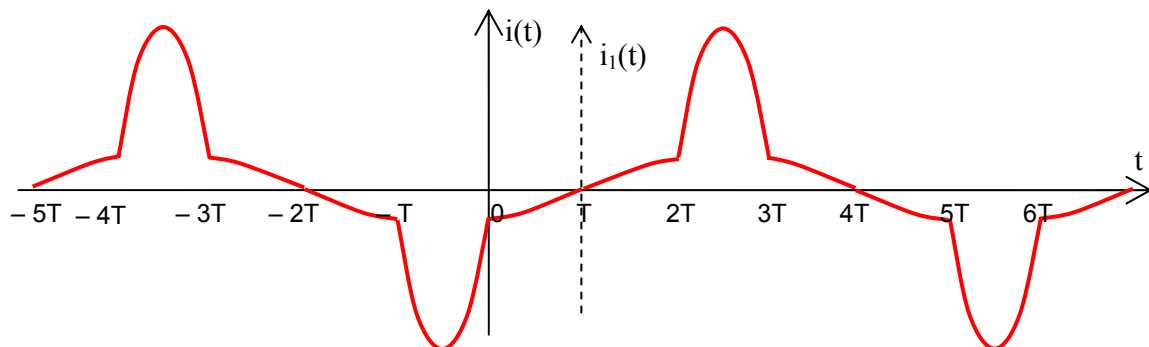(b) The y-axis may be shifted by T so that the new waveform $i_1(t)$ becomes an odd waveform.



$i_1(t) = i(t - T)$



The waveform $i_1(t)$ has both odd symmetry as well as half wave symmetry. Also it is made out of the waveforms $-\cos \omega_0 t$ throughout and an additional periodic waveform superposed $i_2(t)$.

$$\begin{aligned} \text{Thus } i_2(t) &= 0 & 0 \leq t \leq T \\ i_2(t) &= -4 \sin 3\omega_0 t & T \leq t \leq \frac{3}{2} T \end{aligned}$$

Thus for $i_2(t)$, the Fourier coefficients are given as

$$A_0 = 0 \text{ (since mean value} = 0), A_n = 0 \text{ (since odd function),}$$

[1½ marks]

$$B_n = 0 \text{ for even } n \text{ (since half wave symmetry)}$$

Thus for odd n ,

$$\begin{aligned} B_n &= 4 \times \frac{2}{T} \int_T^{\frac{3T}{2}} -4 \sin 3\omega_0 t \cdot \sin n\omega_0 t dt = -\frac{16}{T} \int_T^{\frac{3T}{2}} [\cos(n-3)\omega_0 t - \cos(n+3)\omega_0 t] dt \\ B_n &= -\frac{16}{T} \left[\frac{\sin(n-3)\omega_0 t}{(n-3)\omega_0} - \frac{\sin(n+3)\omega_0 t}{(n+3)\omega_0} \right]_T^{\frac{3T}{2}} \\ &= -\frac{16}{\omega_0 T} \left[\frac{\sin \frac{(n-3)\omega_0 3T}{2} - \sin(n-3)\omega_0 T}{n-3} - \frac{\sin \frac{(n+3)\omega_0 3T}{2} - \sin(n+3)\omega_0 T}{n+3} \right] \\ &= -\frac{48}{\pi} \left[\frac{\sin(n-3)\frac{\pi}{2} - \sin(n-3)\frac{\pi}{3}}{n-3} - \frac{\sin(n+3)\frac{\pi}{2} - \sin(n+3)\frac{\pi}{3}}{n+3} \right] \\ &= \frac{48}{\pi} \left[\frac{\sin(n-3)\frac{\pi}{3} - \sin(n+3)\frac{\pi}{3}}{n-3} \right], \text{ since } n \text{ is odd} \end{aligned}$$

[2 marks]

$$\text{Thus } B_1 = \frac{48}{\pi} \left[\frac{\sin \frac{2\pi}{3}}{2} - \frac{\sin \frac{4\pi}{3}}{4} \right] = \frac{18\sqrt{3}}{\pi} = 9.924$$

B_3 cannot be calculated from the general expression since $(n-3) = 0$.

$$\text{Thus } B_3 = 4 \times \frac{2}{T} \int_T^{\frac{3T}{2}} -4 \sin 3\omega_0 t \cdot \sin 3\omega_0 t dt = \frac{16}{T} \int_T^{\frac{3T}{2}} [\cos 6\omega_0 t - 1] dt = \frac{16}{T} \left[\frac{\sin 6\omega_0 t}{6\omega_0} - t \right]_T^{\frac{3T}{2}}$$

$$\text{i.e. } B_3 = \frac{16}{2\pi} [\sin 9\omega_0 T - \sin 6\omega_0 T - 9\omega_0 T + 6\omega_0 T] = -8$$

$$\text{and } B_5 = \frac{48}{\pi} \left[\frac{\sin \frac{2\pi}{3}}{2} - \frac{\sin \frac{8\pi}{3}}{8} \right] = \frac{18\sqrt{3}}{\pi}$$

[1½ marks]



Thus the Fourier series of the original waveform is

$$i(t) = -\cos \omega_0 t + 9.924 \sin \omega_0(t+T) - 8 \sin 3\omega_0(t+T) + 9.924 \sin 5\omega_0(t+T) + \dots \quad [1 \text{ mark}]$$

$$i(t) = -\cos \omega_0 t + 9.924 \times \cos(60^\circ) \sin \omega_0 t + 9.924 \times \sin(60^\circ) \cos \omega_0 t - 8 \sin(3\omega_0 t + 180^\circ) + 9.924 \sin(5\omega_0 t + 300^\circ) + \dots$$

$$i(t) = 8.808 \sin(\omega_0 t + 33.16^\circ) + 8 \sin 3\omega_0 t + 9.924 \sin(5\omega_0 t + 300^\circ) + \dots \quad [1 \text{ mark}]$$

(c) If the current is supplied from a source $100 \sin \omega_0 t$ with internal resistance 1Ω ,



Terminal voltage $v(t) = e(t) - R \cdot i(t)$

$$v(t) = 100 \sin \omega_0 t - 8.808 \sin(\omega_0 t + 33.16^\circ) - 8 \sin 3\omega_0 t - 9.924 \sin(5\omega_0 t + 300^\circ) + \dots$$

$$= 92.63 \sin \omega_0 t - 4.82 \cos \omega_0 t - 8 \sin 3\omega_0 t - 9.924 \sin(5\omega_0 t + 300^\circ) + \dots$$

$$= 92.76 \sin(\omega_0 t - 0.12^\circ) - 8 \sin 3\omega_0 t - 9.924 \sin(5\omega_0 t + 300^\circ) + \dots \quad [2 \text{ marks}]$$

7 (a)

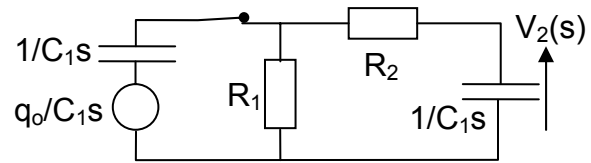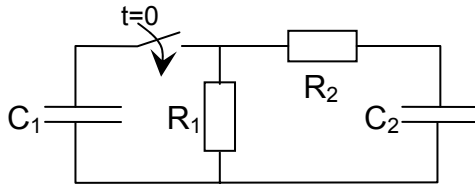

The given circuit has the Laplace Transformed circuit shown.

[1 mark]

$$(b) \quad V_2(s) = \frac{\frac{1}{C_2 s}}{R_2 + \frac{1}{C_2 s}} \cdot \frac{q_0}{C_1 s} \cdot \frac{R_1 \parallel \left(R_2 + \frac{1}{C_2 s}\right)}{\frac{1}{C_1 s} + R_1 \parallel \left(R_2 + \frac{1}{C_2 s}\right)} = \frac{1}{R_2 C_2 s + 1} \cdot \frac{q_0}{C_1 s} \cdot \frac{R_1 \cdot \left(R_2 + \frac{1}{C_2 s}\right)}{R_1 + R_2 + \frac{1}{C_2 s}}$$

$$= \frac{1}{R_2 C_2 s + 1} \cdot \frac{q_0}{C_1 s} \cdot \frac{\frac{1}{C_1 s} + \frac{R_1 \cdot \left(R_2 + \frac{1}{C_2 s}\right)}{R_1 + R_2 + \frac{1}{C_2 s}}}{\frac{1}{C_1 s} + \frac{R_1 \cdot \left(R_2 + \frac{1}{C_2 s}\right)}{R_1 + R_2 + \frac{1}{C_2 s}}}$$

$$= \frac{1}{R_2 C_2 s + 1} \cdot \frac{q_0}{C_1 s} \cdot \frac{\frac{R_1 \cdot (R_2 C_2 s + 1)}{(R_1 + R_2) C_2 s + 1}}{\frac{1}{C_1 s} + \frac{R_1 \cdot (R_2 C_2 s + 1)}{(R_1 + R_2) C_2 s + 1}} = q_0 \cdot \frac{R_1}{(R_1 + R_2) C_2 s + 1 + R_1 C_1 s \cdot (R_2 C_2 s + 1)}$$

$$V_2(s) = \frac{q_0 \cdot R_1}{R_1 C_1 R_2 C_2 s^2 + (R_1 C_2 + R_2 C_2 + R_1 C_1) s + 1}$$

[3 marks]

(c) $C_1 = 90 \text{ nF}$, $C_2 = 10 \text{ nF}$, $q_0 = 0.0225 \text{ C}$, $R_1 = 1 \text{ k}\Omega$ and $R_2 = 100 \Omega$

$$V_2(s) = \frac{0.0225 \times 1000}{1000 \times 90 \times 10^{-9} \times 100 \times 10 \times 10^{-9} s^2 + (10 \times 10^{-6} + 1 \times 10^{-6} + 90 \times 10^{-6}) s + 1}$$

$$\text{i.e. } V_2(s) = \frac{22.5}{90 \times 10^{-12} s^2 + 101 \times 10^{-6} s + 1} = \frac{0.25 \times 10^{12}}{s^2 + 1.1222 \times 10^6 s + 0.011111 \times 10^{12}}$$




$$V_2(s) = \frac{0.25 \times 10^{12}}{(s + 1.11223 \times 10^6)(s + 0.009989 \times 10^6)}$$

$$V_2(s) = \frac{0.25 \times 10^{12}}{1.1022 \times 10^6} \left[\frac{1}{(s + 0.009989 \times 10^6)} - \frac{1}{(s + 1.11223 \times 10^6)} \right]$$

$$v_2(t) = 227 (e^{-0.01t} - e^{-1.112t}) \text{ kV with } t \text{ in } \mu\text{s}$$

[3 marks]

(d) Sketch of waveform is shown

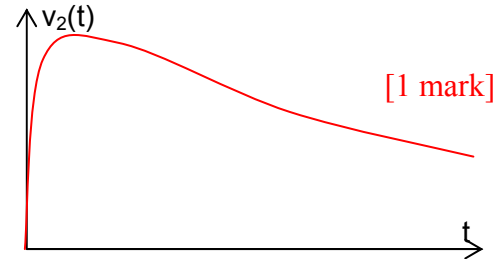

[1 mark]

(e) for maximum value, $dv/dt = 0$

$$\text{i.e. } 0.01e^{-0.01t} = 1.112e^{-1.112t}$$

$$e^{-1.102t} = 0.0899$$

$$t = 2.186 \mu\text{s}$$

$$\text{peak value} = 227 (e^{-0.01 \times 2.186} - e^{-1.112 \times 2.186})$$

$$= 227 (0.978 - 0.088) = 202 \text{ kV}$$

[2 marks]