



EE 201 - THEORY OF ELECTRICITY – Short Answers

Level 2 Semester 1 Examination - September 2005

1. (a) When parallel resonance occurs, current becomes a minimum. It is easily seen that $\omega L = 1/\omega C$ to give an infinite impedance

$$L = \frac{1}{\omega^2 C} = \frac{1}{1000^2 * 10 \times 10^{-6}} = 0.1 \text{ H} = \underline{\underline{100 \text{ mH}}}$$

Current at resonance = 0 A

- (b) if $L = 50 \text{ mH}$

$$j\omega L = j 1000 \times 50 \times 10^{-3} = j 50 \Omega$$

$$1/j\omega C = 1/j 1000 \times 10 \times 10^{-6} = -j 100 \Omega$$

$$\text{impedance of L and C in parallel} = \frac{j50 \times (-j100)}{j50 - j100} = j100 \Omega$$

$$\therefore \text{total impedance of circuit} = 20 + j 100 \Omega = 101.98 \angle 78.69^\circ \Omega$$

$$\therefore I = 200 \angle 0^\circ / 101.98 \angle 78.69^\circ = \underline{\underline{1.961 \angle -78.69^\circ \text{ A}}}$$


$$I_L = 1.961 \angle -78.69^\circ \times (-j100) / (j50 - j100) = \underline{\underline{3.922 \angle -78.69^\circ \text{ A}}}$$

$$I_C = 1.961 \angle -78.69^\circ - 3.922 \angle -78.69^\circ = -1.961 \angle -78.69^\circ = \underline{\underline{1.961 \angle 101.31^\circ \text{ A}}}$$

$$V_r = 20 I = \underline{\underline{39.22 \angle -78.69^\circ \text{ V}}}$$

$$V_L = V_C = j\omega L \cdot I_L = j 50 \times 3.922 \angle -78.69^\circ = \underline{\underline{196.1 \angle 11.31^\circ \text{ V}}}$$

- (c)

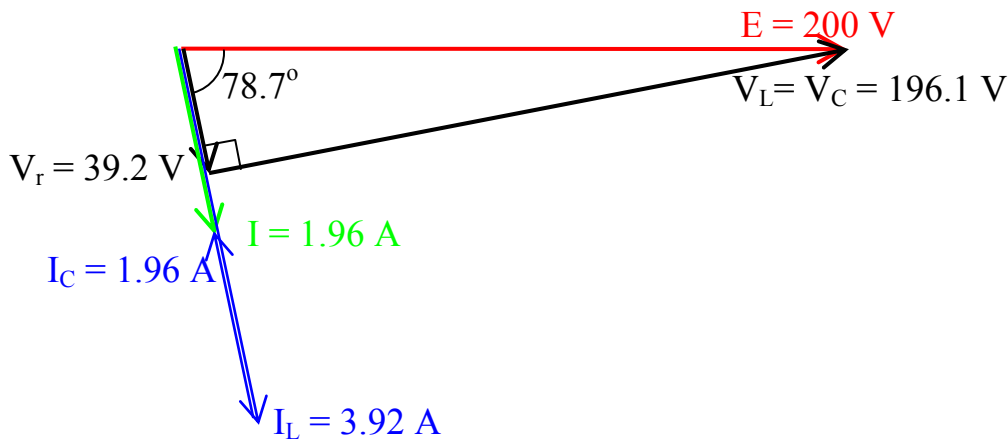

1 mark
1 mark

1 mark

2 marks

2 marks

- (d) $e(t) = 282.8 \cos 1000 t$ corresponds to an rms value of 100 V and phase angle of 0 as in section (b). Thus


$$i_L(t) = \sqrt{2} \times 3.922 \cos (1000t - 78.69^\circ),$$

$$i_L(1\text{ms}) = \sqrt{2} \times 3.922 \cos(57.30^\circ - 78.69^\circ) = \underline{\underline{5.16 \text{ A}}}$$

$$v_C(t) = \sqrt{2} \times 196.1 \cos (1000t + 11.31^\circ),$$

$$v_C(1\text{ms}) = \sqrt{2} \times 196.1 \cos(57.30^\circ + 11.31^\circ) = \underline{\underline{101.1 \text{ V}}}$$

2 marks

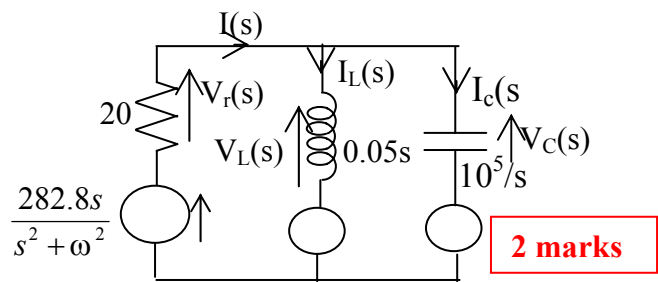


2 marks



EE 201 - THEORY OF ELECTRICITY – Short Answers

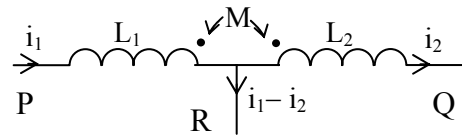2. (a) Consider the two coupled coils on two arms PR and QR of a T-junction as shown with currents i_1 and i_2 flowing in them and a current $(i_1 - i_2)$ flowing in the common branch.



Since the coils are wound in opposition as indicated by the dots, applying Kirchoff's voltage law between PR, and then again between RQ,

$$V_{PR} = L_1 p i_1 - M p i_2 \quad \text{and}$$

$$\text{and } V_{RQ} = L_2 p i_2 - M p i_1$$

If a non-coupled equivalent circuit is to be obtained, voltage drops in a branch should only correspond to currents in its own branch. So re-writing



$$V_{PR} = (L_1 - M) p i_1 + M p (i_1 - i_2)$$

$$\text{and } V_{RQ} = (L_2 - M) p i_2 + M p (i_1 - i_2)$$

These two equations would be satisfied with

$$L_A = L_1 - M, L_B = L_2 - M, \text{ and } L_m = M$$

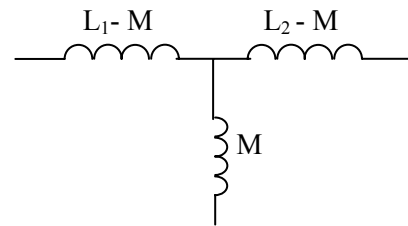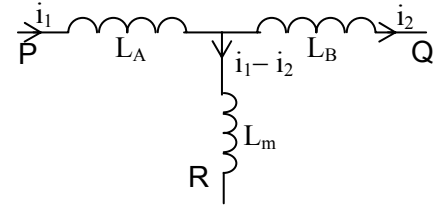This transformation will be valid, independent of what the directions marked for the currents in the diagrams.



2 marks

- (b)


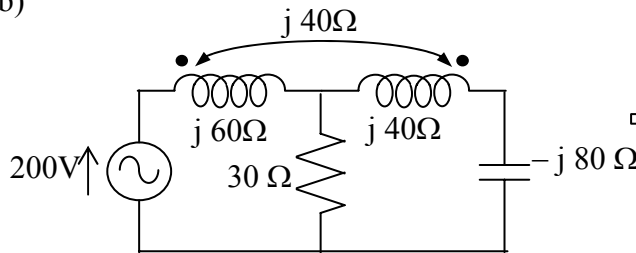


Figure Q2b

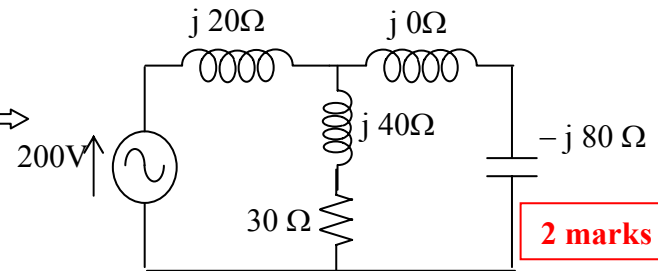

2 marks

- (c) For Thevenin's equivalent circuit,


Thevenin's voltage across 30 Ω

$$= 200 \times \frac{-j80}{j20 - j80} = 266.7 \angle 0^\circ \text{ V}$$

Thevenin's impedance = $j40 + j20 // (-j80)$

$$= j40 + \frac{j20 \times (-j80)}{j20 - j80} = j66.67 \Omega$$

Thevenin's equivalent circuit is

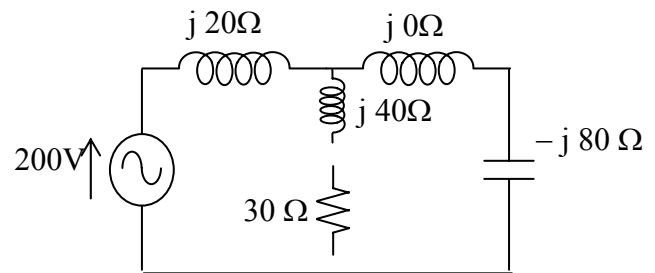


3 marks

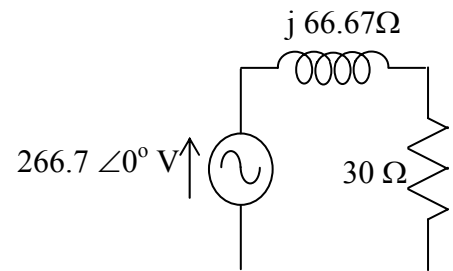- (d) Current through the 30 Ω resistor

$$= 266.7 \angle 0^\circ / (30 + j66.67) = 266.7 \angle 0^\circ / 73.11 \angle 65.77^\circ$$

$$= \underline{\underline{3.648 \text{ A}}}$$



2 marks


**EE 201 - THEORY OF ELECTRICITY – Short Answers**3. (a) $I^2 R = P$

$$\text{supply current } I = \sqrt{\frac{180}{125}} = \underline{\underline{1.2 \text{ A}}}$$

$$\text{circuit impedance } z = (35+125) + j(20+16) = 160 + j36 \Omega$$

$$\text{supply voltage } V = (160 + j36) * 1.2 = 164 \angle 12.68^\circ * 1.2 = 196.8 \angle 12.68^\circ = \underline{\underline{196.8 \text{ V}}}$$

$$\text{supply power factor} = \cos 12.68^\circ = \underline{\underline{0.976 \text{ lag}}}$$

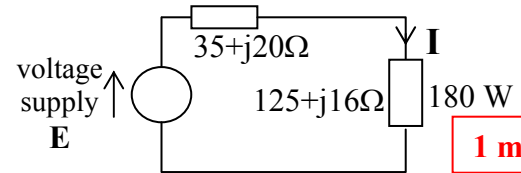**1 mark**

(b) using the star-delta conversion theorem,

$$Y_{AC} = \frac{Y_A \cdot Y_C}{Y_A + Y_B + Y_C} = \frac{\frac{1}{-j6} \times \frac{1}{(4+j3)}}{\frac{1}{-j6} + \frac{1}{(4+j3)} + \frac{1}{(4+j3)}}$$

$$Y_{AC} = \frac{1}{(4+j3) - j6 - j6} = \frac{1}{4 - j9} = 0.0412 + j0.0928,$$

$$Z_{AC} = 4 - j9 \Omega = \underline{\underline{9.85 \angle -66.0^\circ \Omega}}$$

(c) The y-parameter matrix can be obtained from

$$\begin{bmatrix} I_A \\ I_B \end{bmatrix} = \begin{bmatrix} y_{AA} & y_{AB} \\ y_{BA} & y_{BB} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix},$$

$$y_{AA} = \left. \frac{I_A}{V_A} \right|_{V_B=0} = \frac{1}{-j6 + 2 + j1.5} = \frac{1}{2 - j4.5} = 0.203 \angle +66.0^\circ = 0.082 + j0.186$$

$$y_{BA} = \left. \frac{I_B}{V_A} \right|_{V_B=0} = \frac{I_B}{I_A} \times \left. \frac{I_A}{V_A} \right|_{V_B=0} = -\frac{1}{2} \times \frac{1}{2 - j4.5} = -\frac{1}{4 - j9} = 0.102 \angle -114.0^\circ = -0.041 - j0.093$$

$$y_{BB} = \left. \frac{I_B}{V_B} \right|_{V_A=0} = \frac{1}{4 + j3 + \frac{(4+j3)(-j6)}{(4+j3-j6)}} = \frac{1}{9.76 + j1.32} = 0.102 \angle -7.70^\circ = 0.101 - j0.0137$$

$$y_{AB} = \left. \frac{I_A}{V_B} \right|_{V_A=0} = \frac{I_A}{I_B} \times \left. \frac{I_B}{V_B} \right|_{V_A=0} = -\frac{4+j3}{4+j3-j6} \times \frac{1}{9.76 + j1.32} = -\frac{1}{4 - j9} = 0.102 \angle -114.0^\circ = -0.041 - j0.093$$

$$\begin{bmatrix} y_{AA} & y_{AB} \\ y_{BA} & y_{BB} \end{bmatrix} = \begin{bmatrix} 0.203 \angle 66^\circ & 0.102 \angle -114^\circ \\ 0.102 \angle -114^\circ & 0.102 \angle -7.7^\circ \end{bmatrix} \text{ S}$$

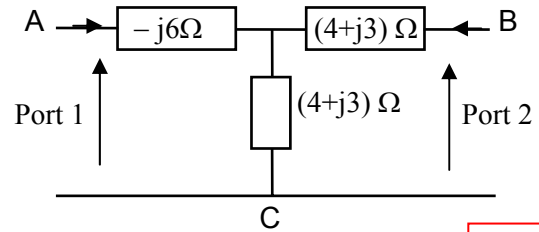
4 marks


Figure Q3

2 marks



EE 201 - THEORY OF ELECTRICITY – Short Answers

4. (a)

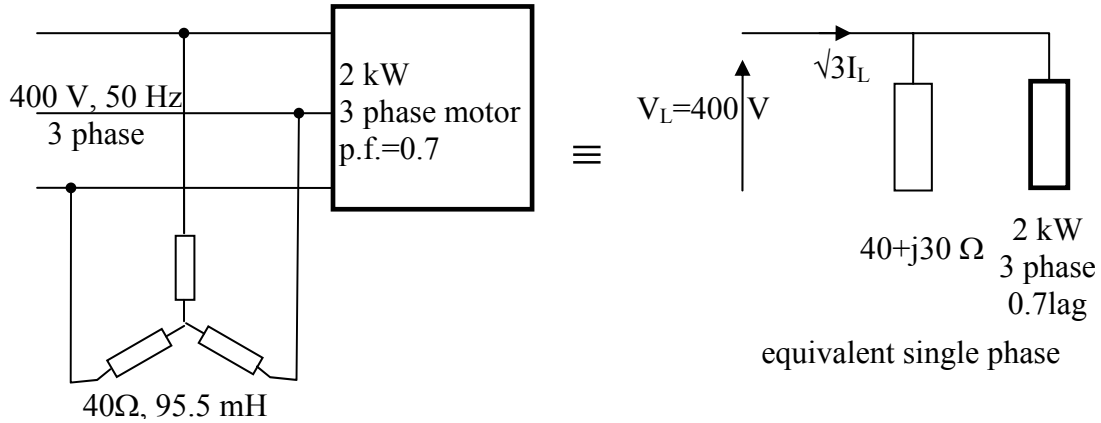

$95.5\text{mH} \rightarrow 95.5 \times 10^{-3} \times 2\pi \times 50 = j30.00\Omega$, gives star connected impedance = $40 + j30 \Omega$

$\therefore \sqrt{3}I_L$ for star connected load = $400/(40 + j30) = 8\angle -36.87^\circ$

and $\sqrt{3}I_L$ for motor load $\rightarrow 2000/400 \times 0.7 = 7.143$ at lagging (motor) p.f. of 0.7
 $\rightarrow 7.143\angle -45.57^\circ$

\therefore total $\sqrt{3}I_L$ for load = $8\angle -36.87^\circ + 7.143\angle -45.57^\circ = 6.4 - j 4.8 + 5.00 - j 5.10$
 $= 11.4 - j 9.9$


\therefore line current supplied from supply = $(11.4 - j 9.9)/\sqrt{3} = \underline{8.72\angle -41.0^\circ \text{ A}}$

Power factor of supply = $\cos 41.0^\circ = \underline{0.755 \text{ lag}}$

3 marks

1 mark

(b)

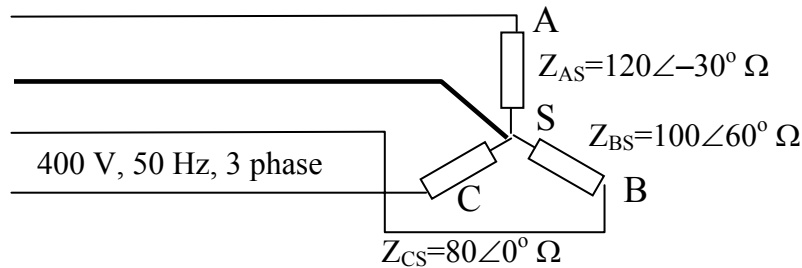

currents in the 3 phases are

$I_A = \frac{230.9\angle 0^\circ}{120\angle -30^\circ} = \underline{1.924\angle 30^\circ \text{ A}}, \quad I_B = \frac{230.9\angle -120^\circ}{100\angle 60^\circ} = \underline{2.309\angle -180^\circ \text{ A}},$

$I_C = \frac{230.9\angle 120^\circ}{80\angle 0^\circ} = \underline{2.886\angle 120^\circ \text{ A}}$

2 marks

(c) sequence components of the currents are given by

$$\begin{bmatrix} I_{a0} \\ I_{a1} \\ I_{a2} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} 1.924\angle 30^\circ \\ 2.309\angle -180^\circ \\ 2.886\angle 120^\circ \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1.924\angle 30^\circ + 2.309\angle -180^\circ + 2.886\angle 120^\circ \\ 1.924\angle 30^\circ + 2.309\angle -60^\circ + 2.886\angle 0^\circ \\ 1.924\angle 30^\circ + 2.309\angle 60^\circ + 2.886\angle 240^\circ \end{bmatrix}$$

$I_{a0} = \frac{1}{3}(1.666 + j0.962 - 2.309 - 1.443 + j2.500) = -0.695 + j1.154 = \underline{1.347\angle 121.1^\circ \text{ A}}$

$I_{a1} = \frac{1}{3}(1.666 + j0.962 + 1.154 - j2.000 + 2.886) = 1.902 - j0.346 = \underline{1.933\angle -10.3^\circ \text{ A}}$

3 marks



EE 201 - THEORY OF ELECTRICITY – Short Answers

$$I_{a2} = \frac{1}{3}(1.666 + j0.962 + 1.154 + j2.000 - 1.443 - j2.500) = 0.459 + j0.154 = \underline{\underline{0.484\angle 18.6^\circ A}}$$

(d) Since there is only a positive sequence voltage, there can be only power associated with positive sequence.

Power associated with zero sequence = 0 W


Power associated with positive sequence = $3 \times 230.9 \times 1.933 \times \cos(-10.3^\circ) = \underline{\underline{1317 W}}$

Power associated with negative sequence = 0 W

1 marks

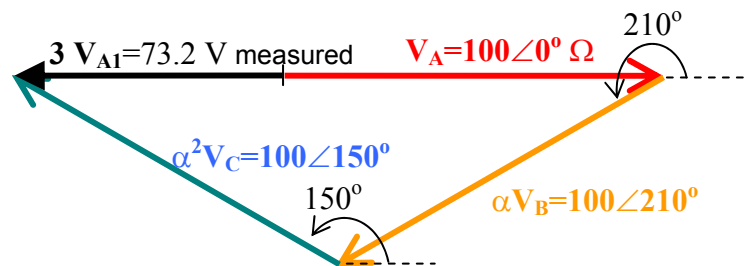
(e) $V_A = 100\angle 0^\circ V$, $V_B = 100\angle 90^\circ V$, $V_C = 100\angle -90^\circ V$

$$V_{A1} = (V_A + \alpha V_B + \alpha^2 V_C)/3 = (100\angle 0^\circ + 100\angle 210^\circ + 100\angle 150^\circ)/3$$



2 marks

5.

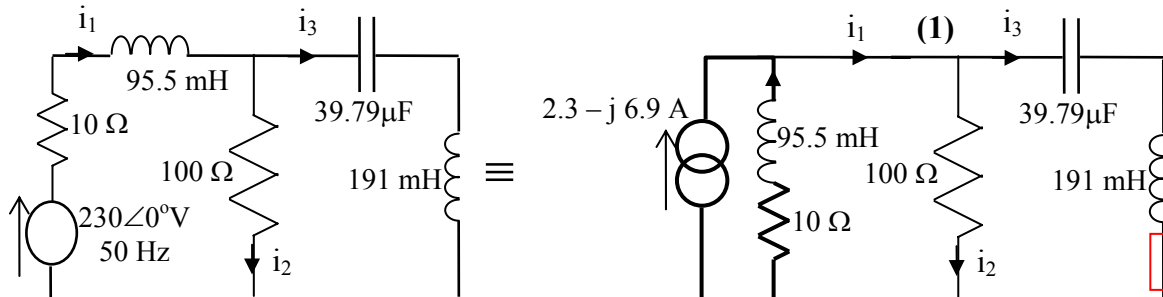

2 mark

circuit can be drawn by taking the 10Ω and the 95.5 mH inductor together in obtaining the equivalent current source. There is only one independent node.

$$\text{Norton's current source} = 230/(10+j30) = 2.3 - j6.9 = 7.30\angle -71.56^\circ$$

$$95.5 \text{ mH} \rightarrow 2\pi \times 50 \times 95.5 \times 10^{-3} \rightarrow j30.0$$

$$39.79 \mu\text{F} \rightarrow 1/2\pi \times 50 \times 39.79 \times 10^{-6} \rightarrow -j80.0$$

$$191 \text{ mH} \rightarrow 2\pi \times 50 \times 191 \times 10^{-3} \rightarrow j60.0$$

$$\text{node branch incidence matrix} = \underline{\underline{\begin{bmatrix} -1 & 1 & 1 \end{bmatrix}}}$$

2 marks

nodal admittance matrix =

$$\left[\frac{1}{10 + j30} + \frac{1}{100} + \frac{1}{-j80 + j60} \right] = [0.01 - j0.03 + 0.01 + j0.05] = [0.02 + j0.02] = 0.02828\angle 45^\circ$$

2 marks

$$\text{Voltage at node (1)} = (2.3 - j6.9)/0.02828\angle 45^\circ = 7.302\angle -71.57^\circ/0.02828\angle 45^\circ = 258.2\angle -116.6^\circ V$$

$$\text{current in branch (1)} = 2.3 - j6.9 - 258.2\angle -116.6^\circ/(10+j30)$$

$$= 2.3 - j6.9 - 258.2\angle -116.6^\circ/31.62\angle 71.57^\circ = 2.3 - j6.9 - 8.166\angle -188.2^\circ$$

$$= 2.3 - j6.9 + 8.08 - j1.16 = 10.38 - j8.06 = \underline{\underline{13.14\angle -37.8^\circ A}}$$

2 marks




EE 201 - THEORY OF ELECTRICITY – Short Answers

$$\text{current in branch (2)} = 258.2 \angle -116.6^\circ / 100 = \underline{2.58 \angle -116.6^\circ \text{ A}}$$

$$\text{current in branch (3)} = 258.2 \angle -116.6^\circ / (-j20) = \underline{12.9 \angle -26.6^\circ \text{ A}}$$

2 marks

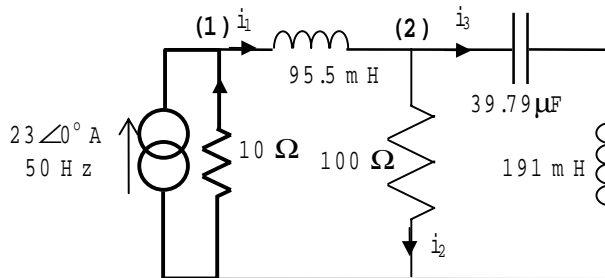alternate circuit by taking only 10Ω for obtaining current source.



This is longer and has 2 independent nodes.

node branch incidence matrix is given by

$$\begin{bmatrix} -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 1 \end{bmatrix}$$

the nodal admittance matrix is given by

$$\begin{bmatrix} \frac{1}{10} + \frac{1}{j30} & -\frac{1}{j30} \\ -\frac{1}{j30} & \frac{1}{j30} + \frac{1}{100} + \frac{1}{-j20} \end{bmatrix} = \begin{bmatrix} 0.1 - j0.0333 & j0.0333 \\ j0.0333 & 0.01 + j0.0167 \end{bmatrix}$$

$$\begin{bmatrix} 23 \\ 0 \end{bmatrix} = \begin{bmatrix} 0.1 - j0.0333 & j0.0333 \\ j0.0333 & 0.01 + j0.0167 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix},$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \frac{1}{\Delta} \begin{bmatrix} 0.01 + j0.0167 & -j0.0333 \\ -j0.0333 & 0.1 - j0.0333 \end{bmatrix} \begin{bmatrix} 23 \\ 0 \end{bmatrix},$$

$$\Delta = (0.1 - j0.0333)(0.01 + j0.0167) - (j0.0333)^2 = 0.001 + 0.000555 + 0.00111 + j0.001666 - j0.000333 \\ = 0.0026666 + j0.0013333 = 0.00298 \angle 26.57^\circ$$

$$V_1 = (0.01 + j0.0167) \times 23 / 0.00298 \angle 26.57^\circ = 0.0194 \angle 59.04^\circ \times 23 / 0.00298 \angle 26.57^\circ = 150.32 \angle 32.4^\circ$$

$$V_2 = -j0.0333 \times 23 / 0.00298 \angle 26.57^\circ = 258.2 \angle -116.6^\circ$$

$$\text{current in branch 1} = (V_1 - V_2) / j30 = (126.9 + j80.55 + 115.6 + j230.9) / j30 = 13.16 \angle -37.9^\circ \text{ A}$$

$$\text{current in branch 2} = V_2 / 100 = 2.58 \angle -116.6^\circ \text{ A}$$


$$\text{current in branch 3} = V_2 / (-j20) = 12.9 \angle -26.6^\circ \text{ A}$$

Note: Current in branch 1 is not equal to $8.13 \angle 171.8^\circ \text{ A}$ as the current of the source of $23 \angle 0^\circ \text{ A}$ must be added as part of the branch 1.



EE 201 - THEORY OF ELECTRICITY – Short Answers

6.

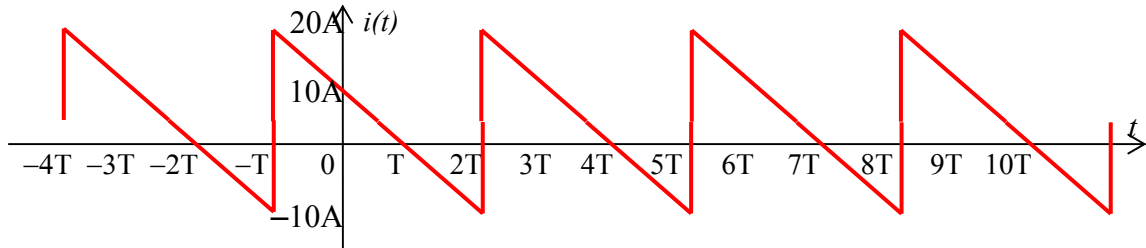Period = $3T$, $\omega = 2\pi/3T$

(a) mean value of waveform = $\frac{1}{2}(20 - 10) = \underline{5 \text{ A}}$

(b) average (rectified) value = $\frac{1}{2}(20 \times 2T + 10 \times T)/3T = 25/3 = \underline{8.33 \text{ A}}$


(c) r.m.s. value

$$= \sqrt{\frac{1}{3T} \int_{-T}^{2T} \left(10 - \frac{10}{T} \times t\right)^2 \cdot dt} = \sqrt{\frac{1}{3T} \times \frac{1}{3} \left(10 - \frac{10}{T} \times t\right)^3 \times \left(-\frac{T}{10}\right) \Big|_{-T}^{2T}} = \sqrt{-\frac{1}{90} \left((-10)^3 - 20^3\right)}$$

2 marks

$$= \sqrt{100} = \underline{10.0 \text{ A}}$$

(d) form factor = $10.0/8.33 = \underline{1.2}$

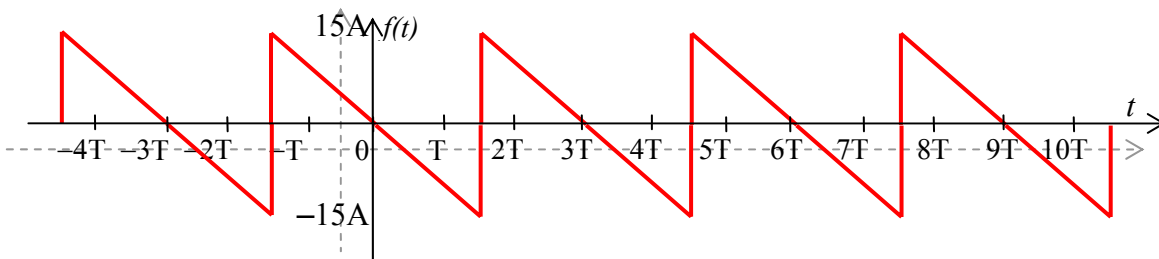(e) waveform may be shifted by the mean value on the y-axis and by an amount $T/2$ on the x-axis, as follows to obtain a more symmetrical waveformwhere $i(t) = 5 + f(t - T/2)$, period = $3T$, $3\omega T = 2\pi$

$$f(t) = A_0/2 + \sum A_n \cos n\omega t + B_n \sin n\omega t$$

function $f(t)$ has mean value = $0 \rightarrow A_0/2 = 0$

$f(t)$ is odd $\rightarrow A_n = 0$ for all n

 $f(t)$ does not have half-wave symmetry \rightarrow even harmonics are present

$$\therefore B_n = 2 \times \frac{2}{3T} \int_0^{3T/2} f(t) \cdot \sin n\omega t \cdot dt = \frac{4}{3T} \left[\int_0^{3T/2} \left(-\frac{10t}{T}\right) \cdot \sin n\omega t \cdot dt \right]$$

$$\text{i.e. } B_n = \frac{4}{3T} \times \left[\left(-\frac{10t}{T}\right) \cdot \frac{\cos n\omega t}{-n\omega} \Big|_0^{3T/2} - \int_0^{3T/2} \left(-\frac{10}{T}\right) \cdot \frac{\cos n\omega t}{-n\omega} \cdot dt \right]$$

$$= \frac{4}{3T} \left[\left(\frac{15}{n\omega}\right) \cos \frac{3n\omega T}{2} - \left(\frac{10}{T}\right) \cdot \frac{\sin n\omega t}{(n\omega)^2} \Big|_0^{3T/2} \right] = \left[\frac{30}{n\pi} \cdot \cos n\pi - \frac{30}{(n\pi)^2} \cdot \sin n\pi \right]$$

$B_1 = (30/\pi) \cdot \cos \pi - 0 = -9.55$, $B_2 = (30/2\pi) \cdot \cos 2\pi - 0 = 4.77$,

$B_3 = (30/3\pi) \cdot \cos 3\pi - 0 = -3.18$, $B_4 = (30/4\pi) \cdot \cos 4\pi - 0 = 2.39$, $B_5 = \dots\dots$

$$\therefore f(t) = -9.55 \sin (2\pi/3T)t + 4.77 \sin (2 \times 2\pi/3T)t - 3.18 \sin (3 \times 2\pi/3T)t + \dots$$

4 marks



EE 201 - THEORY OF ELECTRICITY – Short Answers

$$\text{and } i(t) = 5 + f\left(t - \frac{T}{2}\right) = 5 - 9.55 \sin\left(\frac{2\pi}{3T}t - \frac{\pi}{3}\right) + 4.77 \sin\left(\frac{4\pi}{3T}t - \frac{2\pi}{3}\right) + 3.18 \sin\left(\frac{2\pi}{T}t\right) + \dots \quad \text{2 marks}$$

$$T = 10 \text{ ms}, \quad \omega = 2\pi/3T = 200\pi/3 = 209.4 \text{ rad/s}$$

$$(f) \quad V_n = I_n * [20 + jn(2\pi/0.01) \times 0.01] = I_n * [20 + j 2n\pi/3]$$

$$|V_n| = I_n * \sqrt{[20^2 + 4\pi^2 n^2/9]}, \quad \theta_n = \tan^{-1}[n\pi/10]$$

$$V_{dc} = 5 * 20 = 100 \text{ V}$$


$$V_{1m} = -9.55 * \sqrt{[20^2 + 4\pi^2/9]} = -192.0$$

$$\theta_1 = \tan^{-1}[\pi/30] = 6.0^\circ$$

$$V_{2m} = 4.77 * \sqrt{[20^2 + 16\pi^2/9]} = 97.5, \quad \theta_2 = \tan^{-1}[2\pi/30] = 11.83^\circ$$

$$V_{3m} = -3.18 * \sqrt{[20^2 + 36\pi^2/9]} = -66.7, \quad \theta_3 = \tan^{-1}[3\pi/30] = 17.44^\circ$$
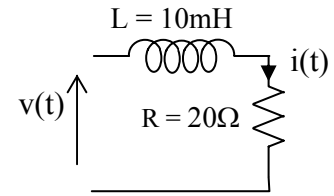
$$\text{and } v(t) = 100 - 192 \sin\left(\frac{2\pi}{3T}t - 54.0^\circ\right) + 97.5 \sin\left(\frac{4\pi}{3T}t - 108.2^\circ\right) + 66.7 \sin\left(\frac{2\pi}{T}t + 17.4^\circ\right) + \dots \quad \text{2 marks}$$



$$\text{OR using } v(t) = L \frac{di}{dt} + Ri$$


$$7. (a) \text{ Laplace transform of the unit step } L[h(t)] = \int_0^{\infty} 1 \cdot e^{-st} dt = \frac{e^{-st}}{-s} \Big|_0^{\infty} = \frac{1}{s}, \quad \text{1 mark}$$

$$(b) \text{ for unit ramp } L[r(t)] = \int_0^{\infty} t \cdot e^{-st} dt = t \cdot \frac{e^{-st}}{-s} \Big|_0^{\infty} - \int_0^{\infty} \frac{e^{-st}}{-s} dt = -\frac{e^{-st}}{(-s)^2} \Big|_0^{\infty} = \frac{1}{s^2} \quad \text{1 mark}$$

$$(c) \text{ for shifted waveform } L[f(t-a)] = \int_0^{\infty} f(t-a) \cdot e^{-st} dt = \int_{-a}^{\infty} f(t) \cdot e^{-s(t+a)} d(t+a)$$

$$= \int_0^{\infty} f(t) \cdot e^{-st} \cdot e^{-sa} dt = e^{-sa} \cdot F(s) \quad \text{1 mark}$$

(d) given waveform can be split into ramp and steps as follows

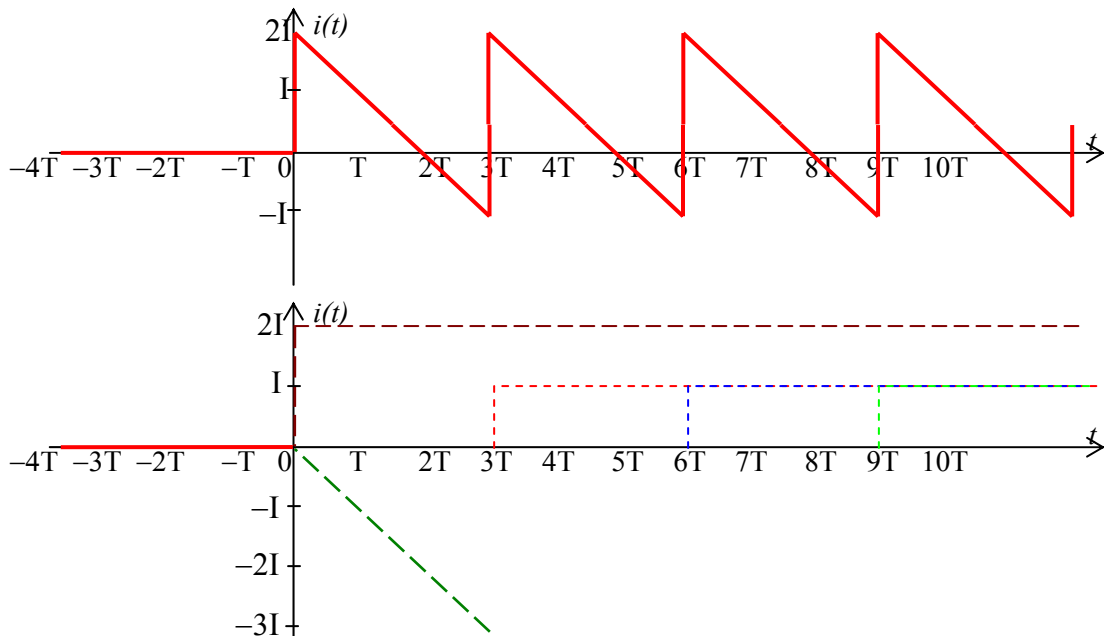

**EE 201 - THEORY OF ELECTRICITY – Short Answers**

i.e. $i(t) = 2I \cdot h(t) - \frac{I}{T} r(t) + I h(t - 3T) + I h(t - 6T) + I h(t - 9T) + \dots$

$$I(s) = \frac{2I}{s} - \frac{I}{s^2 T} + \frac{I}{s} e^{-3sT} + \frac{I}{s} e^{-6sT} + \frac{I}{s} e^{-9sT} + \dots$$

5 marksAlternate Method

For a repetitive waveform, with period T

$$f(t) = f_1(t)|_0^T + f_2(t)|_T^{2T} + f_3(t)|_{2T}^{3T} + f_4(t)|_{3T}^{4T} + \dots$$

$$= f_1(t)|_0^T + f_2(t-T)|_0^T + f_3(t-2T)|_0^T + f_4(t-3T)|_0^T + \dots$$

$$F(s) = L[f_1(t)|_0^T] + L[f_2(t-T)|_0^T] + L[f_3(t-2T)|_0^T] + L[f_4(t-3T)|_0^T] + \dots$$

$$= L[f_1(t)|_0^T] + e^{-sT} L[f_1(t-T)|_0^T] + e^{-2sT} L[f_1(t-2T)|_0^T] + e^{-3sT} L[f_1(t-3T)|_0^T] + \dots$$

$$= \frac{1}{1 - e^{-sT}} L[f_1(t)|_0^T]$$

for the given waveform, considering one period only

$$F_1(s) = \int_0^{3T} \left(2I - \frac{I}{T} t \right) \cdot e^{-st} dt = \left(2I - \frac{I}{T} t \right) \cdot \frac{e^{-st}}{-s} \Big|_0^{3T} - \int_0^{3T} \left(-\frac{I}{T} \right) \cdot \frac{e^{-st}}{-s} dt$$

$$= -\frac{I \cdot e^{-3sT}}{-s} + \frac{2I}{s} + \frac{(e^{-3sT} - 1)}{s^2 T}$$

$$F(s) = \frac{1}{1 - e^{-3sT}} \left[\frac{2I}{s} + \frac{I \cdot e^{-3sT}}{s} + \frac{(e^{-3sT} - 1)}{s^2 T} \right] = \frac{2I}{s} - \frac{I}{s^2 T} + \frac{e^{-3sT}}{1 - e^{-3sT}} \frac{I}{s}$$