

## BSc Engineering Degree Course, Level 2

### EE201 – Theory of Electricity – Professor J R Lucas

#### Problems on Circuit Transients


##### Introduction

Switching of a circuit from one state to another, either by a change in the source condition or by a change in the circuit condition, causes a transient state in the circuit. During this period the behaviour of the circuit is governed by a differential equation. The solution of such a differential equation has two parts, namely the *complementary function* which refers to the changes occurring during the *transient state* and the *particular solution* which refers to a possible solution, and in particular this solution may be taken from the *steady state* condition.
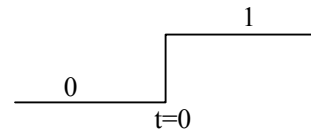
##### Unit Step $h(t)$

One of the commonest reasons for the occurrence of transients is the switching on or switching off of a supply. In such cases, the level of the supply just before and just after would represent two distinct levels, such as in a physical step. Such waveforms are known as step waveforms, and the basic form of this is the **unit step** which has a magnitude **unity** and starts at  $t=0$ .


$$\begin{aligned}h(t) &= 0, \text{ for } t \leq 0 \\ &= 1, \text{ for } t \geq 0\end{aligned}$$


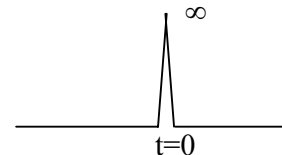
##### Unit Impulse $\delta(t)$

Another of the common reasons for the occurrence of transients is an impulsive action, which has a very large magnitude for a negligible time. This is characterised by the **unit impulse** which has zero magnitude other than at time zero when it has infinite magnitude. Also the area enclosed by the waveform is unity.

$$\begin{aligned}\delta(t) &= 0, \text{ for } t < 0 \\ &= \infty, \text{ for } t = 0 \\ &= 0, \text{ for } t > 0\end{aligned} \quad \int_{-\infty}^{\infty} \delta(t) \cdot dt = 1$$



The unit impulse function also has the following properties.

$$\int_{-\infty}^{\infty} f(t) \cdot \delta(t) \cdot dt = f(0)$$

and 
$$\int_{-\infty}^{\infty} f(t - \tau) \cdot \delta(t) \cdot dt = f(\tau)$$

The unit impulse is the derivative of the unit step.

Both the unit step and the unit impulse can be used to define the natural behaviour of a network.


## Problems

Ex 1 – Simple RL circuit supplied from a step voltage source (switch closed onto a battery)

If the switch is closed at time  $t=0$ , the voltage across the RL combination would be  $e(t)$  which is a step of magnitude  $E$  [or  $E.h(t)$ ] and not a constant as is the supply voltage  $E$ .

$$e(t) = 0, \text{ for } t \leq 0$$

$$= E, \text{ for } t \geq 0$$

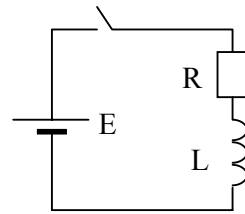

Thus the differential equation governing the behaviour of the circuit would be

$$e(t) = R \cdot i(t) + L \cdot \frac{di(t)}{dt} = R \cdot i + L \cdot p i$$

For complementary function,  $R + L p = 0$ , giving  $p = -R/L$

A particular solution is the steady state solution, which gives the current under steady conditions as  $i(t) = E/R$ . [no voltage drop across inductor at steady state].

Therefore the solution can be written in the form  $i(t) = \frac{E}{R} + A \cdot e^{-\frac{R}{L}t}$  where  $A$  is a constant.


The constant  $A$  can be obtained from the initial conditions as follows.

At  $t=0$ ,  $i(t) = 0$  [since the current through an inductance cannot change suddenly]

$$\therefore 0 = \frac{E}{R} + A \cdot e^{-\frac{R}{L} \times 0} = \frac{E}{R} + A$$



giving  $A = -\frac{E}{R}$ .

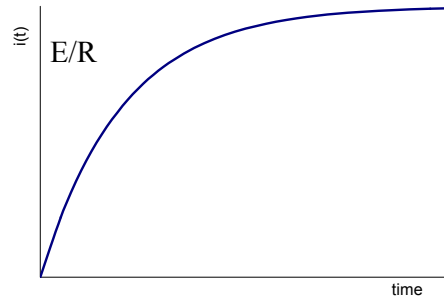Therefore the solution is  $i(t) = \frac{E}{R} \left( 1 - e^{-\frac{R}{L}t} \right)$ .



The voltage drops across each of the elements can now be obtained as

$$v_R(t) = R i(t) = E \left( 1 - e^{-\frac{R}{L}t} \right) \text{ and } v_L(t) = L \cdot \frac{di(t)}{dt} = E \cdot e^{-\frac{R}{L}t}$$

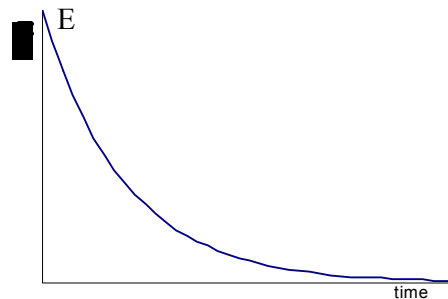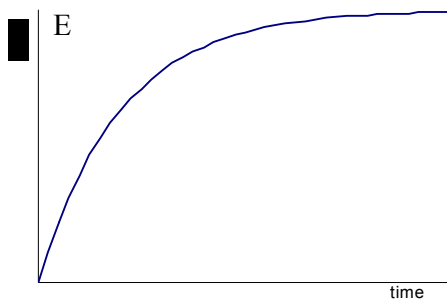


Ex 2 – Simple R C circuit supplied from a step voltage source (switch closed onto a battery)

The differential equation governing the behaviour of the circuit would be

$$e(t) = R \cdot i(t) + \frac{1}{C} \int i(t) dt = R \cdot i(t) + \frac{1}{C \cdot p} i(t)$$

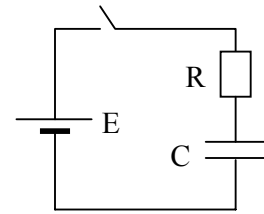For complementary function,  $R + \frac{1}{C \cdot p} = 0$ , giving  $p = -1/RC$



A particular solution is the steady state solution, which gives the current under steady conditions as  $i(t) = 0$ . [no current through capacitor at steady state].

Therefore the solution can be written in the form  $i(t) = 0 + A \cdot e^{-\frac{1}{RC}t}$  where  $A$  is a constant.

$A$  can be obtained from the initial conditions as follows.

At  $t=0$ ,  $v_C(t) = 0$  [since the voltage across a capacitor cannot change suddenly].

$$\therefore v_R(t) = E \text{ and } i(t) = E/R$$

$$\frac{E}{R} = A \cdot e^{-\frac{1}{RC} \times 0} \text{ giving } A = E/R. \text{ Therefore the solution is } i(t) = \frac{E}{R} e^{-\frac{1}{RC}t}.$$


The voltage drops across the elements can now be obtained using Ohm's law.

The sketches of voltage and current can be done as in the earlier example.

Ex 3 – R C circuit supplied from a step voltage source, but with C initially charged to  $V_o$

The differential equation governing the behaviour of the circuit would be
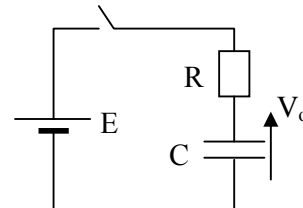
$$e(t) = R \cdot i(t) + \frac{1}{C} \int i(t) dt + V_o = R \cdot i + \frac{1}{C \cdot p} i + V_o$$



The complementary function remains the same as in Ex2 except that the value of the constant will be different.

The particular solution would again be zero.


At  $t=0$ ,  $v_C(t) = V_o$  [since the voltage across a capacitor cannot change suddenly].

$$\therefore v_R(t) = E - V_o \text{ and } i(t) = (E - V_o)/R$$

$$\therefore \frac{E - V_o}{R} = A \cdot e^{-\frac{1}{RC} \times 0} \text{ giving } A = \frac{E - V_o}{R} \therefore i(t) = \frac{E - V_o}{R} \cdot e^{-\frac{1}{RC}t}$$

It can be shown using Ohm's law that

$$v_C(t) = E - (E - V_o) \cdot e^{-\frac{1}{RC}t}$$

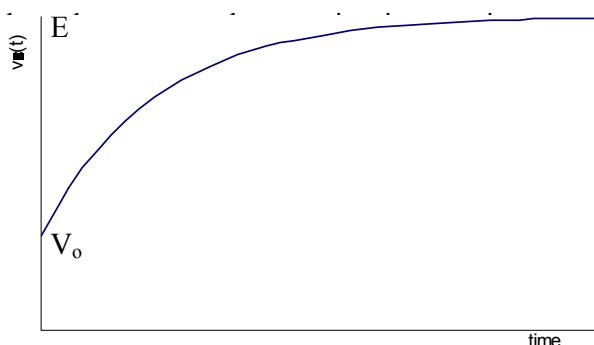

Ex 4 –RLC circuit supplied from a step voltage source

$$e(t) = R.i(t) + L \frac{d i(t)}{d t} + \frac{1}{C} \int i(t) dt = R.i(t) + L.p.i(t) + \frac{1}{C.p} i(t)$$

$$p.e(t) = R.p.i(t) + L.p^2.i(t) + \frac{1}{C} i(t)$$

The complementary function is  $R.p + L.p^2 + 1/C = 0$

The solution of this equation can be real or complex dependant on the values of components.

(a)  $R = 480 \Omega$ ,  $L = 0.4 \text{ H}$ ,  $C = 2.5 \mu\text{F}$ ,  $E = 120 \text{ V}$

complementary function is  $0.4 p^2 + 480 p + 4 \times 10^5 = 0$

i.e.  $p^2 + 1200 p + 10^6 = 0$  giving  $p = -600 \pm \sqrt{600^2 - 10^6} = -600 \pm j 800$

The particular solution in this case would be  $i(t)=0$  at  $t=\infty$

giving a solution of the form  $A.e^{-600t}.e^{j800t} + B.e^{-600t}.e^{-j800t}$ , or  $C.e^{-600t}.\cos(800t+\theta)$

Using initial conditions [2 are required here as there are 2 energy storing elements]

$i(t) = 0$  and  $v_C(t)=0$  at  $t=0$

$0 = C.e^{-600 \times 0}.\cos(800 \times 0 + \theta)$  gives  $\theta = \pm 90^\circ$  as C cannot be zero [trivial solution]

giving the solution  $i(t) = C.e^{-600t}.\sin 800t$

Also since  $i(0)=0$ ,  $v_R(0) = 0$ .  $\therefore v_L(0) = 120 = 0.4 \times \frac{d i}{d t}$  giving  $\frac{d i}{d t} = 300$  at  $t=0$

$$\frac{d i}{d t} = C.[-600 \times e^{-600 \times 0}.\sin 800 \times 0 + e^{-600 \times 0}.800 \times \cos 800 \times 0] = 300$$

giving  $C = 300/800 = 0.375$




$\therefore i(t) = 0.375 e^{-600t}.\sin 800t \text{ A}$

Using Ohm's law, the voltages across the elements are given as

$$v_R(t) = 480 i(t) = 180 e^{-600t}.\sin 800t \text{ V}$$

$$v_L(t) = 0.4 p.i(t) = -90 e^{-600t}.\sin 800t + 120 e^{-600t}.\cos 800t \text{ V}$$
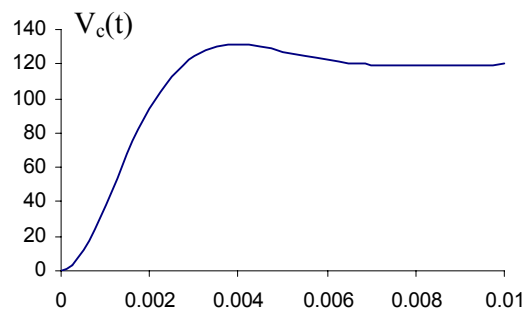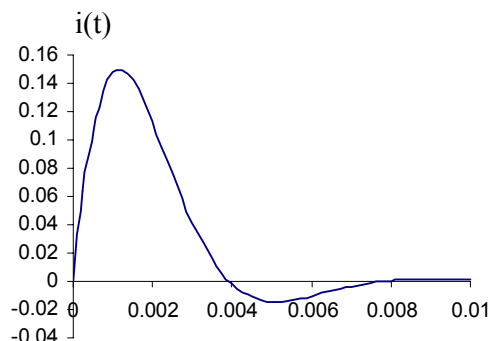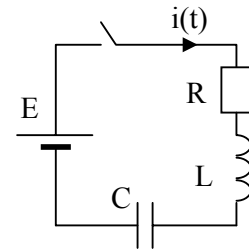
$$v_C(t) = 120 - 90 e^{-600t}.\sin 800t - 120 e^{-600t}.\cos 800t \text{ V}$$



(b)  $R = 800 \Omega, L = 0.4 \text{ H}, C = 2.5 \mu\text{F}, E = 120 \text{ V}$

complementary function is  $0.4 p^2 + 800 p + 4 \times 10^5 = 0$

i.e.  $p^2 + 2000 p + 10^6 = 0$  giving  $(p + 1000)^2 = 0$  or  $p = -1000$  (repeated roots)

In this case the solution is of the form


$$i(t) = A t e^{-1000t} + 0$$

At  $t=0, i(t) = 0$ , [automatically satisfied]

and  $di(t)/dt = 300$

$$\frac{di}{dt} = A e^{-1000 \times 0} - 1000 A \times 0 \cdot e^{-1000 \times 0} = 300 \text{ giving } A = 300$$
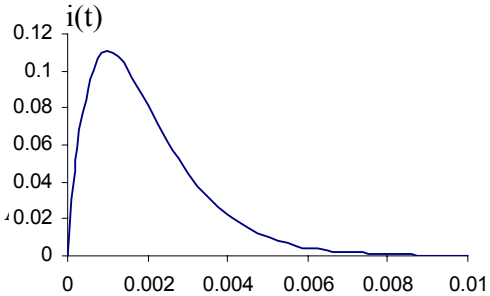
$$\therefore i(t) = 300 t e^{-1000t} \text{ A}$$



(c)  $R = 1000 \Omega, L = 0.4 \text{ H}, C = 2.5 \mu\text{F}, E = 120 \text{ V}$

complementary function is  $0.4 p^2 + 1000 p + 4 \times 10^5 = 0$

i.e.  $p^2 + 2500 p + 10^6 = 0$  giving

$(p + 500)(p + 2000) = 0$  or  $p = -500$  or  $-2000$

In this case the solution is of the form

$$i(t) = A e^{-500t} + B e^{-2000t}$$

At  $t=0, i(t) = 0 = A + B$

At  $t=0, v_C(t) = 0$ , gives  $di(t)/dt = 300$ .

i.e.  $-500A - 2000B = 300$ , gives  $A = 0.2 = -B$

$$\therefore i(t) = 0.2 (e^{-500t} - e^{-2000t}) \text{ A}$$

