

**EE 201 - THEORY OF ELECTRICITY**

Time Allowed: Three Hours

September 2005.

Answer **All** Questions.

Marks allocated for the paper is 70.

Permeability of free space  $\mu_0 = 4 \pi \times 10^{-7}$  H/m

Permittivity of free space  $\epsilon_0 = 8.854 \times 10^{-12}$  F/m

1. (a) If the circuit shown in figure Q1 is at resonance, what would be the value of the inductor L, and what would be corresponding current supplied from the supply. [2 mark]
- (b) If  $L = 50$  mH instead, determine all the currents and voltages indicated on figure Q1. [3 marks]
- (c) Sketch the phasor diagram showing all the currents and voltages calculated in section (b) relative to the supply voltage E. [2 marks]

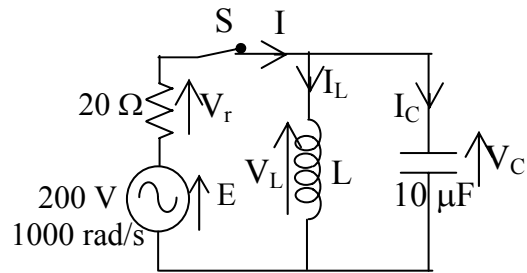


Figure Q1

- (d) If in figure Q1, the supply could be expressed as  $e(t) = 282.8 \cos 1000 t$  V, and the switch S is opened at time  $t = 1$  ms, using calculations already made or otherwise, determine the initial current through the inductor and the initial voltage across the capacitor for the purpose of transient analysis. [2 marks]
- (e) Sketch the transformed circuit corresponding to section (d) for analysis using Laplace Transform. [2 mark]

2. (a) Show from first principles how two inductances  $L_1, L_2$  in two branches of a T-junction which have a mutual inductance M can be represented by a T-junction having non-coupled branches. [2 marks]

(b) Draw the non-coupled equivalent circuit of the circuit shown in figure Q2. [2 marks]

(c) Determine and sketch the Thevenin's equivalent circuit across the  $30 \Omega$  resistor for the circuit shown in figure Q2. [3 marks]

(d) Hence determine the current through the  $30 \Omega$  resistor for figure Q2. [2 marks]

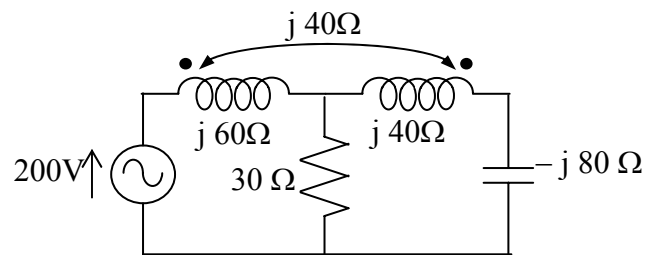


Figure Q2

3. (a) In a single phase circuit, the active power delivered to the load is measured to be 180 W when the load impedance is  $(125+j16) \Omega$  and the source impedance is  $(35+j20) \Omega$ . Determine the magnitudes of the supply voltage E, the supply current I and the supply power factor. [4 marks]

(b) For the star connected circuit shown in figure Q3, determine the impedance of the arm AC of the delta equivalent. [2 marks]

(c) Obtain the y-parameter matrix of the two port circuit shown in figure Q3. [4 marks]

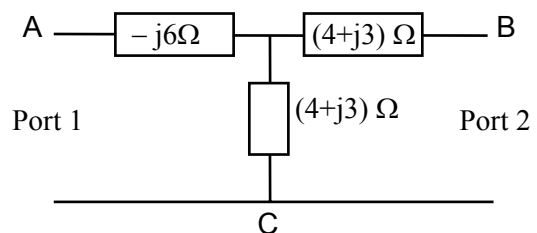


Figure Q3

4. (a) A balanced 400V, 50 Hz, 3 phase supply feeds (i) a star connected load with each arm consisting of a resistance of  $40 \Omega$  in series with an inductance of 95.5 mH, and (ii) a 2 kW three-phase motor with a power factor of 0.7. Determine the current supplied from the supply and the supply power factor. [4 marks]
- (b) A balanced, three phase, 400 V, 4-wire supply, sequence ABC, supplies an unbalanced star-connected load consisting of  $Z_{AS} = 120\angle-30^\circ \Omega$ ,  $Z_{BS} = 100\angle60^\circ \Omega$ , and  $Z_{CS} = 80\angle0^\circ \Omega$ . Determine the currents in the three phases. [2 marks]
- (c) Determine the sequence components of the unbalanced currents in section (b) [3 marks]
- (d) Determine the total power associated with each of the sequence components in section (c). [1 marks]
- (e) Show graphically how the positive sequence component of the phase voltages  $V_A = 100\angle0^\circ \text{ V}$ ,  $V_B = 100\angle90^\circ \text{ V}$ ,  $V_C = 100\angle-90^\circ \text{ V}$  is determined. [2 marks]

5. For the circuit shown in figure Q5, replace the voltage source by an equivalent current source and redraw the circuit. [2 mark]
- By suitably numbering the nodes, determine the node-branch incidence matrix. [2 marks]
- Hence or otherwise determine the nodal admittance matrix. [2 marks]
- Using nodal analysis determine the currents in all the branches of the original circuit. [4 marks]

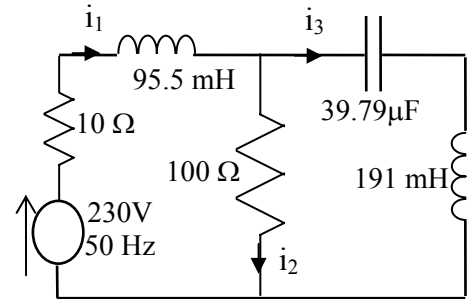


Figure Q5

6. For the periodic current waveform  $i(t)$  shown in figure Q6, determine (a) the mean value, (b) the average value, (c) the rms value and (d) the form factor. [2 marks]

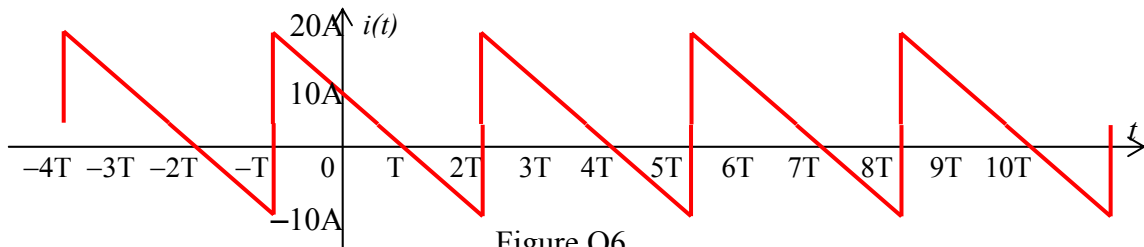


Figure Q6

- (e) Write down the Fourier Series of the current waveform  $i(t)$  shown to 4 significant terms. [6 marks]
- (f) If  $T = 10 \text{ ms}$ , and this current  $i(t)$  is passed through a series combination of a resistor of  $20 \Omega$  and an inductor of 10 mH, determine the Fourier series of the resulting voltage. [2 marks]
7. Determine from first principles, the Laplace transform of (a) the unit step waveform  $h(t)$ , and (b) the causal unit ramp waveform  $r(t) = t$ . [2 marks]
- (c) Determine the Laplace transform  $F_a(s)$  of the causal waveform  $f(t-a)$ , in terms of the Laplace transform  $F(s)$  of the causal waveform  $f(t)$ . [1 mark]
- (d) Using the properties derived in (a), (b) and (c), or otherwise determine the Laplace Transform of the waveform shown in figure Q7. [5 marks]

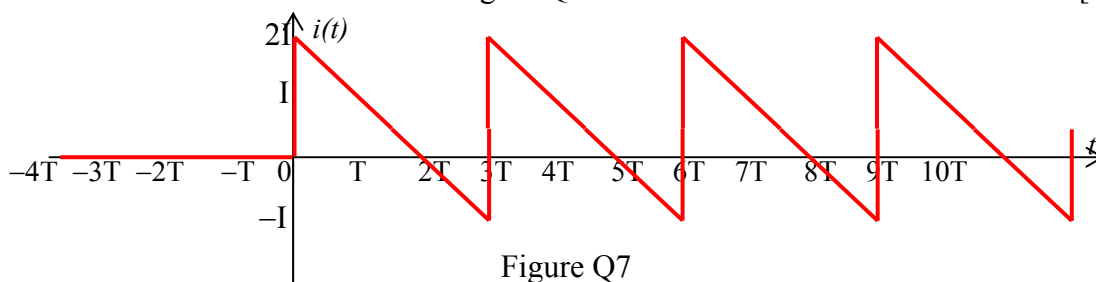


Figure Q7