



University of Moratuwa, Sri Lanka
Faculty of Engineering
Department of Electrical Engineering
B. Sc. Engineering Honours Degree Course
Semester 2 Examination

EE2092 – THEORY OF ELECTRICITY

Time Allowed: 2 Hours

May 2012

Additional Material

Graph Paper will be provided if required.

A table of Laplace transforms is provided on the other side of this page.

Instructions to Candidates

This paper contains 5 questions in 6 pages, including the cover page.

Answer All Questions.

This examination accounts for 70% of the module assessment.

Each question carries a total 14 marks. Maximum marks allocated for each part of a question is indicated in square brackets at the end of the part.

Total allocation for the paper is 70 marks.

This is a closed book examination and only authorised calculators will be permitted.

Technical Data:

Permeability of free space μ_0 = $4\pi \times 10^{-7}$ H/m

Permittivity of free space ϵ_0 = 8.854×10^{-12} F/m

Velocity of light in free space = 2.998×10^8 m/s

Table of Laplace Transforms of common causal functions $f(t)$

$f(t)$	$F(s) = \mathcal{L}[f(t)]$
Unit impulse – δt	1
Unit step – $U(t)$	$\frac{1}{s}$
t	$\frac{1}{s^2}$
t^n	$\frac{n!}{s^{n+1}}$
e^{-at}	$\frac{1}{(s+a)}$
$1 - e^{-at}$	$\frac{a}{s(s+a)}$
$t e^{-at}$	$\frac{1}{(s+a)^2}$
$t^n e^{-at}$	$\frac{n!}{(s+a)^{n+1}}$
$e^{-at} - e^{-bt}$	$\frac{b-a}{(s+a)(s+b)}$
$\sin(\omega t)$	$\frac{\omega}{(s^2 + \omega^2)}$
$\sin(\omega t + \phi)$	$\frac{\omega \cos(\phi) + s \sin(\phi)}{(s^2 + \omega^2)}$
$t \sin(\omega t)$	$\frac{2\omega s}{(s^2 + \omega^2)^2}$
$\cos(\omega t)$	$\frac{s}{(s^2 + \omega^2)}$
$\cos(\omega t + \phi)$	$\frac{s \cos(\phi) - \omega \sin(\phi)}{(s^2 + \omega^2)}$
$t \cos(\omega t)$	$\frac{s^2 - \omega^2}{(s^2 + \omega^2)^2}$
$e^{-at} \sin(\omega t)$	$\frac{\omega}{(s+a)^2 + \omega^2}$
$e^{-at} \cos(\omega t)$	$\frac{s+a}{(s+a)^2 + \omega^2}$
$\sinh(\omega t)$	$\frac{\omega}{(s^2 - \omega^2)}$
$\cosh(\omega t)$	$\frac{s}{(s^2 - \omega^2)}$

Question 1

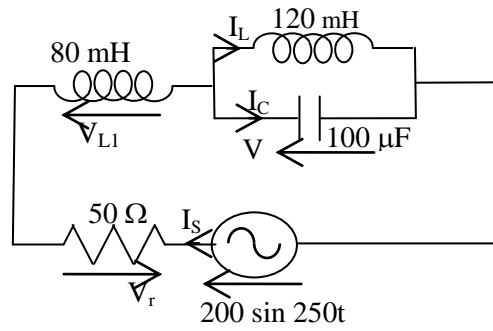


Figure Q1

For the circuit shown in figure Q1,

- Write down the differential equations governing the behaviour of the circuit. [2 marks]
- Calculate the total impedance of the circuit in ohm. [2 marks]
- Calculate the current I_s supplied from the source. [1 mark]
- Determine the currents I_L and I_C . [2 marks]
- Determine the voltages V_r , V_{L1} and V . [2 marks]
- Sketch a phasor diagram showing all the voltages and currents in the circuit. [3 marks]
- If the supply frequency is allowed to vary, determine the frequency at which series resonance would occur. [2 marks]

Question 2

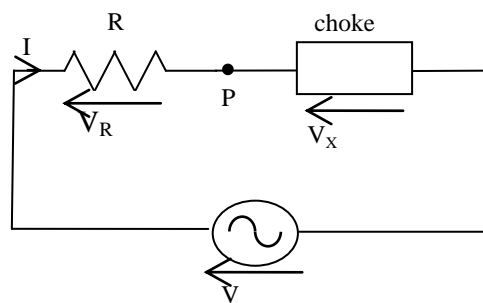


Figure Q2ab

- A practical choke (inductance L and series resistance r), connected in series with a pure resistance R , is supplied from a constant voltage source (V, ω) . If the resistance R is allowed to vary, sketch the locus of the voltage of the intersection P between the choke and the resistor. [3 marks]
- One of the readings in Q2(a) corresponds to $V = 250V$ at 50 Hz, current $I = 10A$ lagging voltage by 30° , the voltage magnitudes across the resistor $V_R = 150V$ and choke $V_X = 141.6V$. Complete the phasor diagram and calculate the inductance L and the resistance r of the choke. [3 marks]
- Derive the non-coupled equivalent circuit of a two winding transformer. [2 marks]
A 80/20kV transformer has a primary winding inductance of 16H, and a coupling coefficient of 0.95. Using any standard equations derive the values of the inductive impedances of all the elements of the non-coupled equivalent circuit, [2 marks]
- Sketch the equivalent circuit of an operational amplifier and show that the voltage difference of the input terminals may be taken as a virtual zero. [2 marks]
- It is required to construct a summing amplifier to add 75% of input A voltage and 25% of input B voltage. If the resistance connected across the operational amplifier is 1 k Ω , use a diagram to show what should be the input resistances to be connected for the two inputs? [2 marks]

Question 3

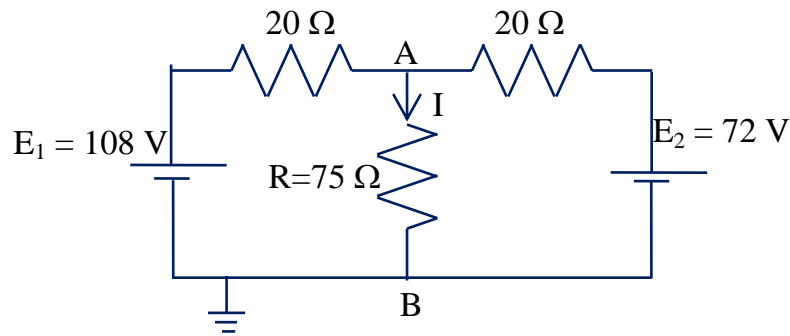


Figure Q3ab

- (a) For the circuit shown in figure Q3ab, obtain the Norton's equivalent circuit across AB and hence obtain the current I. [3 marks]
- (b) Using compensation theorem, determine the resistance to which R must be changed if the desired current I in figure Q3ab is 1.0A. [2 marks]

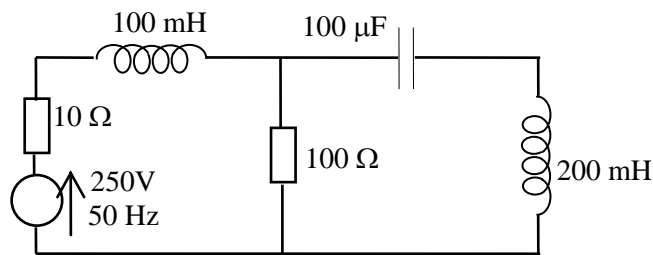


Figure Q3c

- (c) For the circuit shown in figure Q3c, write down the branch-mesh incidence matrix and the branch impedance matrix. [3 marks]
- Hence determine the mesh impedance matrix. [2 marks]

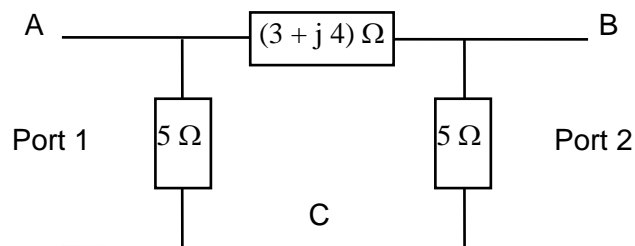


Figure Q3de

- (d) Determine the ABCD matrix of the two-port network shown in figure Q3de. [2 marks]
- (e) Convert the circuit shown in figure Q3de to an equivalent star-connected network between nodes A, B and C and redraw the circuit. [2 marks]

Question 4

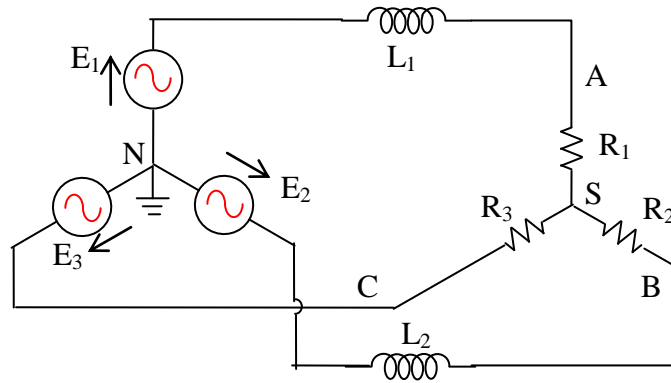


Figure Q4(a)

- (a) The supply shown in figure Q4(a) is a balanced 3phase, 400V, 50 Hz source. If $L_1 = L_2 = 100 \text{ mH}$, and $R_1 = R_2 = R_3 = 100 \Omega$, determine the voltage of the star point S. [4 marks]
- Hence determine the potential at A. [2 marks]
- (b) A balanced 400 V, 3-phase, 50 Hz supply feeds (i) a 3-phase delta-connected balanced load consisting of arms of value $(80+j60) \Omega$ each and (ii) a three phase motor load of 3 kW at a power factor of 0.6 lag, Determine the line current, power factor and the active power at the supply. [3 marks]
- Determine also the rating of the delta connected capacitor bank required to improve the overall power factor to 0.95 lagging. [2 marks]
- (c) The phase components of the currents in an unbalanced system A-B-C is given as $I_A = 20\angle-30^\circ \text{ A}$, $I_B = 15\angle60^\circ \text{ A}$ and $I_C = 20\angle-120^\circ \text{ A}$. Determine the sequence components of the currents. [2 marks]
- If the corresponding sequence components of the voltages are $V_{A0} = 50\angle-30^\circ \text{ V}$, $V_{A1} = 200\angle0^\circ \text{ V}$, $V_{A2} = 50\angle-30^\circ \text{ V}$, determine the total active power. [1 mark]

Question 5

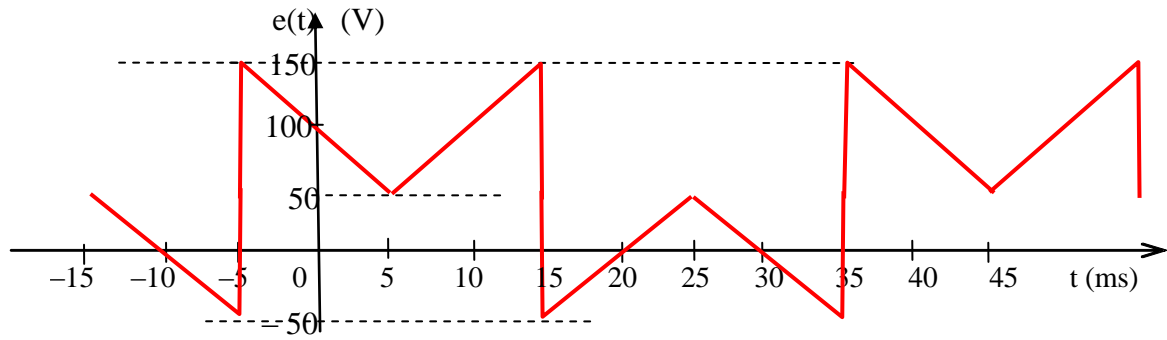


Figure Q5a

- (a) For the voltage waveform $e(t)$ shown in figure Q5a, write down any simplifications that can be used to determine the Fourier series and determine the first 4 significant terms of the Fourier series. [7 marks]
- (b) If a current $i(t) = 1 + 10 \sin 100t + 3 \sin (300t + \pi/3) + 2 \sin(500t - \pi/6)$ is passed through a series combination of a resistor $R = 10 \Omega$ and an inductor $L = 100 \text{ mH}$, determine the Fourier series of the resulting voltage $v(t)$. [2 mark]

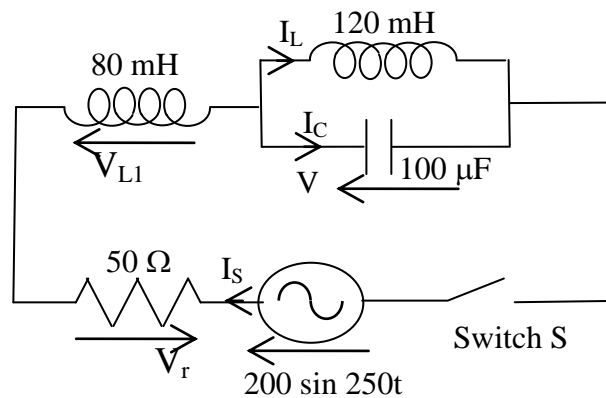


Figure Q5c

- (c) Figure Q5c shows a circuit which is switched at time $t = 0$. Draw the corresponding Laplace transformed circuit [1 mark]
- Write an expression for the current $I_s(s)$ in the Laplace domain [2 marks]
- Hence show how the corresponding current $i_s(t)$ may be determined. [2 marks]

[END OF QUESTION PAPER]