




UEE 201 - THEORY OF ELECTRICITY - Answers

Final Part I Examination Repeat - July 2002


A1 (a) Effective reluctance $S = \frac{l_0}{\mu A} + \frac{l_{air}}{\mu_0 A}$
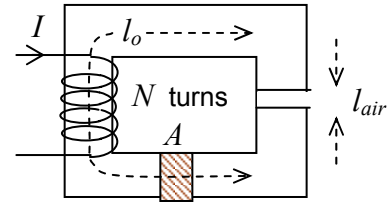
$$\text{Inductance} = \frac{N^2}{\frac{l_0}{\mu A} + \frac{l_{air}}{\mu_0 A}}$$



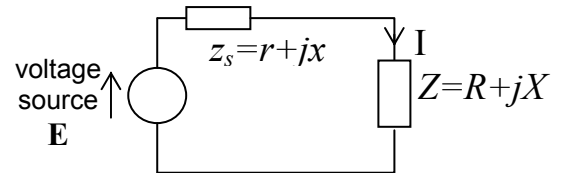(b) $I = \sqrt{\frac{P}{R}}$

$$E = \sqrt{\frac{(R+r)^2 + (X+x)^2}{R}} \cdot P$$





(c) at resonance $L\omega = 1/C\omega$

$L = 2.533 \text{ mH}$

$Q = (R+r)/L\omega = 1.005$

(d) $V_{oc} = 60 \angle 53.13^\circ \text{ V}$, $Z_{th} = 24 \angle 53.13^\circ \Omega = 14.4 + j19.2$


Thevenin's circuit

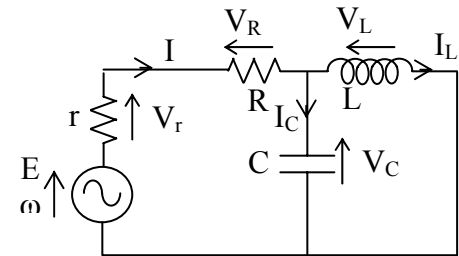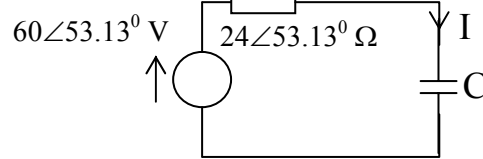


(e) $C \rightarrow -j 333.3 \Omega$, $L \rightarrow j 30 \Omega$

Taking V_C as vertical,


Phasor diagram

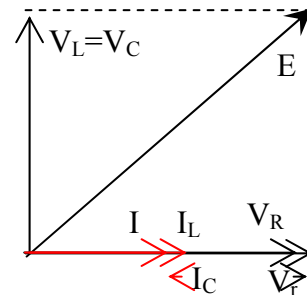

(f) $Z_{AB} = 3 - j 12 \Omega$

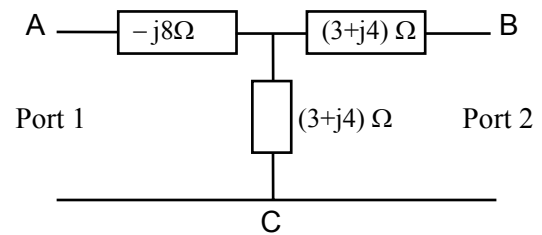

(g)

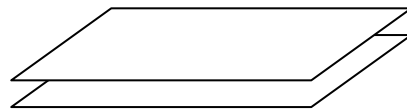

$C = 50 \text{ pF}$


thickness $d = 15.5 \mu\text{m}$



UEE 201 - THEORY OF ELECTRICITY - Answers

A2. Uncoupled equivalent circuit

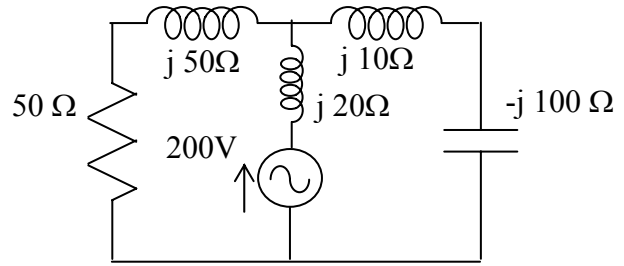- Current supplied = $2.016 \angle -5.22^\circ$ A
- Power supplied = 401.6 W
- Supply power factor = 0.996 lag




A3. $R_1 + R_2 = 123.46 \Omega$

$|Z_1| = |Z_2| = |Z| = 127.78 \Omega$

$X_1 + X_2 = \pm 32.94 \Omega$

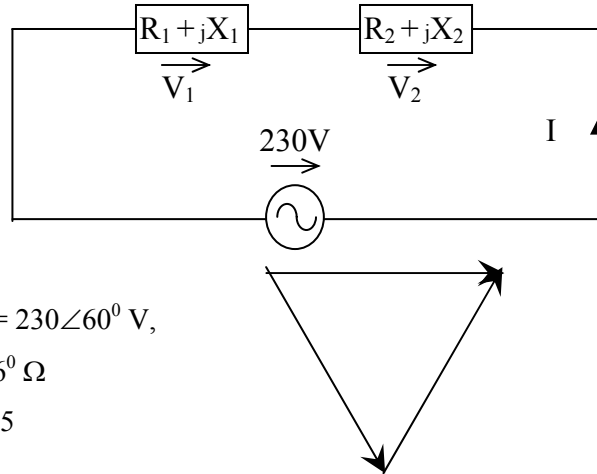$\cos \phi = 0.9662, \phi = \pm 14.94^\circ$



One solution

$E = 230 \angle 0^\circ$ V, $V_1 = 230 \angle -60^\circ$ V, $V_2 = 230 \angle 60^\circ$ V,

$Z_1 = 127.78 \angle -74.94^\circ$ or $127.78 \angle -45.06^\circ \Omega$
 $= 33.20 - j123.39$, or $90.26 - j90.45$

$Z_2 = 90.26 + j90.45$, or

Thus for this solution

$R_1 = 33.20 \Omega$, $X_1 = 123.29 \Omega$ inductive, $R_2 = 90.26 \Omega$, $X_2 = 90.45 \Omega$ capacitive,

- A4. (i) Current supplied to Load = $4.62 \angle -36.87^\circ$ A
- (ii) Active power supplied to load = 2.56 kW
- (iii) Line voltage at supply = $413.9 \angle 0.73^\circ$ V
- (iv) Power factor at supply = 0.792 lag



Reactive power at load = 1.92 k var, new power factor = 0.95 giving $\phi_{new} = 18.19^\circ$

New reactive power required = 0.841 k var

Thus reactive power supplied by each capacitor = $(1.92 - 0.841)/3 = 0.36$ k var

Value of each capacitor = 7.1 μ F each.

A5. (a) Equivalent voltage source

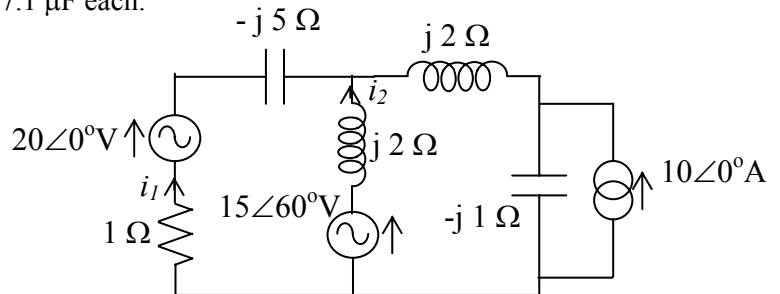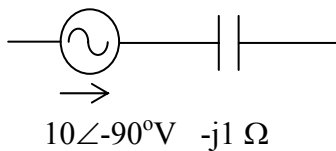

(b) Mesh impedance matrix

$$[Z_m] = \begin{bmatrix} 1 - j3 & -j2 \\ -j2 & j3 \end{bmatrix}$$

(c) Mesh voltage source vector


$$E_{gm} = \begin{bmatrix} 18.02 \angle -46.10^\circ \\ 24.18 \angle 71.93^\circ \end{bmatrix}$$

(d) $i_1 = 3.97 \angle 84.6^\circ$ A




UEE 201 - THEORY OF ELECTRICITY - Answers

A6.

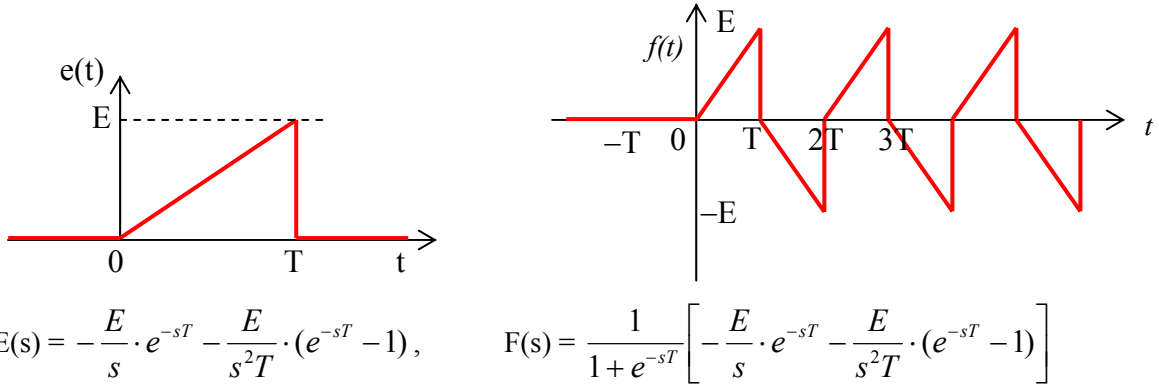

$$E(s) = -\frac{E}{s} \cdot e^{-sT} - \frac{E}{s^2 T} \cdot (e^{-sT} - 1), \quad F(s) = \frac{1}{1 + e^{-sT}} \left[-\frac{E}{s} \cdot e^{-sT} - \frac{E}{s^2 T} \cdot (e^{-sT} - 1) \right]$$

A7. (a)

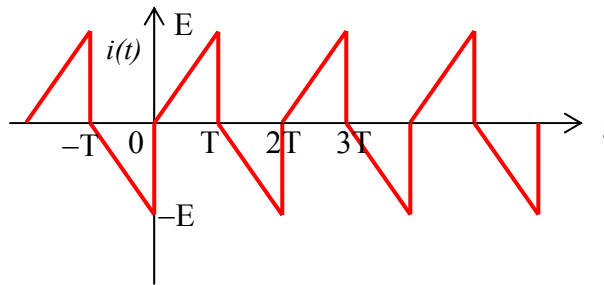


mean = $a_0/2 = 0$, half wave symmetry \rightarrow no even harmonics, period = $2T$

$$a_n = -\frac{4E}{n^2 \pi^2}, \quad b_n = \frac{2E}{n\pi}$$

$$i(t) = \left(-\frac{4E}{\pi^2} \cos \omega_0 t + \frac{2E}{\pi} \sin \omega_0 t \right) + \left(-\frac{4E}{9\pi^2} \cos 3\omega_0 t + \frac{2E}{3\pi} \sin \omega_0 t \right) + \left(-\frac{4E}{25\pi^2} \cos 5\omega_0 t + \frac{2E}{5\pi} \sin 5\omega_0 t \right) + \left(-\frac{4E}{49\pi^2} \cos 7\omega_0 t + \frac{2E}{7\pi} \sin 7\omega_0 t \right) + \dots$$

(b)

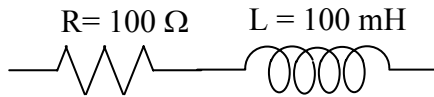

$$v = R i + L p i$$

fundamental term of voltage

$$v(t) = 100 \times \left(-\frac{4E}{\pi^2} \cos \omega_0 t + \frac{2E}{\pi} \sin \omega_0 t \right) + 100 \times 10^{-3} \times \left(\frac{4E}{\pi^2} \omega_0 \sin \omega_0 t + \frac{2E}{\pi} \omega_0 \cos \omega_0 t \right)$$