

**UEE 201 - THEORY OF ELECTRICITY - Answers****Final Part I Examination 1994/95 - October 1996**

A1 (a) $Z_{AB} = 10 - j 7.5 \Omega$

(b) $Y_N = \frac{Z_1 + Z_2}{Z_1 Z_2}$, $I_N = I + \frac{E}{Z_1}$


(c) $I = I_1 \cdot \frac{E_3}{E_1} + I_2 \cdot \frac{E_4}{E_2}$

(d) 1200 W

(e) $E = j\omega L_1 i_1 + j\omega M i_2 + Z_1 (i_1 - i_2)$

(f) $290 \angle 90^\circ \text{ V}$

(g) $9.708 \angle 12.22^\circ \text{ A}$

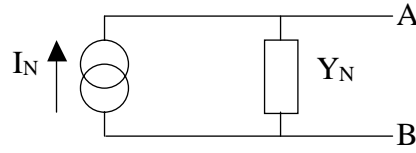

A2 $P_{\max} = \frac{1.05 E^2}{x}$, $R = 0.499 x$, $X = -0.4756 x$

A3 $L_1 = 39.79 \text{ mH}$, $R_2 = 19.2 \Omega$, $L_2 = 45.84 \text{ mH}$, $R_3 = 0 \Omega$, $C_3 = 79.58 \mu\text{F}$

A4 (a) 5.37 A, (b) 383.5 V, (c) 0.942 lag
3 of 6.24 μF , 404.1 V

A5 8A current source in shunt with a 1 Ω resistor.

Branch-Node incidence matrix = $\begin{bmatrix} 1 & 0 \\ -1 & 1 \\ 0 & 1 \end{bmatrix}$, Branch admittance matrix = $\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$

Nodal Admittance matrix = $\begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ -1 & 1 \\ 0 & 1 \end{bmatrix}$

10 A, 11 A, 1 A, 4 A

A6 (a) $\begin{bmatrix} 6 + j2 & 4 - j2 \\ 4 - j2 & 6 + j2 \end{bmatrix} \Omega$ (b) $\begin{bmatrix} 3.000 \angle 15^\circ \\ 0.000 \\ 3.000 \angle 135^\circ \end{bmatrix} \text{ A}$

A7 $0.1575 \sin(314.16t + 2.3^\circ) + 0.1384 \sin(3 \times 314.16t - 172.7^\circ) + 0.1050 \sin(5 \times 314.16t + 14.0^\circ) + 0.656 \sin(7 \times 314.16t - 153.9^\circ) + \dots \text{ A}$

Form factor = 2.3 (or 2.15 with approximations)

Peak factor = 2.72 (or 2.91 with approximations)

Power Consumed = 25.57 W

Overall power factor = 0.605 (or 0.674 with approximations)

A8 $\frac{E_m}{L\omega} [0.6e^{-0.333\omega t} - 0.1154e^{-0.666\omega t} + 0.7894\sin(\omega t - 37.87^\circ)] \text{ A}$

$E_m [-0.2e^{-0.333\omega t} + 0.0769e^{-0.666\omega t} + 0.7894\cos(\omega t - 37.87^\circ)] \text{ V}$