

## UEE 201 - THEORY OF ELECTRICITY

0900 - 1200 hrs

30 June 1999

Answer **FIVE** Questions Only. Question 1 carries 28 marks, and all other Questions carry 18 marks each

Permeability of free space  $\mu_0 = 4 \pi \times 10^{-7}$  H/m

Permittivity of free space  $= 8.854 \times 10^{-12}$  F/m

- 1 (a) Calculate the value of the impedance  $Z_{AC}$  in the delta equivalent of the circuit shown in figure Q1abc. [4 marks]

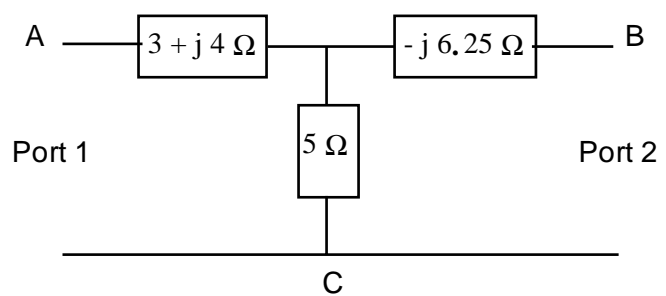


Figure Q1 abc

- (b) Obtain the parameters **A** and **C** in the transmission line parameters for the two port network shown in figure Q1abc. [3 marks]

- (c) If an alternating voltage of 100V is applied across Port 1 of the circuit shown in figure Q1abc, determine the Thevenin's equivalent circuit across Port 2. [4 mark]

- (d) Write down the Kirchoff's Voltage law equation for the loop 1 in figure Q1d and express it in a simplified form. [3 mark]

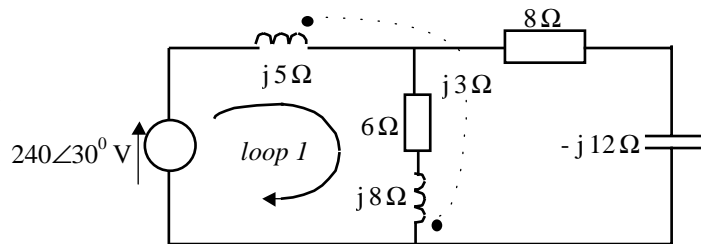


Figure Q1d

- (e) An alternating voltage source of 200 V, has an internal impedance of  $(1 + j 2)$   $\Omega$ . It supplies a variable load of power factor 0.8 lagging. Determine the values of resistance and reactance of the load when receiving maximum power from the supply. [6 mark]

- (f) For the periodic waveform shown in figure Q1f, determine the **mean value**, **average value**, **rms value** and **form factor**. [4 mark]

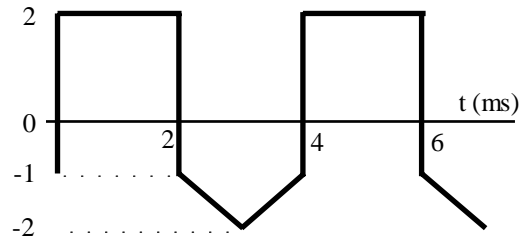


Figure Q1f

- (g) A toroid of magnetic material ( $\mu_r = 1500$ ) of length 20 cm and cross section area  $0.8 \text{ cm}^2$  has a cut of 1 mm in its circumference. 500 turns are uniformly wound on the circumference. Determine the total reluctance of the magnetic path and the inductance of the coil. [4 marks]

- 2 For the circuit shown in figure Q2, determine from first principles the currents in all the branches. The mutual inductances between the inductances  $L_1$ ,  $L_2$  and  $L_3$  are  $M_{12}$ ,  $M_{23}$  and  $M_{31}$ .

The component values are  $R_1 = 0.36R$ ,  $R_2 = R_3 = R$ ,  $X_{L1} = X_{L2} = X_{L3} = 1.2R$ ,  $X_{M12} = X_{M23} = X_{M31} = R$  and  $E/R = 7$ . [18 marks]

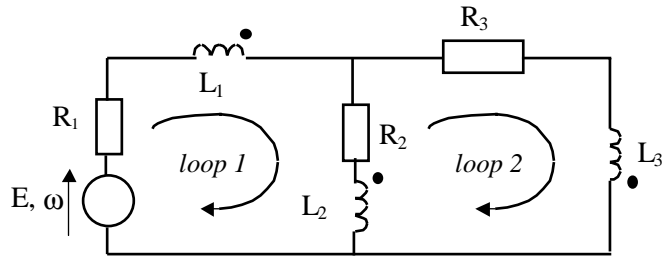


Figure Q2

- 3 A certain circuit consists of two components  $Z_1$  and  $Z_2$  in series. When an alternating voltage of magnitude 234 V is applied across the combination, the magnitude of the current is measured to be 1.8 A. With this current, the active power loss in the circuit is measured to be 417.7 W and the voltage magnitudes across  $Z_1$  and  $Z_2$  are each found to be equal to 234 V. Determine possible values for the resistive and reactive components of  $Z_1$  and  $Z_2$ . [18 marks]

- 4 A 50 Hz, balanced, 3 phase source supplies a balanced load consisting of three impedances ( $R = 4 \Omega$  in series with  $L = 10$  mH each) connected in star, at 400 V. Determine (a) the line current, and (b) the active power consumed. [6 marks]

If each of the three wires connecting the load to the supply has an impedance of ( $r = 1 \Omega$ ,  $l = 5$  mH), determine (c) the line voltage at the supply, and (d) the power factor at the supply. [6 marks]

It is required to improve the load power factor to 0.95 by the use of a delta connected capacitor bank. Assuming that the load voltage remains at 400 V, determine (e) the values of the 3 capacitors required. [6 marks]

5

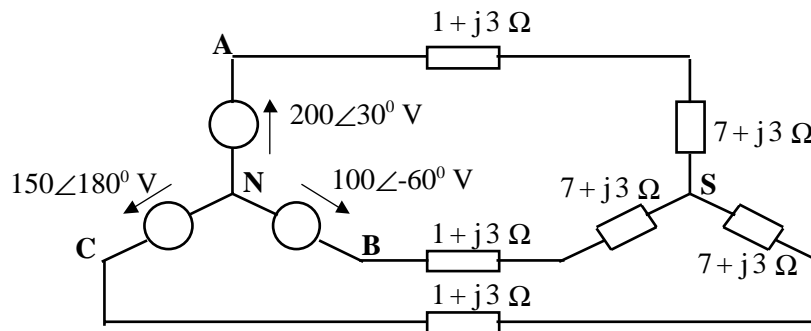


Figure Q5

Figure Q5 shows an unbalanced star connected source supplying a balanced star connected load through wires of equal impedance. Determine using Millman's theorem the current in each line. [8 marks]

Determine the symmetrical components of these three line currents. [6 marks]

Using the property that the load is balanced, determine the symmetrical components of the voltages across the load. [2 marks]

Determine the power consumed by the load. [2 marks]

- 6 (a) A certain two port network has an impedance matrix with  $z_{11} = 10 + j10$ ,  $z_{12} = j10$ ,  $z_{21} = j10$  and  $z_{22} = 10 + j10$ . Determine the corresponding two port transmission line parameter matrix. [4 marks]
- (b) For the circuit shown in figure Q6, write down the node-branch incidence matrix. [3 marks]
- Write down the Node admittance matrix by inspection [4 marks]
- Hence determine the voltages at nodes 1, 2 and 3. [7 marks]

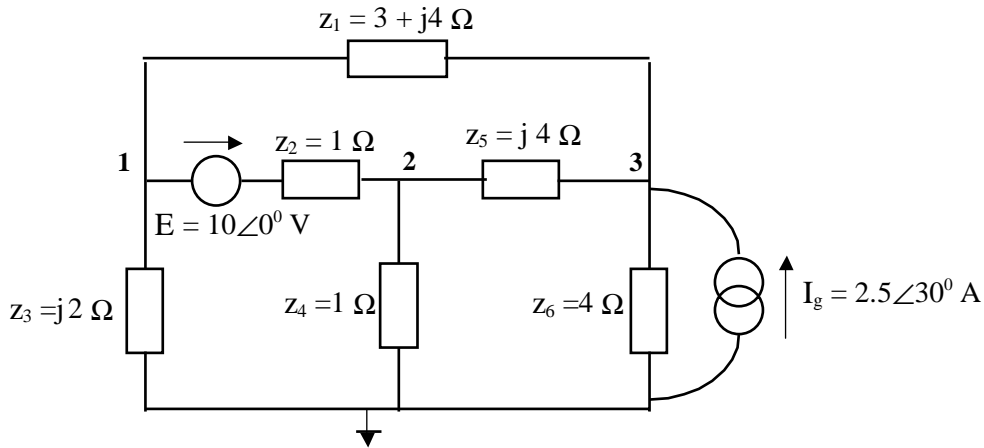


Figure Q6

- 7 Figure 7 shows the current passing through a certain power electronic device. Determine the Fourier series of this current to 3 significant terms. [14 marks]

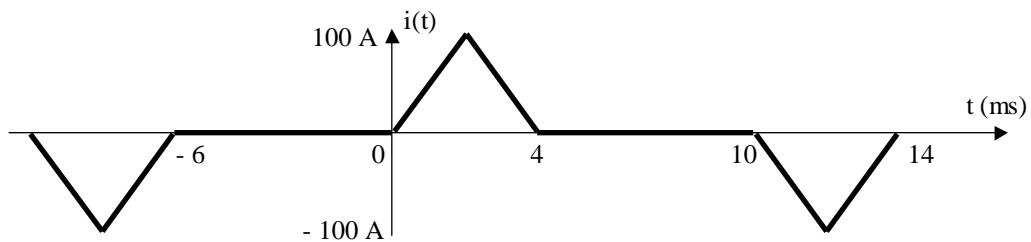


Figure Q7

This current is passed through a series combination of a resistance of  $100 \Omega$  and an inductance of  $100 \text{ mH}$ . Determine the fundamental term of the Fourier series of the voltage across the combination. [4 marks]

- 8 For the transient current waveform shown in figure Q8, determine from first principles the Laplace Transform. [6 marks]

This transient current passes through a series combination of an inductance  $L = 2 \text{ mH}$  and a resistance  $R = 1 \Omega$ .

- (a) Determine the transform of the voltage appearing across the combination. [6 marks]

- (b) Determine the inverse transform of the voltage and sketch the waveform of the voltage. [6 marks]

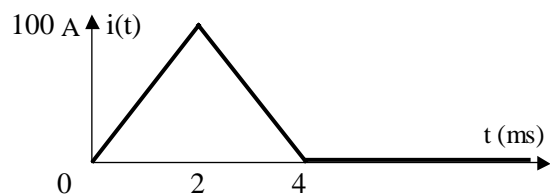


Figure Q8